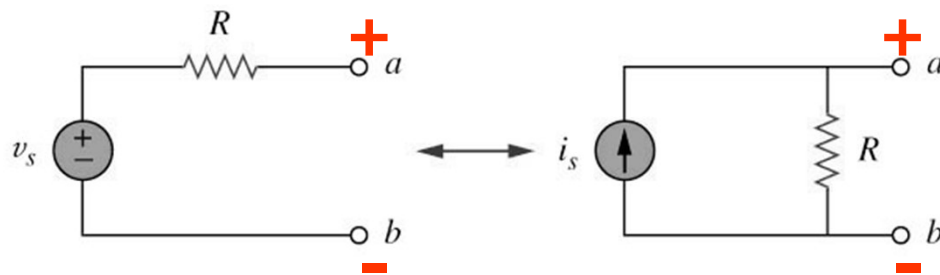



4.4 Source Transformation (1)

- An equivalent circuit is one whose v - i characteristics are identical with the original circuit.
- It is the process of replacing **a voltage source v_s in series with a resistor R** by **a current source i_s in parallel with a resistor R** , or vice versa.

4.4 Source Transformation (2)




(a) Independent source transform

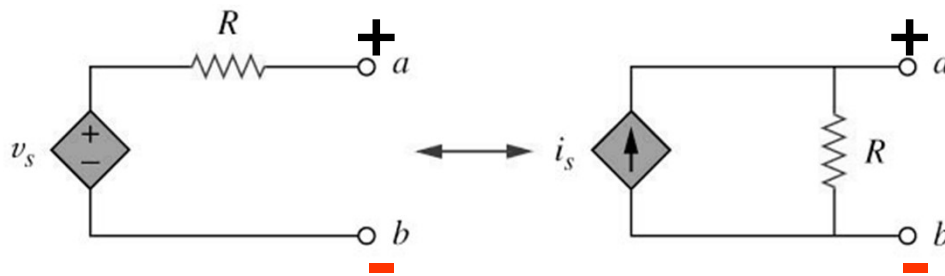


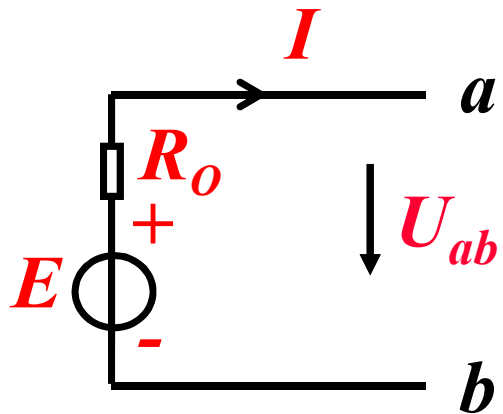(b) Dependent source transform

- The arrow of the current source is directed toward the positive terminal of the voltage source.
- The source transformation is not possible when $R = 0$ for voltage source and $R = \infty$ for current source.



$$U_{ab} = E - I \cdot R_o$$

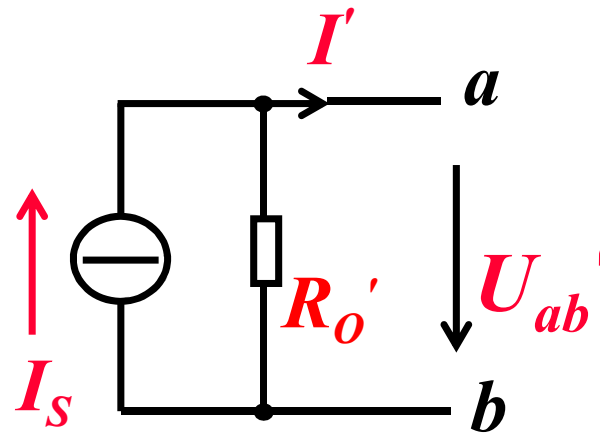

$$\begin{aligned} U_{ab}' &= (I_s - I') \cdot R_o' \\ &= I_s \cdot R_o' - I' \cdot R_o' \end{aligned}$$


if


$$\begin{aligned} I &= I' \\ U_{ab} &= U_{ab}' \end{aligned}$$







then $E - I \cdot R_o = I_s \cdot R_o' - I' \cdot R_o'$


$$E = I_s \cdot R_o'$$

$$R_o = R_o'$$


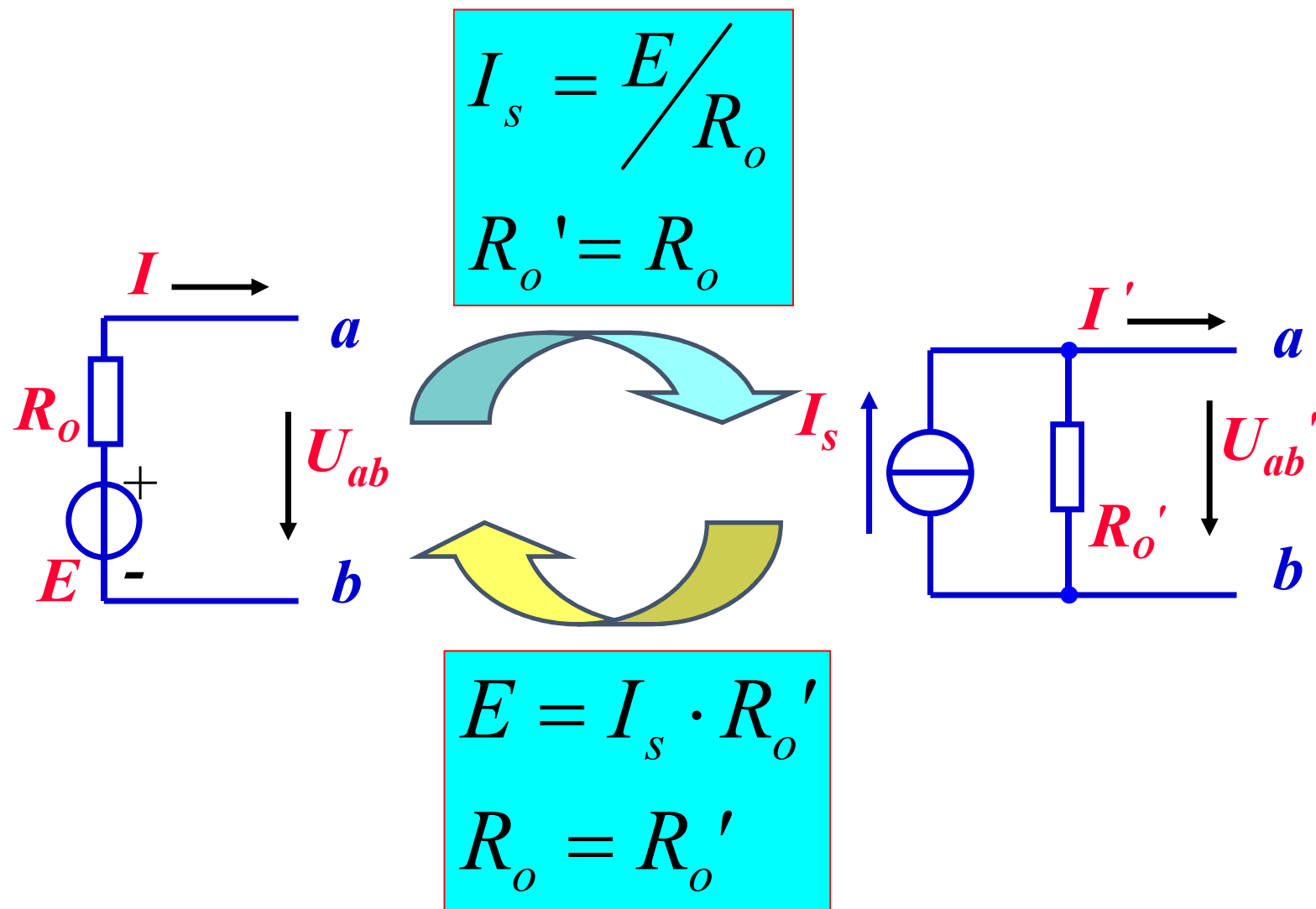


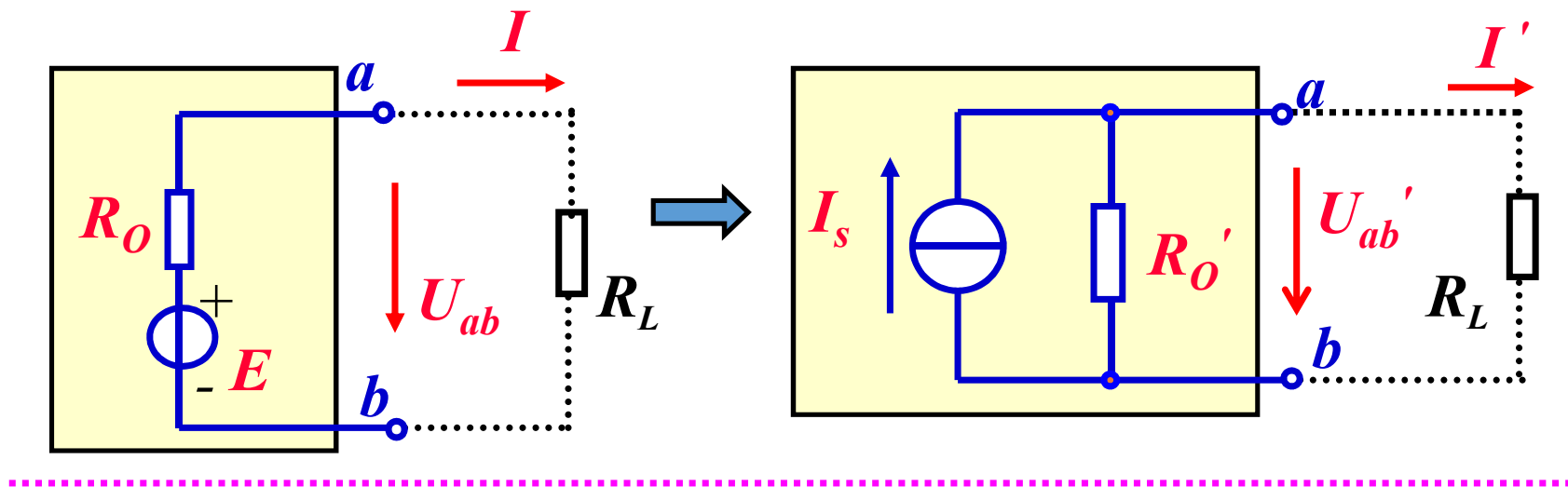

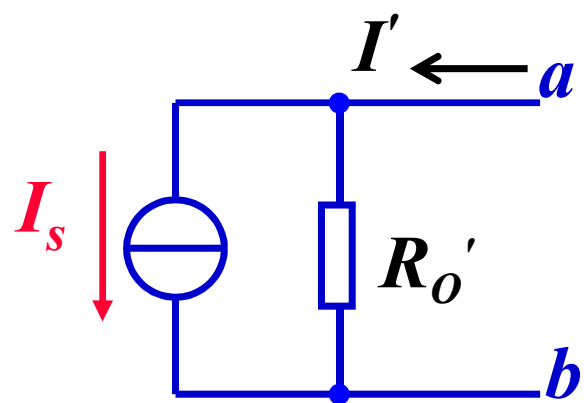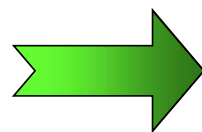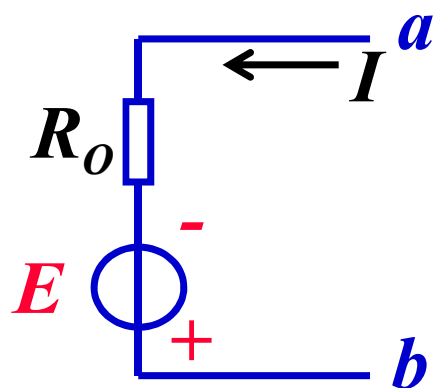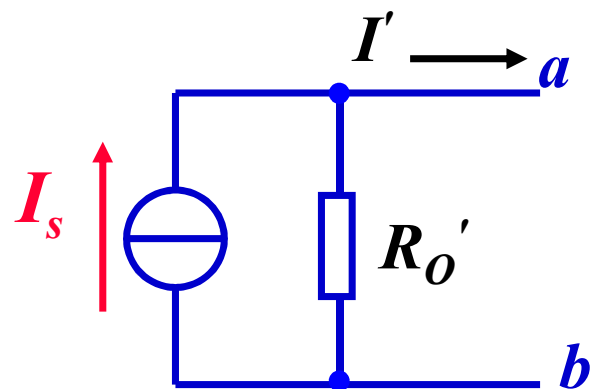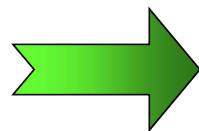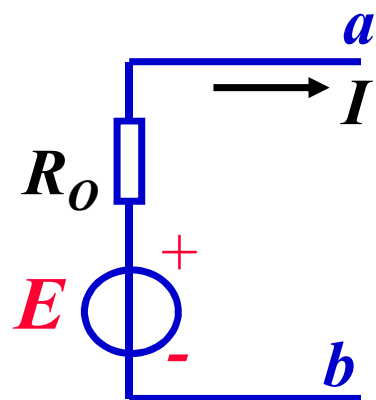

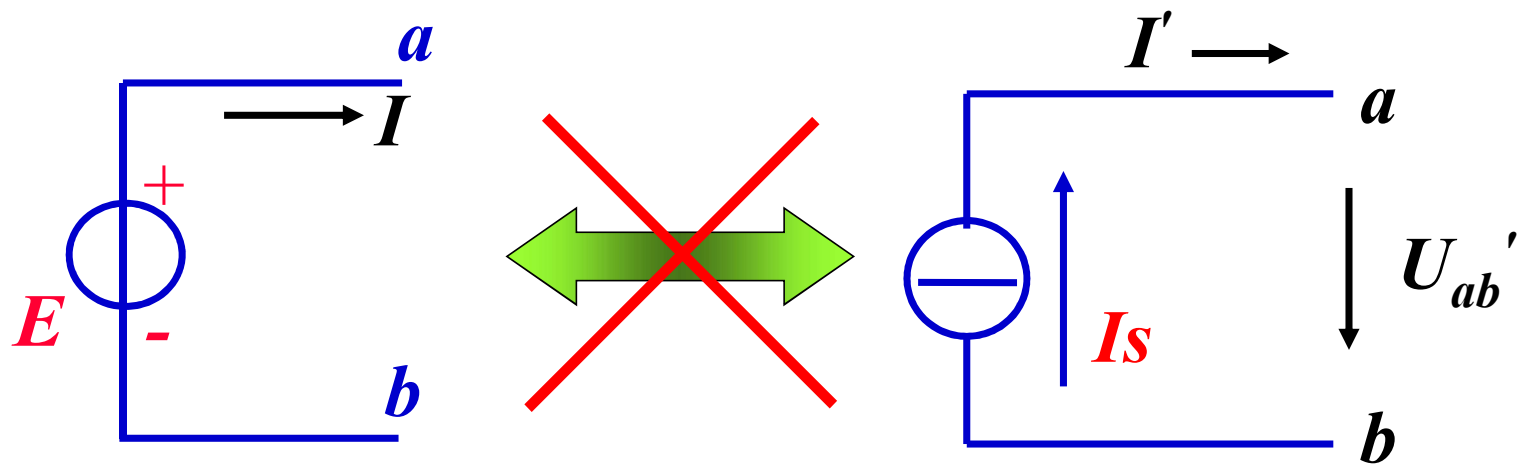



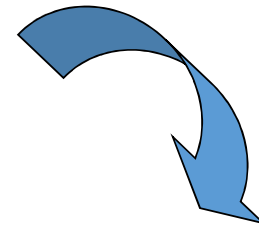
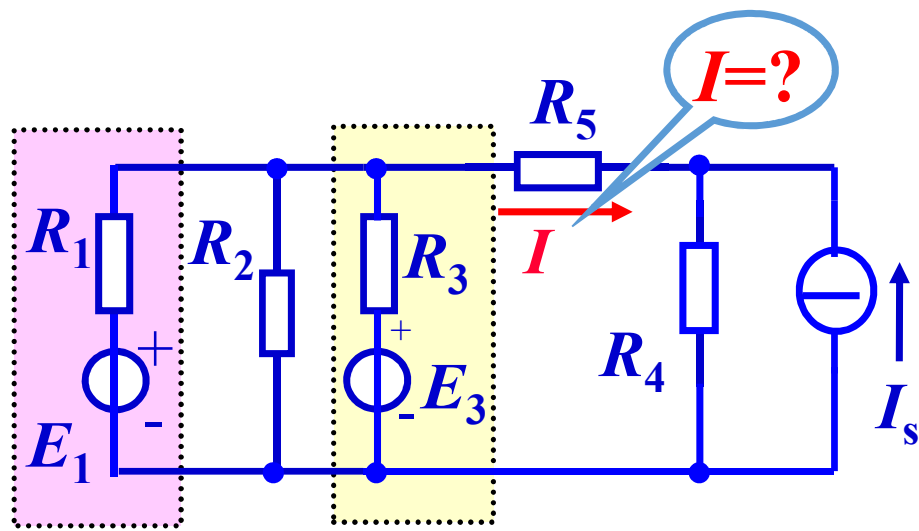
$$I_s = \frac{E}{R_o} = \frac{E}{0} = \infty$$




$$I_1 = \frac{E_1}{R_1}$$

$$I_3 = \frac{E_3}{R_3}$$

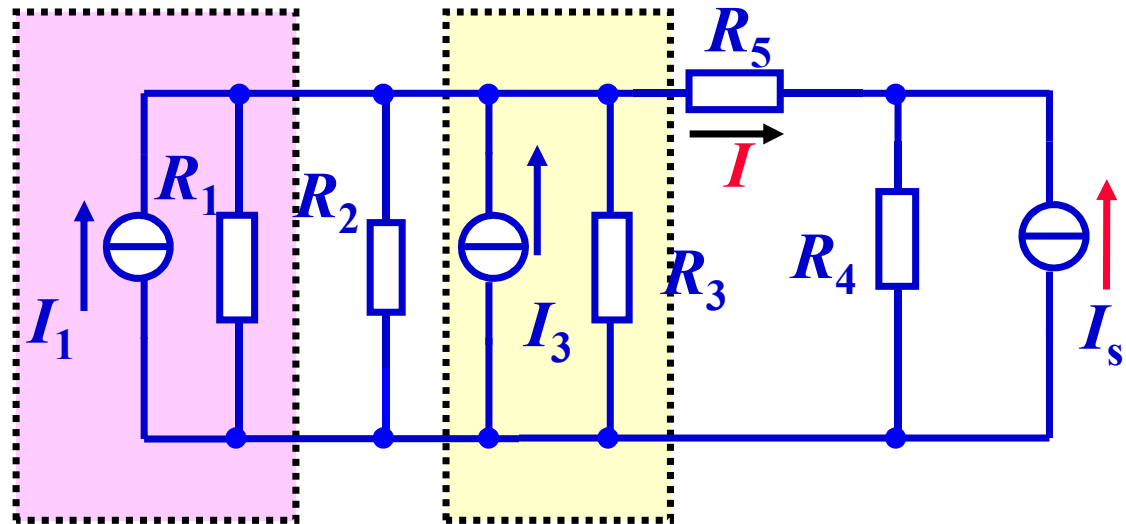

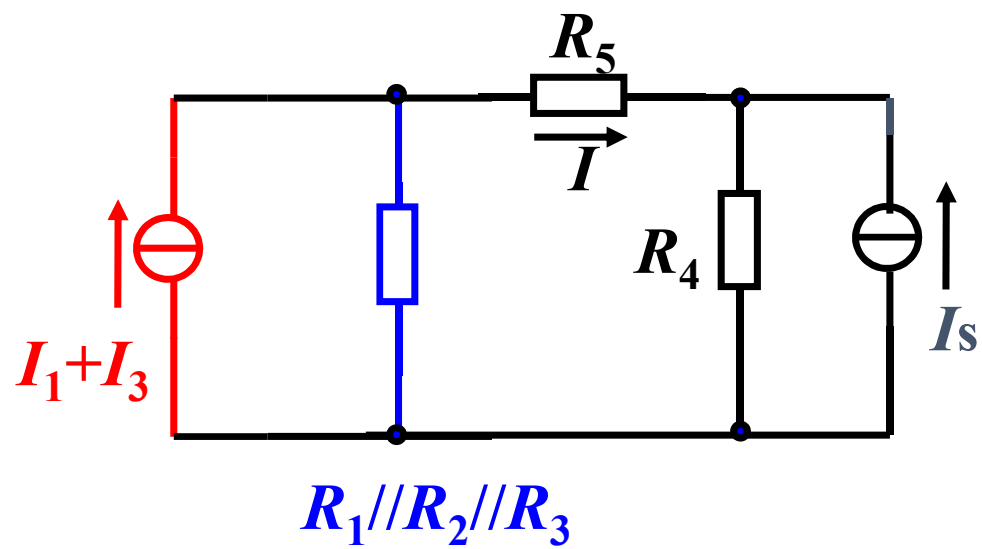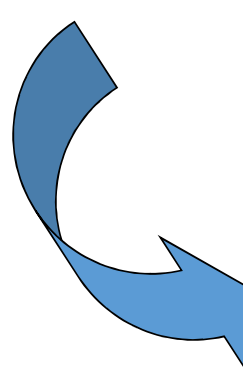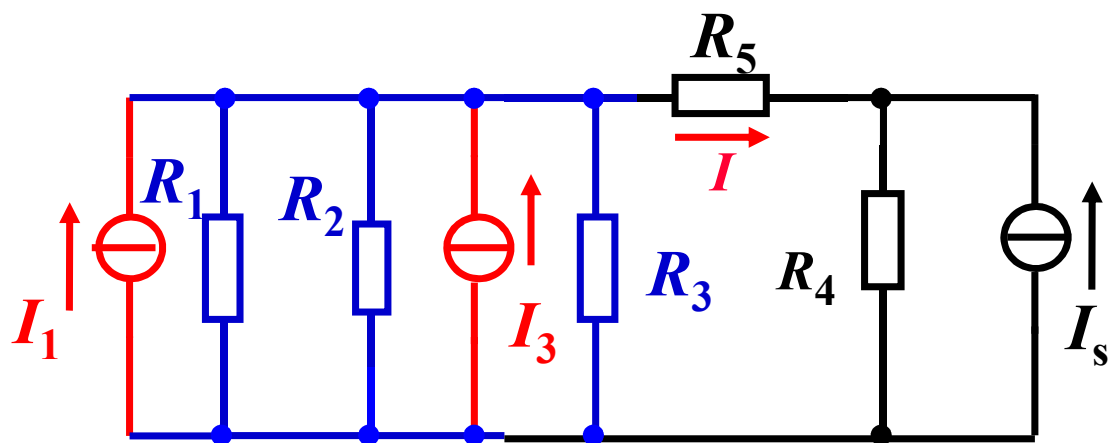

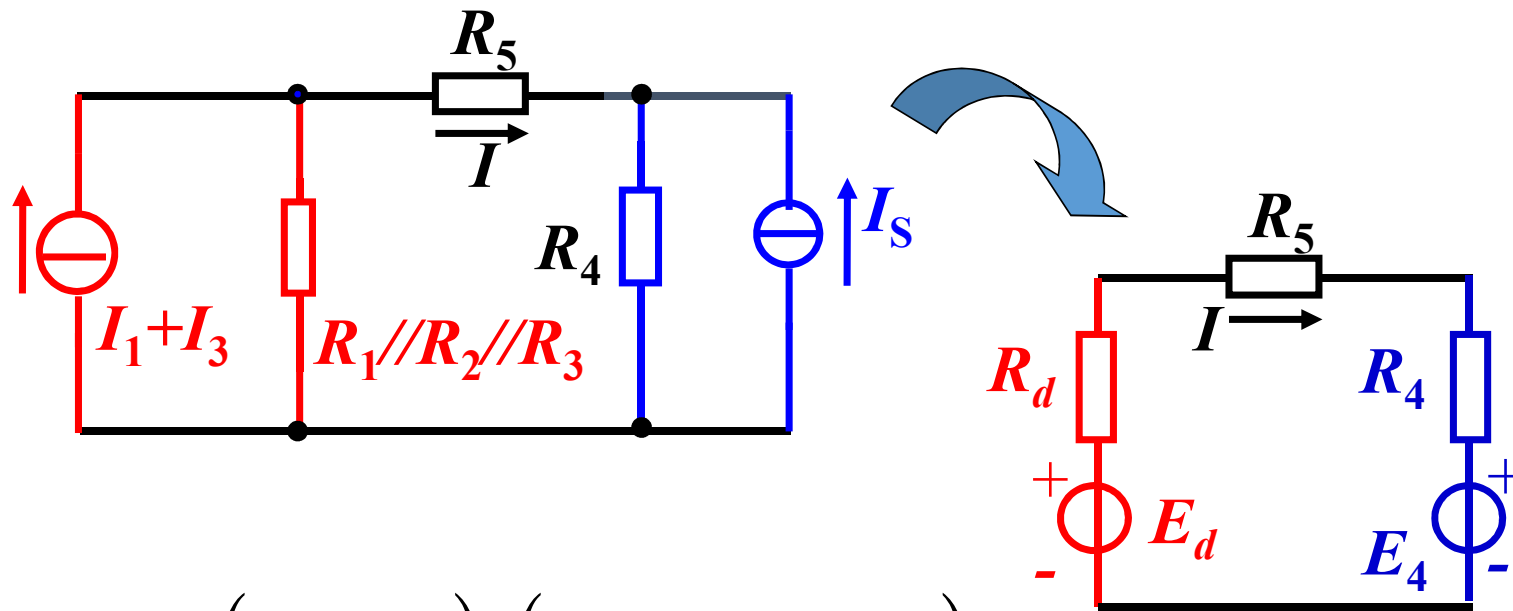


$$\begin{cases} E_d = (I_1 + I_3) \cdot (R_1 // R_2 // R_3) \\ R_d = R_1 // R_2 // R_3 \\ E_4 = I_S \cdot R_4 \end{cases}$$


$$I = \frac{E_d - E_4}{R_d + R_5 + R_4}$$



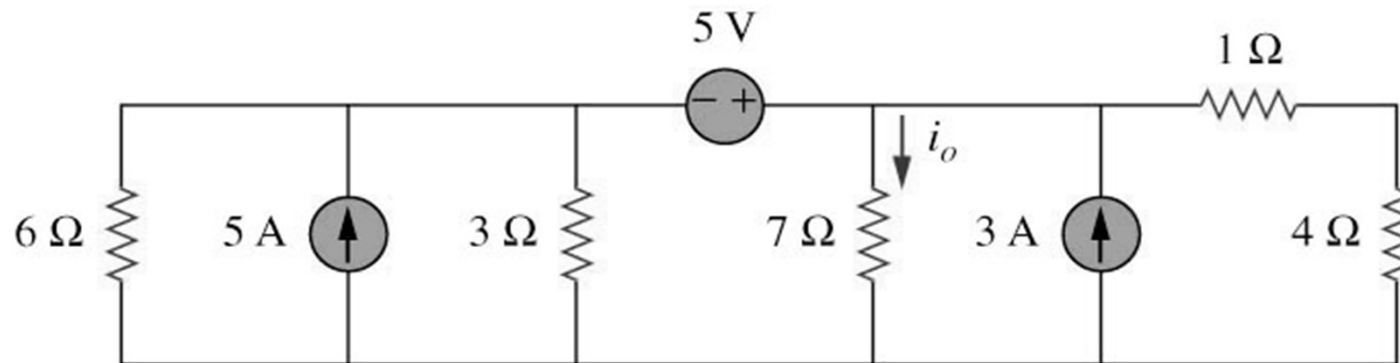
Example 4

Find i_o in the circuit shown below using source transformation.




$$i_o = 1.78\text{A}$$

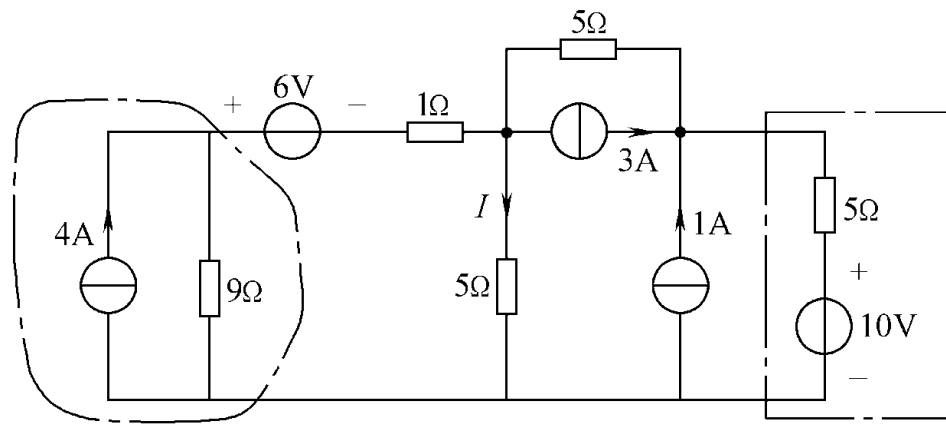

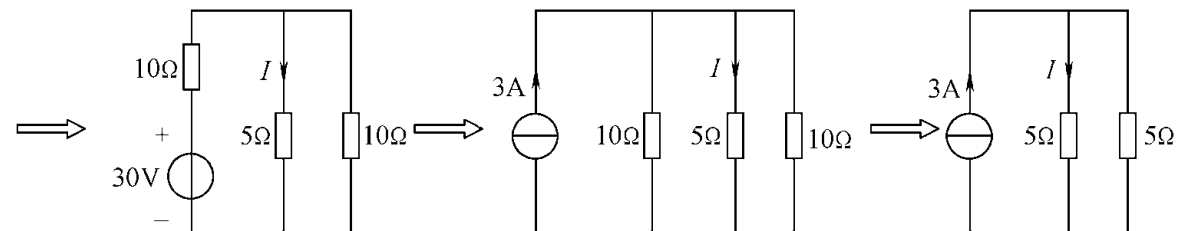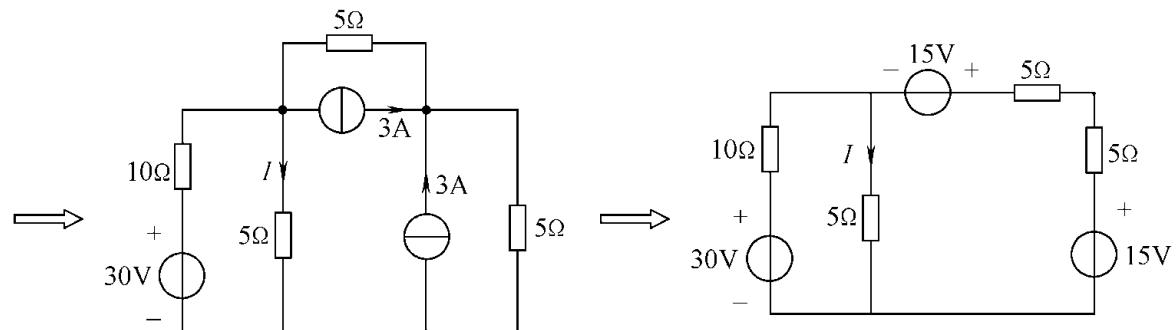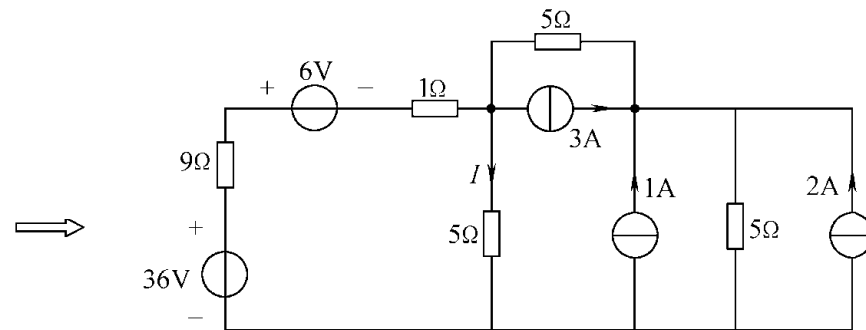


$$I = 1.5A$$
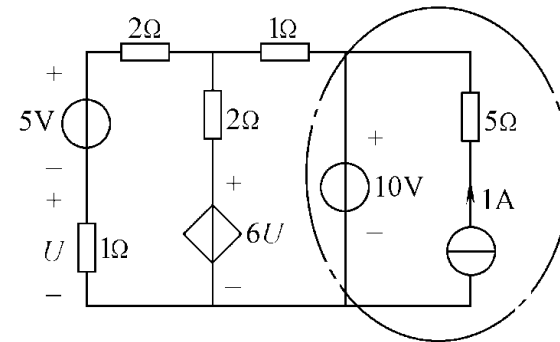
$$U = \frac{(10 + 3U) \cdot \frac{2}{3} - 5}{3 + \frac{2}{3}} \times 1$$



$$U = 1V$$

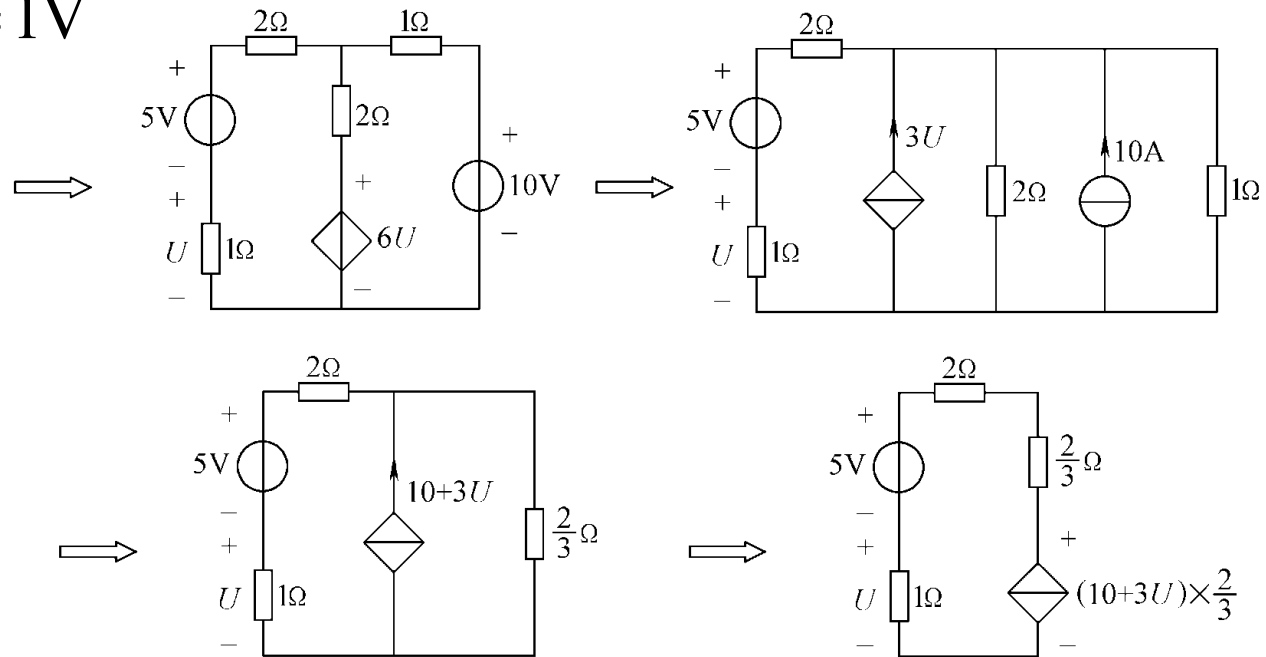

§ 1-7 支路电流法

对一个具有 b 条支路和 n 个结点的电路，以**支路电流为独立变量**，根据**KCL**列 $(n-1)$ 个独立方程、根据**KVL**列 $(b-n+1)$ 个**独立方程**，解得各支路电流。

步骤：

(1) 设定各支路 i 的参考方向；

(2) 根据KCL对 $(n-1)$ 个独立**结点**列**方程**；


(3) 选取 $(b-n+1)$ 个独立回路，指定回路的**绕行方向**，列出KVL**回路方程**。

步骤:

(1) 设定各支路 i 的参考方向;

(2) 根据KCL对 $(n-1)$ 个独立**结点**列**方程**;

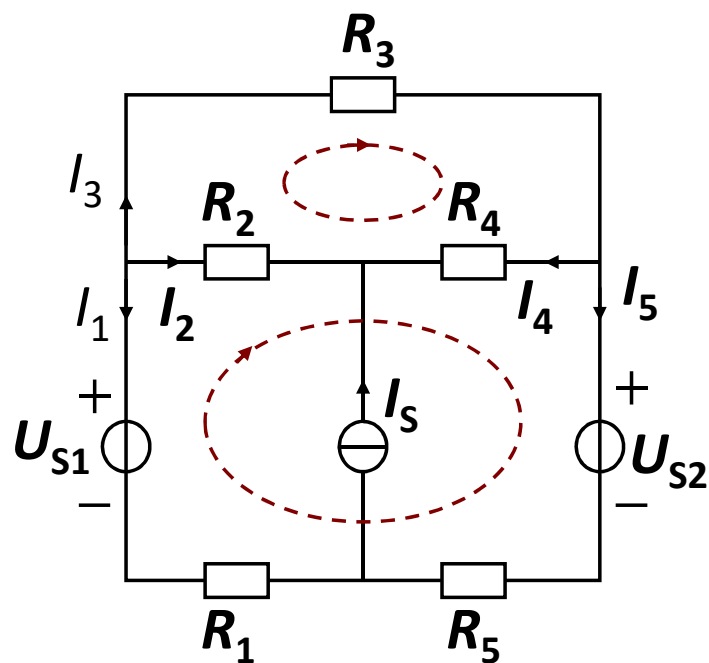(3) 选取 $(b-n+1)$ 个独立回路, 指定回路的**绕行方向**, 列出KVL**回路方程**。



例:用支路电流法求图中各支路电流, 并说明 U_1 、 U_2 是提供还是吸收功率。

