

Sinusoidal Steady-State Analysis Steps

- ① Transform the **circuit** to the phasor or frequency domain.
Transform all independent **sources to their phasor** equivalent.
 $u, i \longrightarrow \dot{U}, \dot{I}$
Calculate the **impedance (Z)** of all passive circuit elements.
 $R, L, C \longrightarrow Z, Y$
- ② Apply analysis method in the frequency domain.
- ③ Transform the resulting phasor to the time domain.

Nodal and Mesh Analysis, Superposition, Source Transformations, and Thevenin's theorem...

80

9.8 Phasor Diagrams

Provide a graphical (geometrical) method for solving circuit.

Key 1: Choose appropriate reference phasor


Current for series circuits; voltage for parallel circuits

Key 2: Current and voltage relation for **elements** and **branches**

$\left\{ \begin{array}{l} \text{Resistor} \\ \text{Inductor} \\ \text{Capacitor} \end{array} \right.$	i and u in phase; i lags u by 90° ; i leads u by 90° .	$\left\{ \begin{array}{l} \text{RL branches, } i \text{ lags } u \text{ by } \varphi. \\ \text{RC branches, } i \text{ leads } u \text{ by } \varphi; \end{array} \right.$
	$0 < \varphi < 90^\circ$	

81

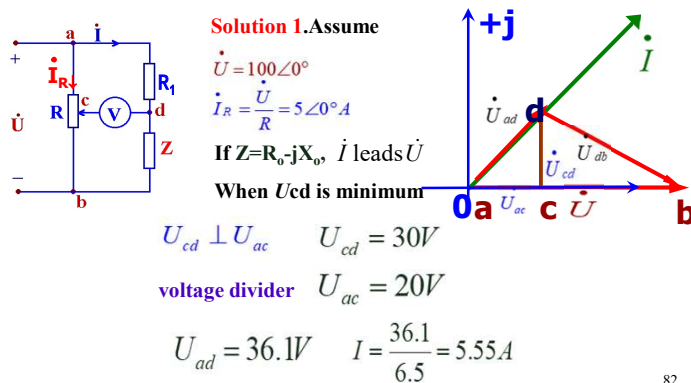Example 9. In the following circuit, $U=100V$, $R=20\Omega$, $R_1=6.5\Omega$. C is moveable. If $R_{ac}=4\Omega$, the minimum U_{cd} can be reached and the value is $30V$. Try to find Z .



82

$$\because \triangle adc \cong \triangle abe \quad \frac{U_{ad}}{U_{cd}} = \frac{U}{U_{eb}} \quad \begin{array}{l} U_{ad} = 36.1V \\ U_{cd} = 30V \\ U_{ac} = 20V \end{array} \Rightarrow U_{eb} = 83.1V$$

$$Z = R_0 + jX_0$$

$$x_0 = \frac{U_{eb}}{I} = 15\Omega$$


$$\because \triangle adc \cong \triangle abe \quad \frac{U_{ae}}{U_{ab}} = \frac{U_{ac}}{U_{ad}}$$

$$U_{ae} = 55.4V$$

$$R_0 = \frac{U_{ae}}{I} - R_1 = 3.51\Omega$$

$$\therefore Z = 3.5 - j15(\Omega)$$

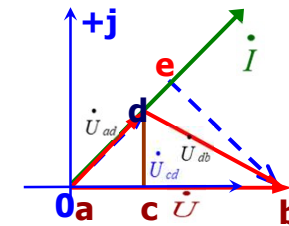
In the similar way, $Z = 3.5 + j15(\Omega)$



83

Solution 2. Assume

$$\dot{U} = 100\angle 0^\circ$$

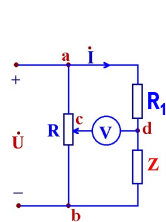

$$\dot{U}_{ac} = \frac{R_{ac}}{R} \dot{U} \quad \dot{U}_{ad} = \frac{R_1}{R_1 + Z} \dot{U}$$

$$\dot{U}_{cd} = \dot{U}_{ad} - \dot{U}_{ac}$$

$$= \left(\frac{R_1}{R_1 + Z} - \frac{R_{ac}}{R} \right) \dot{U}$$

R_{ac} changes accompanying with the movement of C.

If U_{cd} is minimum

$$\left(\frac{6.5}{6.5 + Z} - \frac{4}{20} \right) 100\angle 0^\circ = \pm j30$$

$$\therefore Z = 3.5 \pm j15(\Omega)$$

84

9.9 AC Circuit Power Analysis

(交流电路功率分析)

9.9.1 Instantaneous Power (瞬时功率)


$p(t) = u(t)i(t)$ (associated direction is assumed)

$$R: p(t) = u(t)i(t) = i^2(t)R = \frac{u^2(t)}{R}$$

$$C: p(t) = u(t)i(t) = cu(t) \frac{du(t)}{dt} = \frac{1}{c} i(t) \int_{-\infty}^t i(t') dt' u$$

$$L: p(t) = u(t)i(t) = Li(t) \frac{di(t)}{dt} = \frac{1}{L} u(t) \int_{-\infty}^t u(t') dt'$$

Network: $p(t) = u(t)i(t)$

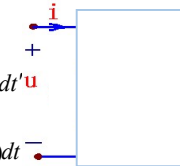

85

Power due to sinusoidal excitation

$$u(t) = \sqrt{2}U \cos \omega t \quad i(t) = \sqrt{2}I \cos(\omega t - \varphi) \quad \varphi = \varphi_u - \varphi_i$$



$$p(t) = u(t)i(t) = 2UI \cos \omega t \cos(\omega t - \varphi)$$

$$\text{Thus } = UI \cos \varphi + UI \cos(2\omega t - \varphi) \quad \text{Unit: W}$$

constant

sinusoidal
 $T = T/2$

$$R: p(t) = UI + UI \cos 2\omega t$$

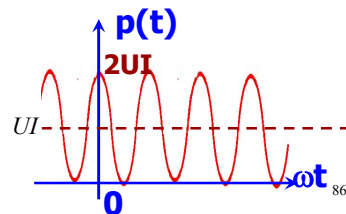
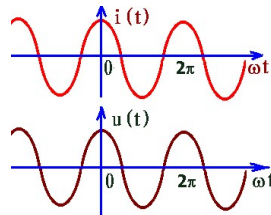


86

$$L: \varphi = \varphi_u - \varphi_i = 90^\circ$$

$$p = UI \cos \varphi + UI \cos(2\omega t - \varphi)$$

$$= UI \cos(2\omega t - 90^\circ)$$

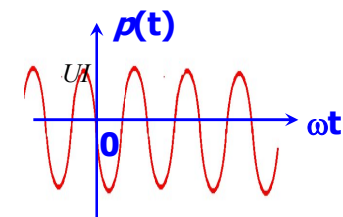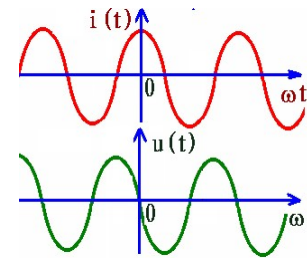


87

C: $\varphi = \varphi_u - \varphi_i = -90^\circ$


$$p = UI \cos \varphi + UI \cos(2\omega t - \varphi)$$

$$= UI \cos(2\omega t + 90^\circ)$$

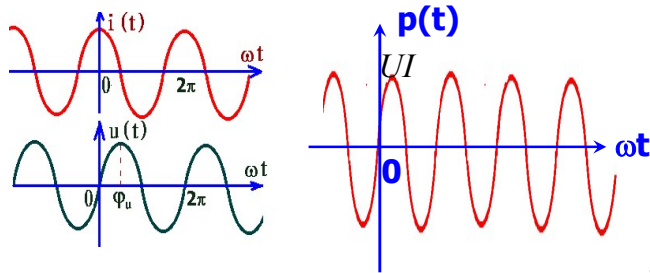

88
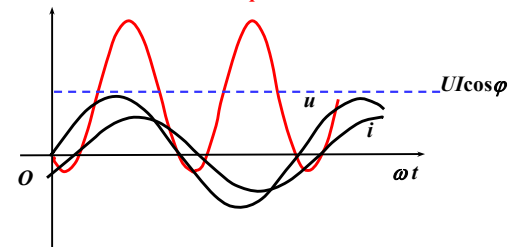
$$p = UI \cos \varphi + UI \cos(2\omega t - \varphi)$$



$p(t)$ could be positive or negative for different time

$p(t) > 0$, absorbed power; (吸收功率)

$p(t) < 0$, developed power; (发出功率)

89

9.9.2 Average Power

(平均功率, 有功功率-Active Power)

$$P = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(t) dt$$

1. Average energy for periodic waveforms

$$P = \frac{1}{T} \int_0^T p(t) dt$$

2. Average energy in the sinusoidal steady state

$$u(t) = \sqrt{2}U \cos \omega t \quad i(t) = \sqrt{2}I \cos(\omega t - \varphi) \quad \varphi = \varphi_u - \varphi_i$$

$$p = UI \cos \varphi + UI \cos(2\omega t - \varphi)$$

$$P = \frac{1}{T} \int_0^T p(t) dt = UI \cos \varphi \quad \text{Unit: W}$$

$\cos \varphi$: power factor(功率因数);


$\varphi = \varphi_u - \varphi_i$: power-factor angle

90

R: $P_R = UI \cos \varphi = UI \cos 0^\circ = UI = I^2 R = U^2 / R$

L: $P_L = UI \cos \varphi = UI \cos 90^\circ = 0$

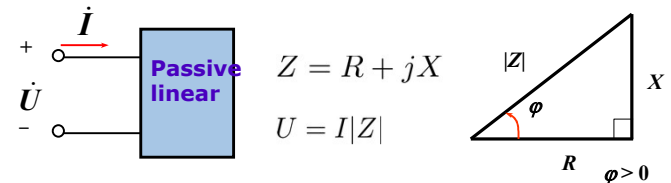C: $P_C = UI \cos \varphi = UI \cos(-90^\circ) = 0$



$$P = UI \cos \varphi = I|Z|I \cos \varphi = I^2|Z| \cos \varphi = I^2 R$$

Average Power is the power absorbed by equivalent resistance.

Active Power

91

$$Z = R + jX$$

$$\begin{cases} \cos\varphi = 1, X=0 \\ \cos\varphi = 0, R=0 \end{cases}$$

Generally, $0 \leq \cos\varphi \leq 1$

$X > 0, \varphi > 0$, inductive, (current) lagging power-factor;

$X < 0, \varphi < 0$, capacitive, (current) leading power-factor;

$\cos\varphi = 0.5$ (滞后), $\varphi = 60^\circ$;

$\cos\varphi = 0.5$ (超前), $\varphi = -60^\circ$;

92

Example 1 $u(t) = 707\cos 10\omega t(V)$, $i(t) = 1.41\cos(\omega t - 53.1^\circ)$

Find P


Solution 1: $P = UI \cos\varphi = \frac{707}{\sqrt{2}} \times \frac{1.41}{\sqrt{2}} \cos 53.1^\circ = 300 W$

Solution 2:

$$\dot{I} = 1\angle -53.1^\circ \quad \dot{U} = 500\angle 0^\circ V$$

$$Z = \frac{\dot{U}}{\dot{I}} = 500\angle 53.1^\circ = 300 + j400 \Omega$$


$$P = I^2 R = 1 \times 300 = 300 W$$

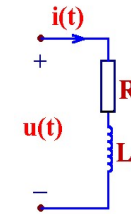

93

Example 2 $f = 50\text{Hz}$, Find P

1)

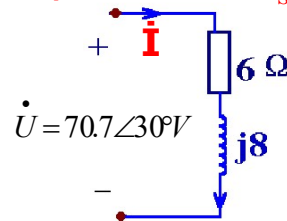

Solution :

$$\dot{I} = \frac{\dot{U}}{Z} = \frac{70.7\angle 30^\circ}{6 + j8} = \frac{70.7\angle 30^\circ}{10\angle 53.1^\circ} = 7.07\angle -23.1^\circ$$

$$P = UI \cos\varphi = 300 W$$


or

$$P = PR = I^2 R = 300 W$$

$$\cos\varphi = \cos(53.1^\circ) = 0.6$$

94


2) Find P .

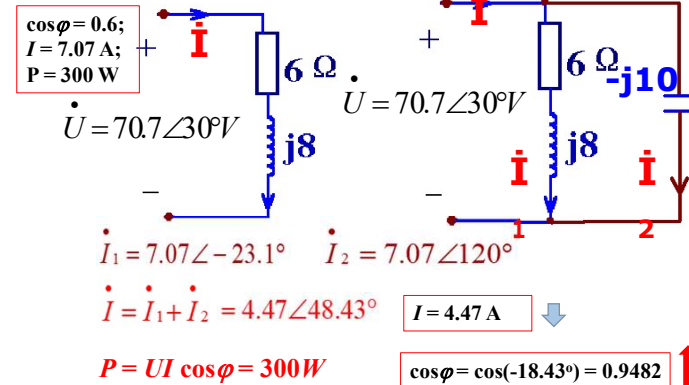

95

Example 3 $f = 50\text{Hz}$, $U = 50\text{V}$, $I = 1\text{A}$, $P = 3\text{W}$

Find R , L .

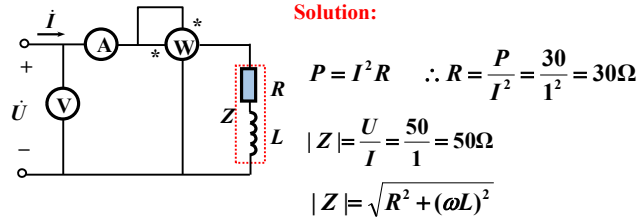


$$L = \frac{1}{\omega} \sqrt{|Z|^2 - R^2} = \frac{1}{314} \sqrt{50^2 - 30^2} = \frac{40}{314} = 0.127\text{H}$$

96

3. Maximum power transfer

Impedance load

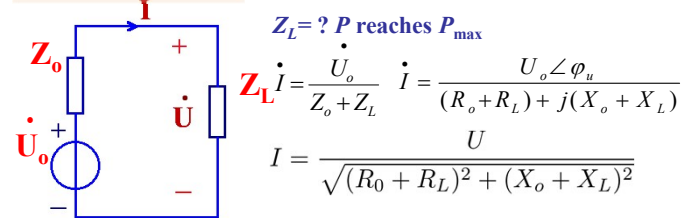

$$P = I^2 R_L = \frac{R_L U^2}{(R_o + R_L)^2 + (X_o + X_L)^2} \quad X_L = -X_o$$


$$\frac{d}{dR_L} \left[\frac{R_L}{(R_o + R_L)^2} \right] = 0 \quad \frac{R_o - R_L}{(R_o + R_L)^3} = 0 \quad R_L = R_o$$

$$\therefore Z_L = R_o - jX_o = Z_o^* \quad P_{\max} = \frac{U_o^2}{4R_o}$$

97

3. Maximum power transfer

Resistive load

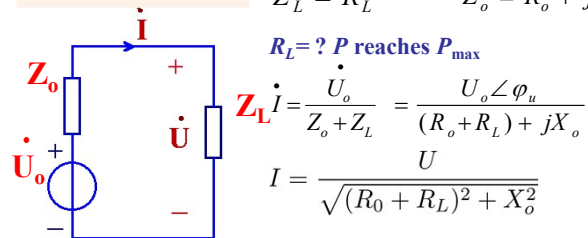


$$P = I^2 R_L = \frac{R_L U^2}{(R_o + R_L)^2 + X_o^2}$$

$$R_L = \sqrt{R_o^2 + X_o^2} = |Z_o| \quad P_m = \frac{U_o^2 |Z_o|}{(R_o + |Z_o|)^2 + X_o^2}$$

98

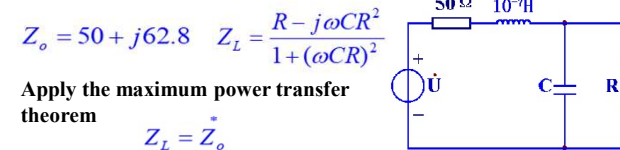Example. $\dot{U} = 0.1 \angle 0^\circ \text{V}$, $f = 100\text{MHz}$.

Find 1) What are the values of R and C if it is known that R is absorbing maximum power P_{\max} ?



$$\text{So } \frac{R}{1 + (\omega CR)^2} = 50 \quad \frac{\omega CR^2}{1 + (\omega CR)^2} = 62.8$$

$$\omega CR = 1.256 \quad \therefore R = 128.8768\Omega$$

$$C = 15.5\text{pF} \quad P_m = \frac{U^2}{4R_o} = 50\mu\text{W}$$

99


Example . $\dot{U} = 0.1\angle 0^\circ V, f = 100\text{MHz}.$

Find 2) Remove C , What is the value of R to absorb the maximum power?

$$Z_o = 50 + j62.8$$


$$R = |Z_o| = 80.2735\Omega$$

$$P_m = \frac{U_o^2 |Z_o|}{(R_o + |Z_o|)^2 + X_o^2} = 38.38\mu W$$

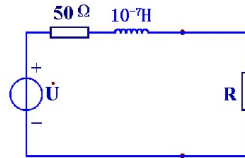

100

9.9.3 Reactive Power (无功功率)

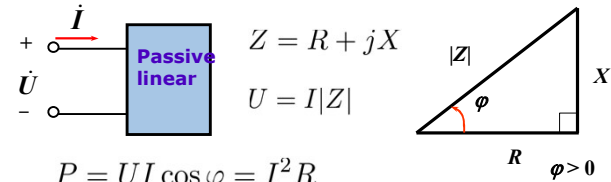

$$P = UI \cos \varphi = I^2 R$$

Define

$$Q = UI \sin \varphi = I|Z|I \sin \varphi = I^2|Z| \sin \varphi = I^2 X$$

$$\text{R: } Q_R = UI \sin 0^\circ = 0$$

Unit: Var

$$\text{L: } Q_L = UI \sin 90^\circ = UI = U^2 / X_L = X_L I^2 > 0, \text{ absorbed reactive power}$$

$$\text{C: } Q_C = UI \sin 90^\circ = UI = U^2 / X_C = X_C I^2 < 0, \text{ developed reactive power}$$

Time rate of energy flow back and forth between the source and the reactive loads. Compensation between capacitor and inductor.

101

9.9.4 Complex Power (复功率)

Define 共轭复数

$$\tilde{S} = \dot{U} \dot{I}^*$$

$$\tilde{S} = U \angle \varphi_u I \angle -\varphi_i = UI \angle \varphi_u - \varphi_i$$

$$= UI \cos(\varphi_u - \varphi_i) + jUI \sin(\varphi_u - \varphi_i) \quad \varphi = \psi_u - \psi_i$$

$$= UI \cos \varphi + jUI \sin \varphi$$

$$= P + jQ \quad \text{Unit: VA}$$

The complex sum of active power and reactive power

102


9.9.5 Power Factor (功率因数) and Apparent Power (视在功率)

Power Factor Angle $\varphi = \varphi_u - \varphi_i$

Power Factor $\cos \varphi$

Leading Power Factor: current leads voltage (capacitive load)

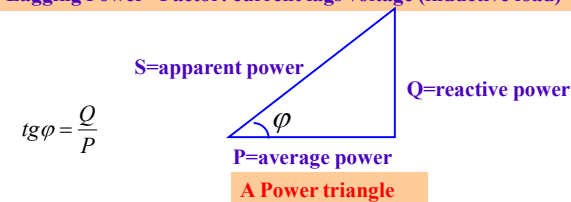Lagging Power Factor: current lags voltage (inductive load)



Apparent Power: $S = \sqrt{P^2 + Q^2} = UI$ **Unit: VA**

Apparent power represent the volt-amps capacity required to supply the average power.

103