


# 1-4 *Circuit Elements*

- A element is the basic building block of a circuit.
- An electric circuit is simply an interconnection of the elements.
- Circuit analysis is the process of determining voltages across (or the currents through) the elements of the circuit.
- There are two types of elements found in electric circuits:
  - ✓ Passive elements: An passive element is not capable of generating energy. Example passive element are resistors, capacitors, and inductors.
  - ✓ Active elements: An active element is capable of generating energy. Type active element include generators, batteries, and operational amplifiers.

# Lumped parameter element:

Electromagnetic process generate inside element

**Lumped Condition:**

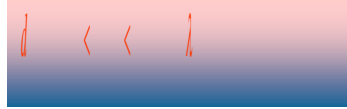

**For example:**

- For work frequency:  $f = 50\text{Hz}$ :  $\lambda = vT = \frac{v}{f} = \frac{3 \times 10^8}{50} = 6000\text{km}$
- For audio frequency:  $f = 25 \text{ kHz}$ :  $\lambda = \frac{v}{f} = \frac{3 \times 10^8}{25 \times 10^3} = 12\text{km}$

Lumped parameter circuit: It consists of lumped element

**Notice:**

*In lumped parameter circuit,  $u$ 、 $i$  is function of time, but it is independent of space coordinate*

## An ideal basic circuit element has three attributes:

- ✓ It has **only two terminals**, which are points of connection to other circuit components;
- ✓ It is described mathematically **in terms of current and/or voltage**;
- ✓ It **cannot be subdivided into** other elements.

### *Note that:*

- ✓ We use the word **ideal** to imply that a basic circuit element does not exist as a realizable physical component.
- ✓ We use the word **basic** to imply that the circuit element cannot be further reduced or subdivided into other elements.
- ✓ Thus the basic circuit elements form the building blocks for constructing circuit models, but *they themselves cannot be modeled with any other type of element.*

- There are five ideal basic circuit elements:

- ✓ voltage sources

- ✓ current sources

- ✓ resistors,

- inductors

- capacitors.

- Although this may seem like a small number of elements with which to begin analyzing circuits, many practical systems can be modeled with just sources and resistors. They are also a useful starting point because of their relative simplicity: *the mathematical relationships* between voltage and current in sources and resistors *are algebraic*.

- Thus you will be able to begin learning the basic techniques of circuit analysis with only algebraic manipulations.


- In this section we discuss their characteristics.

# 1-5 Resistance



## ● Resistance

A element which *dissipates energy* but stores none is said to consist solely of resistance.

$$f(u, i) = 0$$

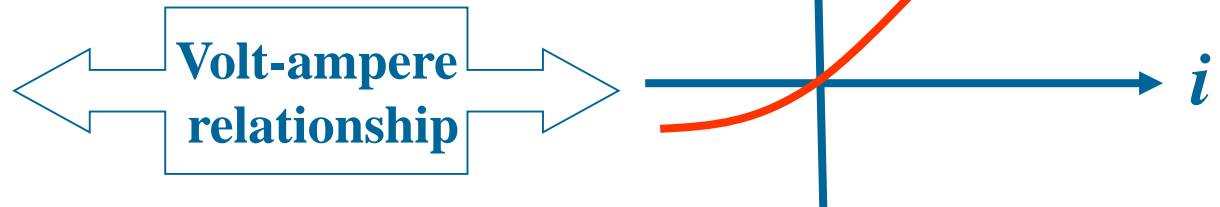

## ● Symbol for resistance

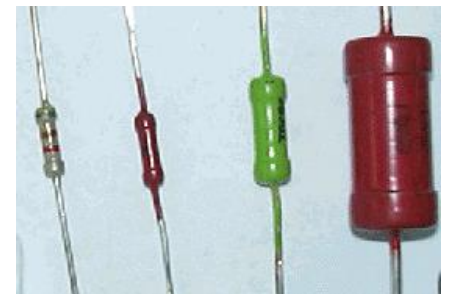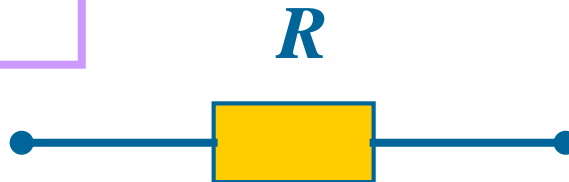

# ● Practical Resistors

## 金属膜电阻器

Metal Film Fixed Resistor (MF TYPE)



## 金属氧化物电阻器

Metal Oxide Film Resistor (MOF TYPE)



## 碳膜电阻器

Carbon Film Fixed Resistor



## 熔断涂覆电阻器

Fusible Film Resistor



## 线绕涂覆电阻器

Wire Wound Resistor (KNP TYPE)



## 绕涂覆电阻器

Wire Wound Resistor (KNH TYPE)



●  $u \sim i$  relations




Ohm's Law

$$u = R i$$


$$R = u / i$$

$$i = u / R = G u$$

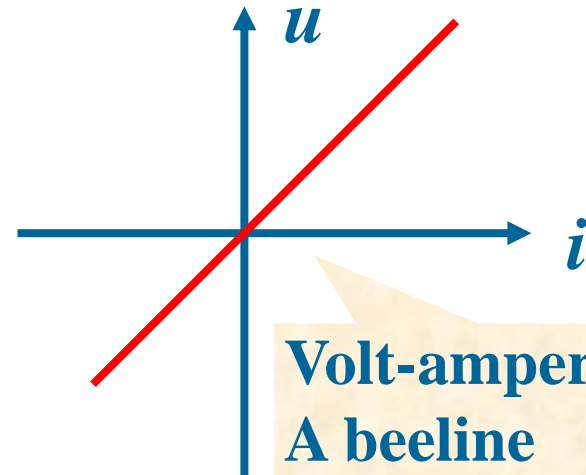$u$ 、 $i$  : Associate  
reference direction



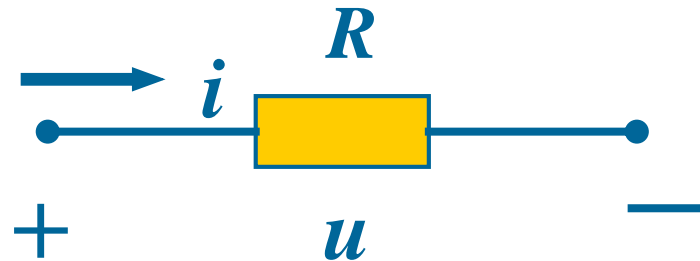Volt-ampere :  
A beeline  
through origin



● in S.I. units


$R$ --Resistance :  $\Omega$  (欧) (Ohm, 欧姆)

$G$ —conductance: S(西门子) (Siemens, 西门子)

**Notice:**

Ohm's Law

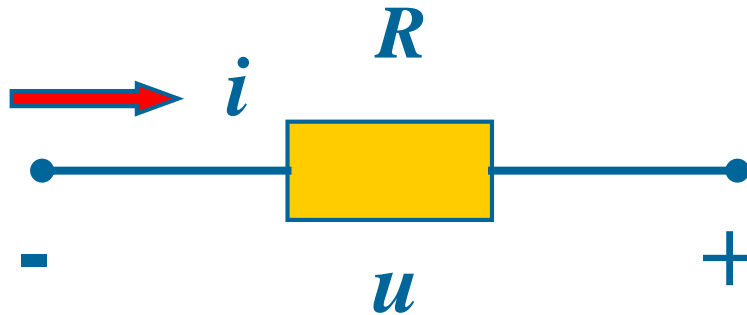- (1) Be the same with linearity resistance
- (2) Imply linearity resistance is nonmemory
- (3) In non-Associate reference direction




The expression for Ohm's Law is


$$u = -R i \quad i = -G u$$



## ● Power of Resistance

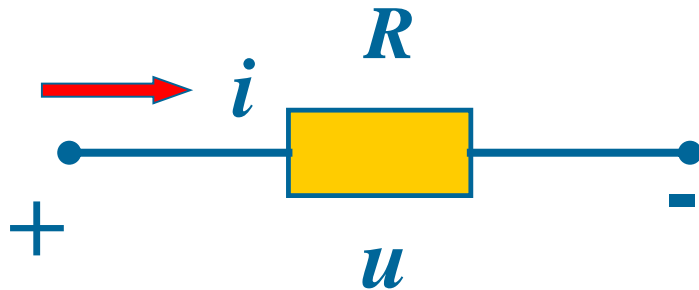

$$p = u i = i^2 R = u^2 / R$$

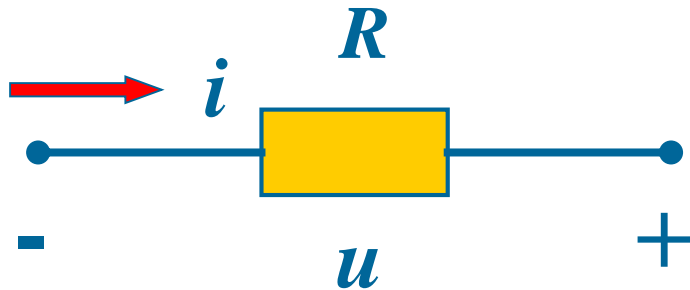

$$\begin{aligned} p &= -u i = -(-R i) i = i^2 R \\ &= -u(-u/R) = u^2 / R \end{aligned}$$

*Resistor dissipate energy*

## ● Energy of Resistance


The energy absorbed by resistor from time  $t$  to time  $t_0$  is :

$$W_R = \int_{t_0}^t p \, d\xi = \int_{t_0}^t u i \, d\xi$$

Energy is the capacity to do work, measured in joules (J)


## ● *Open circuit and short circuit*

### ✓ short circuit

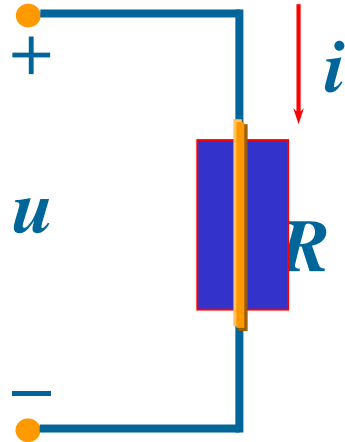


$$i \neq 0 \quad u = 0$$
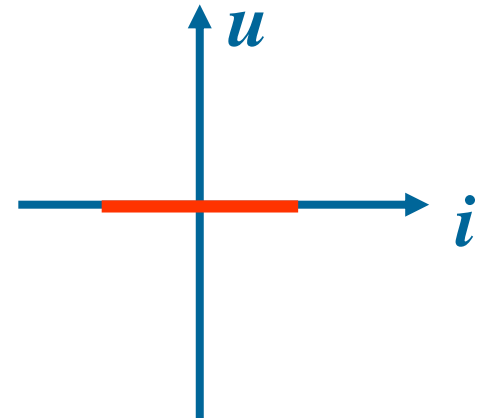
$$R = 0 \quad \text{or} \quad G = \infty$$






### ● Open circuit

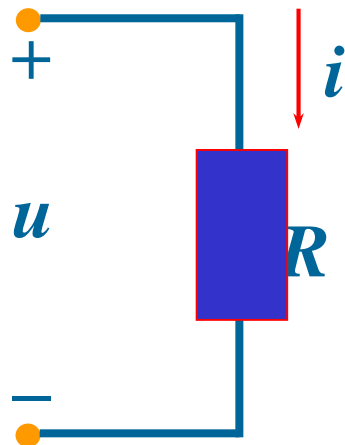

$$i = 0 \quad u \neq 0$$

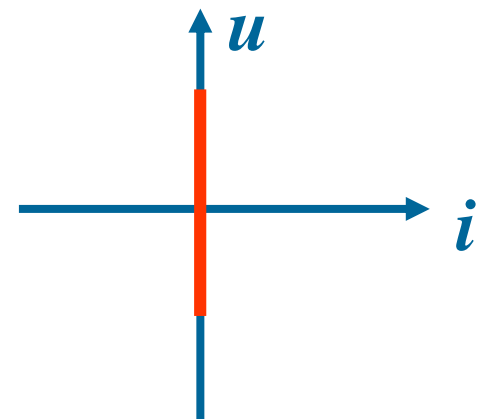
$$R = \infty \quad \text{or} \quad G = 0$$



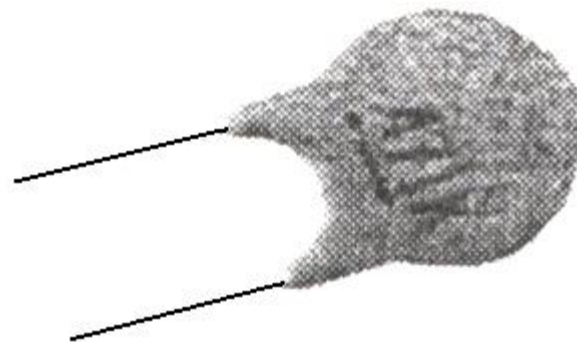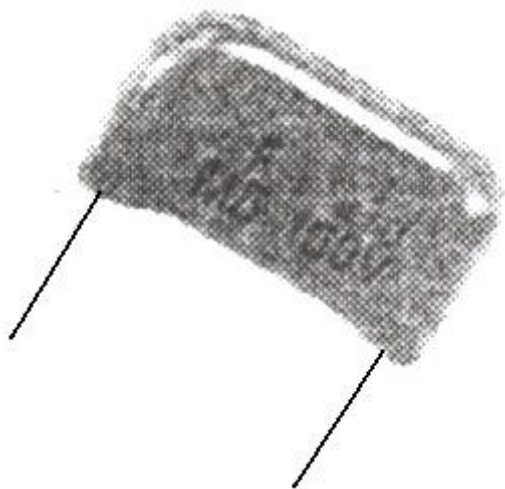

**A capacitor consists of two  
conducting plates separated  
by an insulator(or dielectric).**


**Circuit symbol**

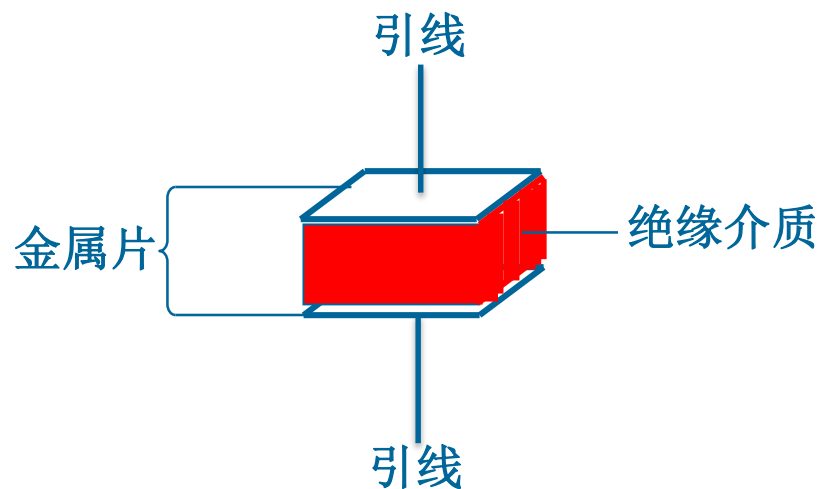
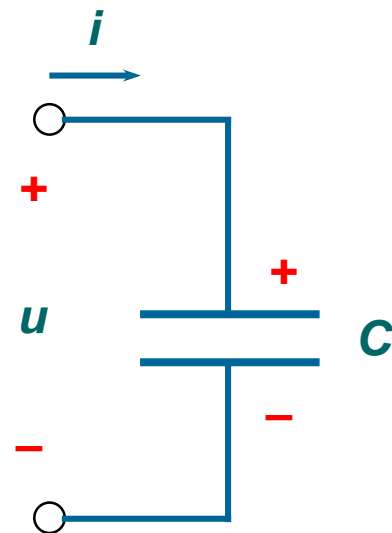
## 6.1、电容器 CAPACITORS


A capacitor is a passive element designed to store energy in its electric field.

Capacitors are widely used in the tuning circuits of radio receivers and as dynamic memory elements in computer systems.



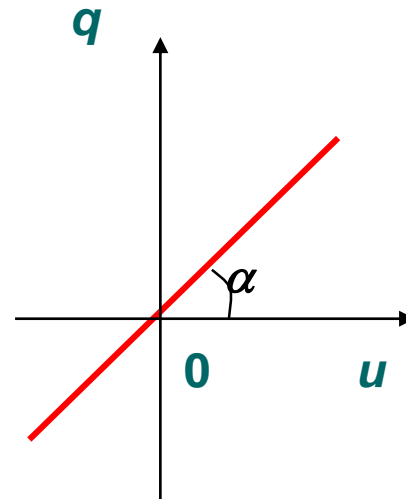**1. Circuit theory definition: a two\_terminal element will be called a capacitor if at any time t, its charge  $q(t)$  and its voltage  $v(t)$  satisfy a relation defined by a curve in the  $q\_v$  Plane.**



$$C \stackrel{\text{def}}{=} \frac{q}{u}$$



**Capacitance: is the ratio of the charge on one plate of a capacitor to the voltage difference between the two plates, measured in farads(F).**


$$F = C/V = A \cdot s / V = s / \Omega$$

Nonlinear capacitor:

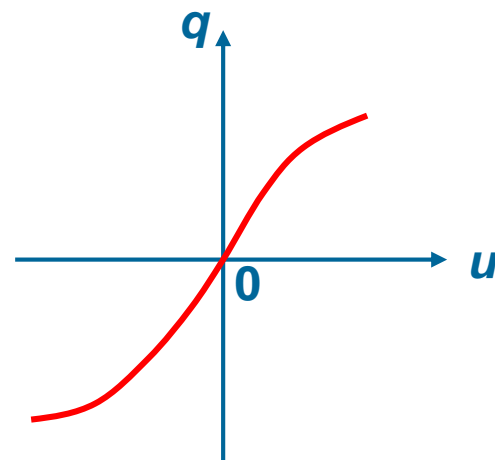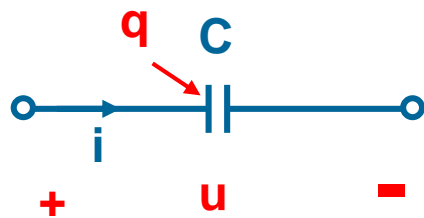


To the linear capacitor:

$$q = Cu$$

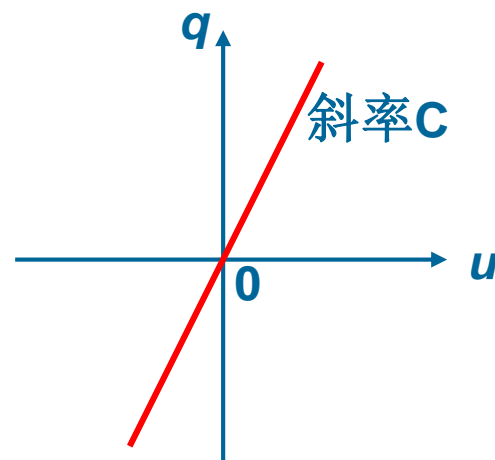
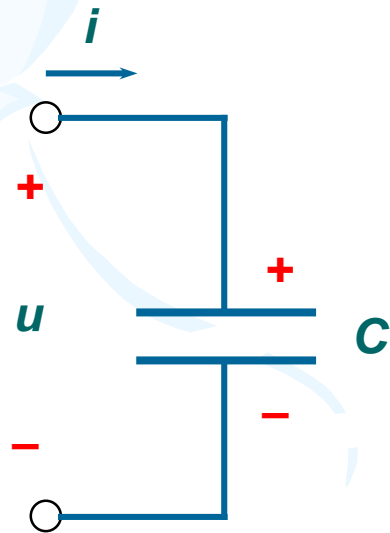
## 2. U-I relationship of the linear capacitor:



$$i = \frac{dq}{dt} = C \frac{du}{dt}$$

$$u(t) = \frac{1}{C} \int_{-\infty}^t i d\xi = u(t_0) + \frac{1}{C} \int_{t_0}^t i d\xi$$


$$q(t) = q(t_0) + \int_{t_0}^t i d\xi$$





$$i(t) = C \frac{du(t)}{dt}$$
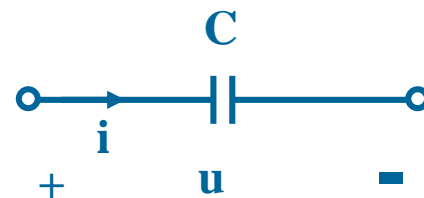
$$u(t) = u(0) + \frac{1}{C} \int_0^t i(\xi) d\xi$$




### 3、Character

#### (1) dynamic character

#### Isolate DC

(如放大器电路中电容的耦合作用)

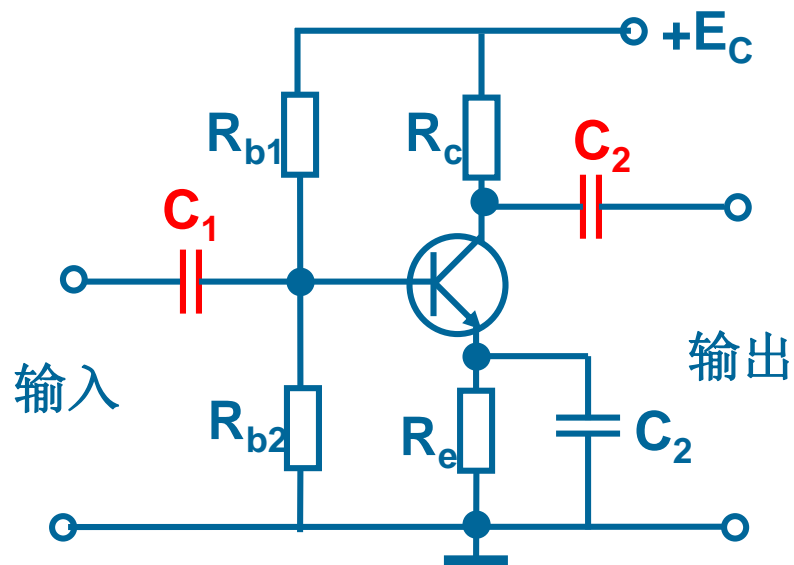

$$i(t) = C \frac{du(t)}{dt}$$

(2) memory

$$0 \leq t \leq 1$$

$$u(t) = u(0) + 5 \times 10^5 \int_0^t 10^{-6} d\xi = 0.5t$$

$$u(1) = 0.5V$$

$$1 \leq t \leq 2$$

$$u(t) = u(1) + 5 \times 10^5 \int_0^t 0 d\xi = 0.5V$$



$$2 \leq t \leq 3$$

$$u(t) = u(2) + 5 \times 10^5 \int_2^t 10^{-6} d\xi = 0.5 + 0.5(t-2)$$

$$u(3) = 1V$$

$$u(t) = u(0) + \frac{1}{C} \int_0^t i(\xi) d\xi$$

Example: a timer

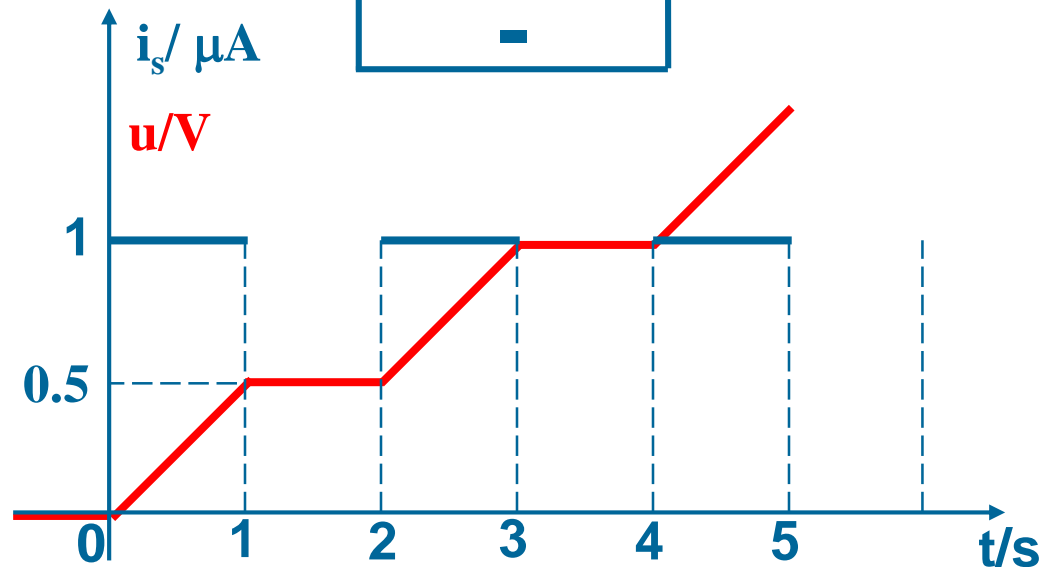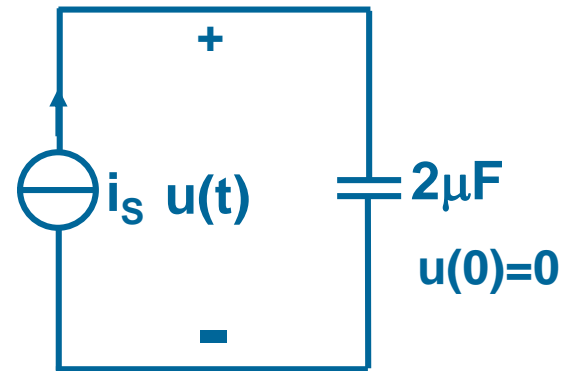

$$i(t) = C \frac{du(t)}{dt}$$


$$u(t) = u(0) + \frac{1}{C} \int_0^t i(\xi) d\xi$$

(3) the voltage across a capacitor is continuous.

$i(t)$  is bounded

如果 $i(t)$ 在任一时间都有界，则 $u(t)$ 在任一时间的变化都是连续的。即在任一时间，电容电压都不可能即时地从一个值跃变到另一个值。


特别，如果在 $t=0$ 时有界，

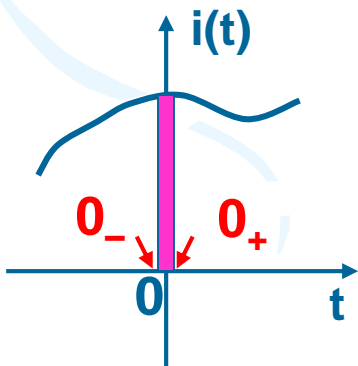


$$\text{则 } u(0_+) = u(0_-) + \frac{1}{C} \int_{0_-}^{0_+} i(t) dt$$


$$u(0_+) = u(0_-)$$
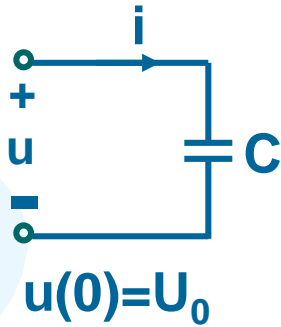
#### (4) The capacitor with initial voltage


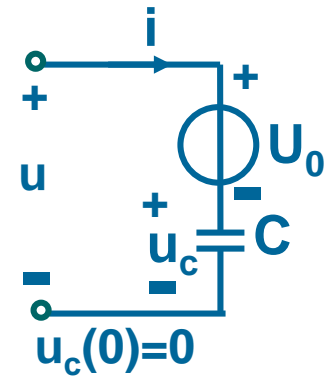
$$u(t) = U_0 + \frac{1}{C} \int_0^t i(\xi) d\xi$$



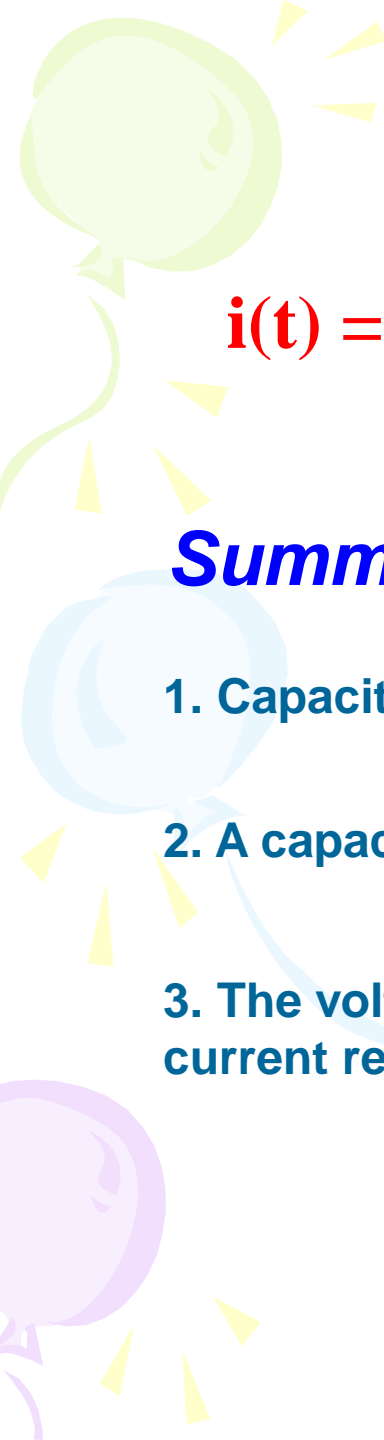
$$i(t) = C \frac{du(t)}{dt}$$

$$u(t) = u(0) + \frac{1}{C} \int_0^t i(\xi) d\xi$$

## ***Summary:***

1. Capacitors have memory.
2. A capacitor is an open circuit to dc.
3. The voltage on a capacitor cannot change abruptly as long as the current remains bounded.






The instantaneous power delivered to the capacitor is:

$$p = vi = cv \frac{dv}{dt}$$

The energy stored in the capacitor is:

$$w = \int_{-\infty}^t p dt = c \int_{-\infty}^t v \frac{dv}{dt} dt = c \int_{-\infty}^t v dv = \frac{1}{2} cv(t)^2 \Big|_{t=-\infty}^t$$

## 6. 2 series capacitors

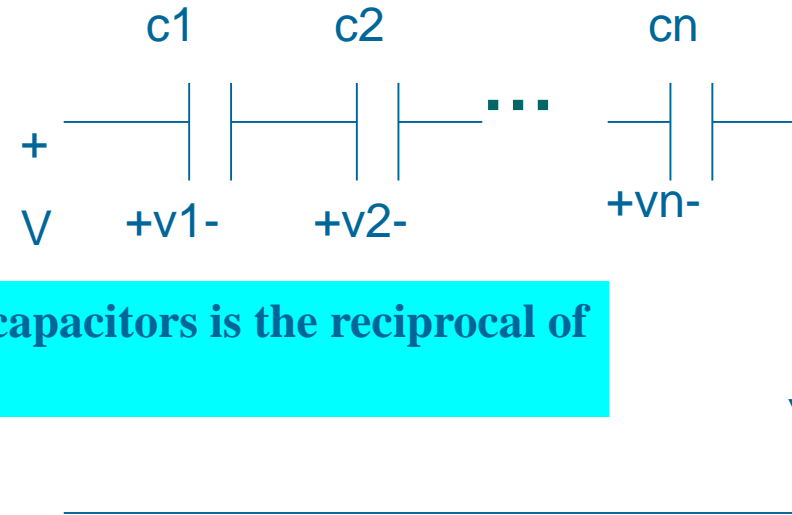

The equivalent capacitance of  $n$  series-connected capacitors is the reciprocal of the sum of the individual capacitances.

$$V = v_1 + v_2 + \dots + v_n$$


$$v = \frac{1}{c_1} \int_{t_0}^t i(t) dt + v_1(t_0) + \frac{1}{c_2} \int_{t_0}^t i(t) dt + v_2(t_0) + \dots + \frac{1}{c_n} \int_{t_0}^t i(t) dt + v_n(t_0)$$

$$= \left( \frac{1}{c_1} + \frac{1}{c_2} + \dots + \frac{1}{c_n} \right) \int_{t_0}^t i(t) dt + v_1(t_0) + v_2(t_0) + \dots + v_n(t_0)$$

$$= \frac{1}{c_{eq}} \int_{t_0}^t i(t) dt + v(t_0)$$

$$\frac{1}{c_{eq}} = \frac{1}{c_1} + \frac{1}{c_2} + \dots + \frac{1}{c_n}$$

## 6. 3 parallel capacitors

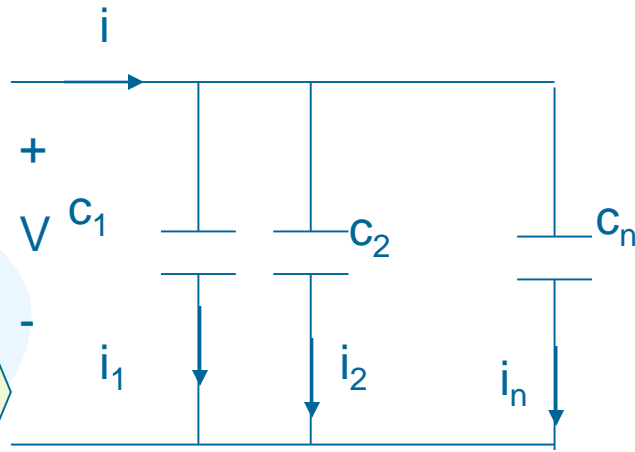

$$i = i_1 + i_2 + i_3 + \dots + i_n$$

$$i = c_1 \frac{dv}{dt} + c_2 \frac{dv}{dt} + \dots + c_n \frac{dv}{dt}$$

$$= \left( \sum_{k=1}^n c_k \right) \frac{dv}{dt} = c_{eq} \frac{dv}{dt}$$

$C_{eq}$

$$\therefore C_{eq} = C_1 + C_2 + \dots + C_n$$


The equivalent capacitance of  $n$  parallel-connected capacitors is the sum of the individual capacitances.



## Discussion: Parallel capacitors with initial voltages:

情况一 并联前各电容电压相同

情况二 并联前各电容电压不同

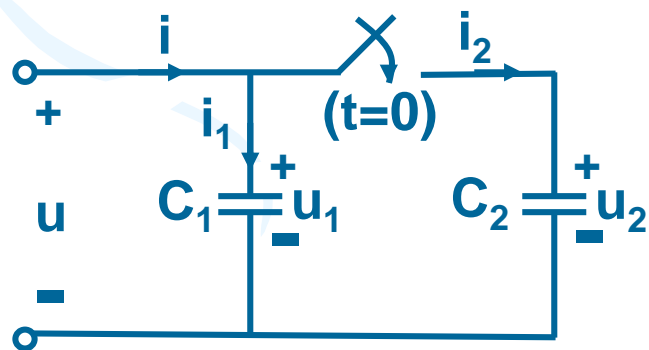


$$u_1(0_-) \neq u_2(0_-)$$

$$u_1(0_+) = u_2(0_+) = u(0_+)$$

$$i(t) = C \frac{du(t)}{dt}$$

$$u(t) = u(0) + \frac{1}{C} \int_0^t i(\xi) d\xi$$

Conservation of the charge:

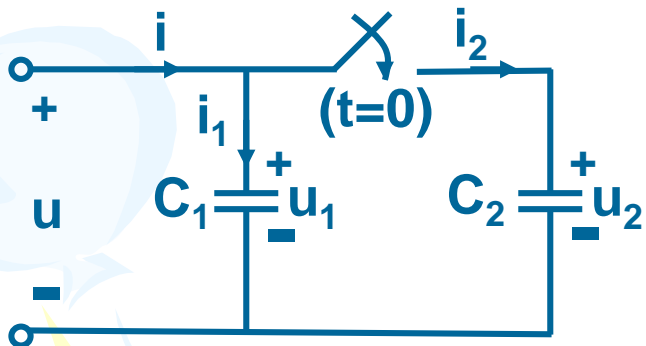


$$\sum_{k=1}^m q_k(0_+) = \sum_{k=1}^m q_k(0_-)$$

$$(C_1 + C_2)u(0_+) = C_1 u_1(0_-) + C_2 u_2(0_-)$$


When the switch is closed, some charge is dumped from one capacitor to another instantaneously, this implies that an impulse of current flows from one capacitor to another.

## Nonlinear, time-varying capacitors:

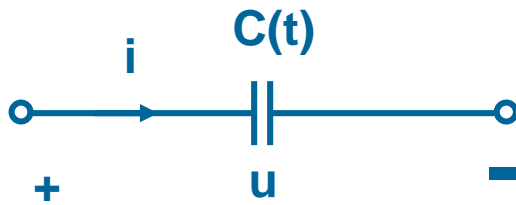



$$q = C(t)u$$
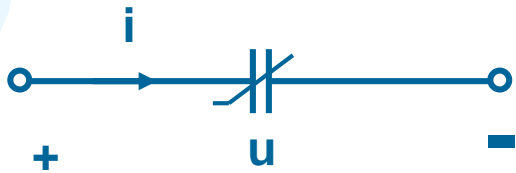
$$i = \frac{dq}{dt} = C(t) \frac{du}{dt} + u \frac{dC(t)}{dt}$$




$$q = f(u)$$
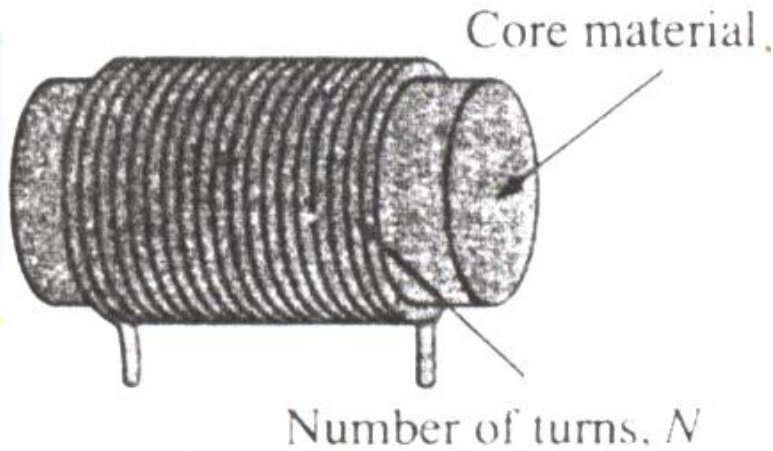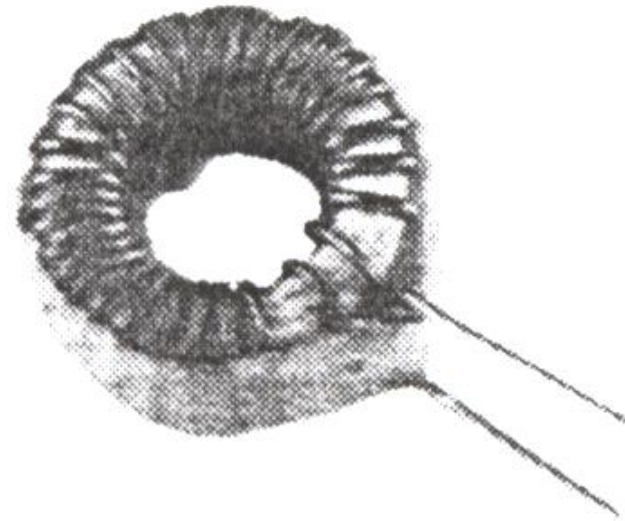
$$i = \frac{dq}{dt} = \frac{df(u)}{du} \frac{du}{dt}$$



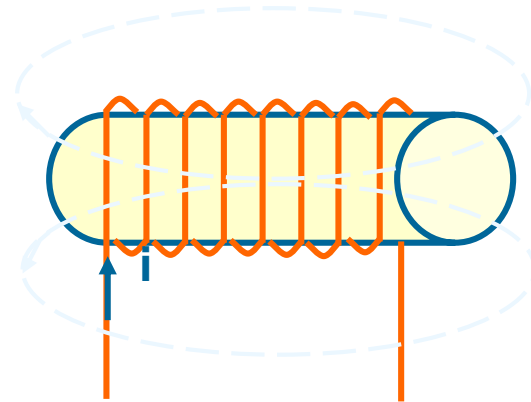**An practical inductor is usually formed into a cylindrical coil with many turns of conducting wires.**





**An inductor is a passive element designed to store energy in its magnetic field.**


**Inductors are widely used in power supplies, transformers, radios, TVs, radars, and electric motors.**

**The element called an inductor is an idealization of the physical inductors.**

## 6.4 INDUCTOR


**1. Circuit theory definition: a two-terminal element will be called an inductor if at any time  $t$ , its flux  $\Psi(t)$  and its current  $I(t)$  satisfy a relation defined by a curve in the  $\Psi$ - $I$  Plane.**

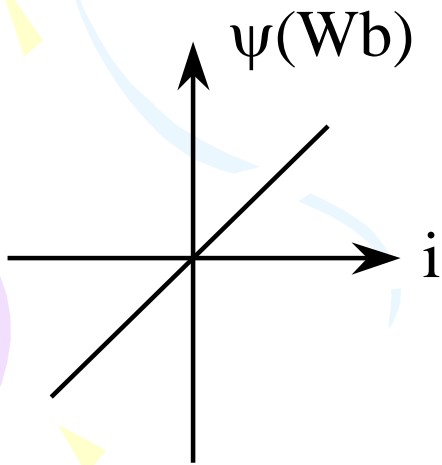**2 Characteristics of the linear time-invariant inductors**



$$\Psi(t) = Li(t)$$

## (1). Linear inductor

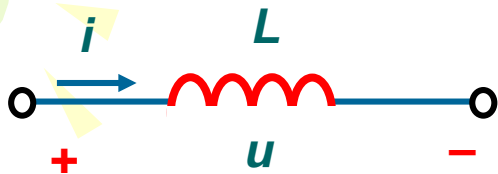

Joseph Henry (1797-1878),

$$L \stackrel{\text{def}}{=} \frac{\psi}{i}$$


$\psi = N \phi$  *flux*(电感线圈的磁链)

$L$  *inductance*(自感系数)

*unit:* H (Henry) 亨(利)

## (2). VCR of the linear inductors :

Faraday's induction law:

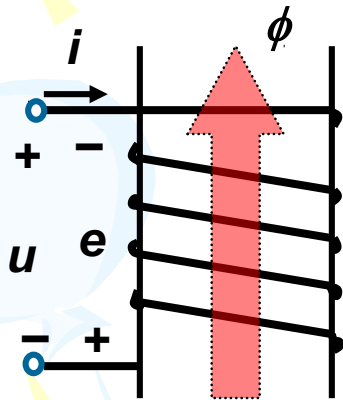

$$u(t) = \frac{d\psi}{dt}$$

$$= L \frac{di(t)}{dt}$$



## (2)、VCR

$$u(t) = \frac{d\psi}{dt} = L \frac{di(t)}{dt}$$

$$i(t) = i(0) + \frac{1}{L} \int_0^t u(\xi) d\xi$$

## (3)、characters

\*dynamic

\*memory

\* the current is continuous as long as the voltage is bounded.



$u(t) = L \frac{di(t)}{dt}$


$$i(t) = i(0) + \frac{1}{L} \int_0^t u(\xi) d\xi$$

(3) the current through an inductor is continuous

$u(t)$  is bounded


Specially, if  $u(t)$  is bounded at  $t=0$ ,

$$i(0_+) = i(0_-)$$



$$u(t) = L \frac{di(t)}{dt}$$

$$i(t) = i(0) + \frac{1}{L} \int_0^t u(\xi) d\xi$$
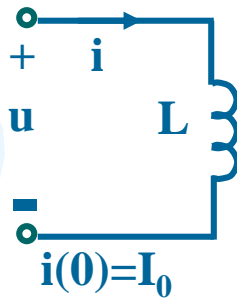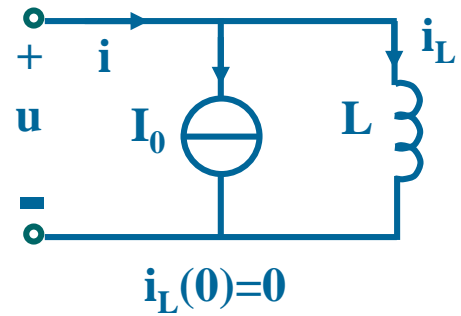
#### (4) An inductor with initial current



$$i(t) = i(0) + \frac{1}{L} \int_0^t u(\xi) d\xi$$






**The instantaneous power delivered to the inductor is:**

$$p = vi = L \frac{di}{dt} i$$

**The energy stored in the capacitor is:**

$$w = \int_{-\infty}^t p dt = L \int_{-\infty}^t i \frac{di}{dt} dt = L \int_{-\infty}^t i di = \frac{1}{2} Li(t)^2 \Big|_{t=-\infty}^t$$

## SUMMARY:

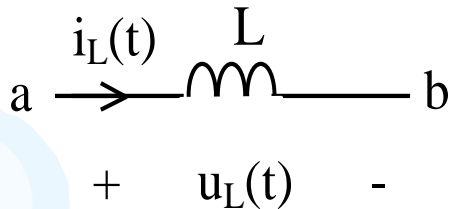

$$u_L(t) = L \frac{di_L(t)}{dt}$$


$$i = \frac{1}{L} \int_{-\infty}^t v(t) dt = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

**Remark: 1). Inductors have memory.**

**2). The inductors look like a short circuit to dc.**

**3) The current in an inductor cannot change abruptly as long as the voltage across it remains bounded.**

## 6.5 parallel inductors

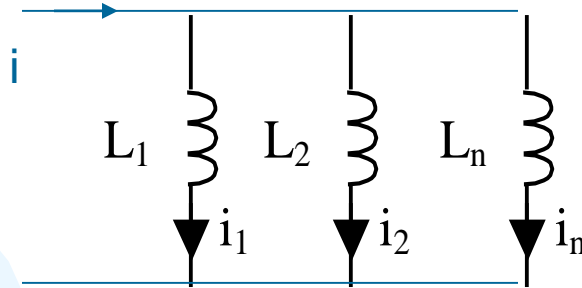

The equivalent inductance of  $n$  parallel-connected inductors is the sum of the reciprocals of the individual inductances.

$$i = i_1 + i_2 + i_3 + \dots + i_n$$


$$i = \frac{1}{L_1} \int_{t_0}^t v(t) dt + i_1(t_0) + \frac{1}{L_2} \int_{t_0}^t v(t) dt + i_2(t_0) + \dots + \frac{1}{L_n} \int_{t_0}^t v(t) dt + i_n(t_0)$$

$$= \left( \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right) \int_{t_0}^t v(t) dt + i_1(t_0) + i_2(t_0) + \dots + i_n(t_0)$$

$$= \frac{1}{L_{eq}} \int_{t_0}^t i(t) dt + i(t_0)$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

## 6.6 Series Inductors

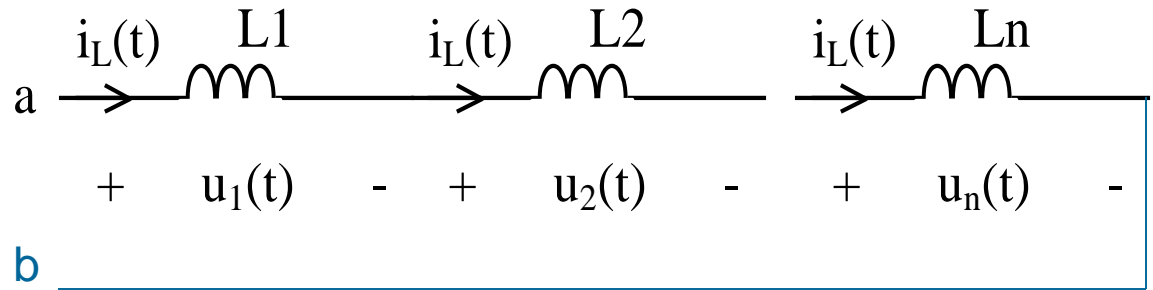

The equivalent inductance of  $n$  series-connected inductors is the sum of the individual inductances.


$$v = L_1 \frac{di_L}{dt} + L_2 \frac{di_L}{dt} + \cdots + L_n \frac{di_L}{dt}$$
$$= \left( \sum_{k=1}^n L_k \right) \frac{di_L}{dt} = L_{eq} \frac{di_L}{dt}$$

$$\therefore L_{eq} = L_1 + L_2 + \cdots + L_n$$

# A DISSCUSSION : SERIES INDUCTORS WITH INITIAL CURRENTS:

Case 1: inductors carry the same initial current

Case 2 : initial currents are not equal.

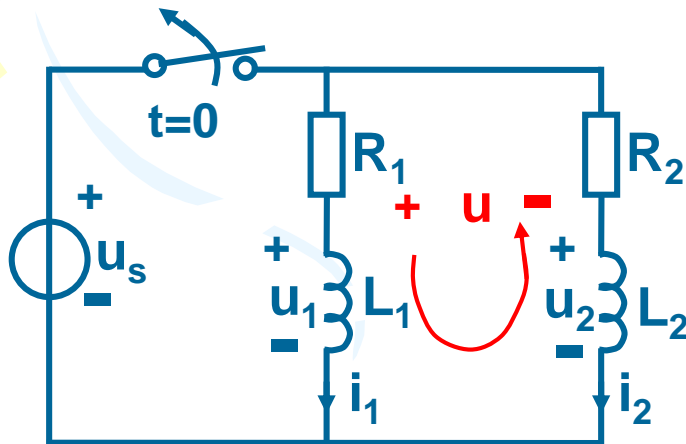

$$i_1(0_-) \neq i_2(0_-)$$

$$i_1(0_+) = -i_2(0_+)$$




## Conservation of flux:

irrespective of the manner in which the connection is made for the  $m$  inductors, the total flux remains fixed.

$$\sum_{k=1}^m \psi_k(0_+) = \sum_{k=1}^m \psi_k(0_-)$$



( $m$ 为回路包含电感元件的总数)

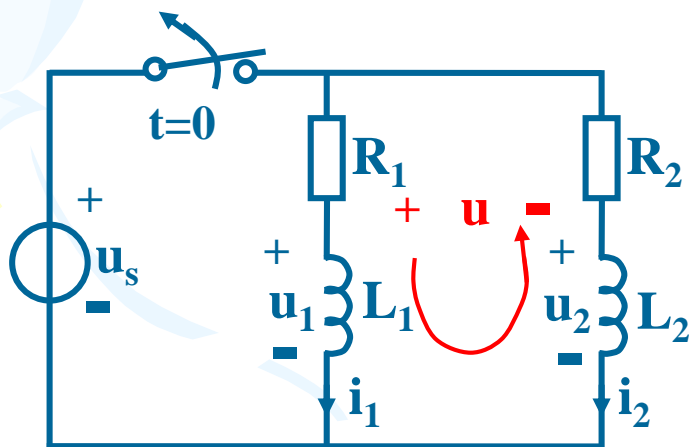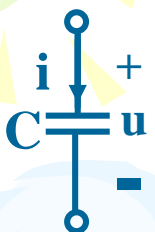


$$L_1 i_1(0_+) - L_2 i_2(0_+) = L_1 i_1(0_-) - L_2 i_2(0_-)$$

$$(L_1 + L_2) i_1(0_+) = L_1 i_1(0_-) - L_2 i_2(0_-)$$

# Comparisons between L,C

元件	约束方程	电压-电流关系		连续性	储存的能量
	$q=C u$	$i(t)=C \frac{du(t)}{dt}$	$u(t)=u(0)+\frac{1}{C} \int_0^t i(\xi) d \xi$	电压	$\varepsilon(t)=0.5 C u^2(t)$
	$\psi=L i$	$u(t)=L \frac{di(t)}{dt}$	$i(t)=i(0)+\frac{1}{L} \int_0^t u(\xi) d \xi$	电流	$\varepsilon(t)=0.5 L i^2(t)$


**A real, nonideal capacitor:**

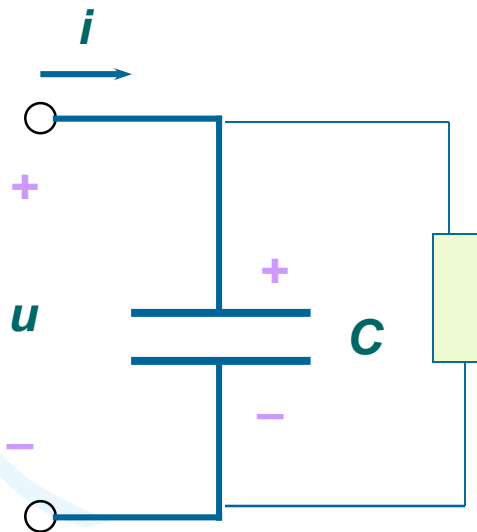

*Leakage resistance*

**Leakage resistance may be as high as 100M $\Omega$ .**

**A real, nonideal inductor:**

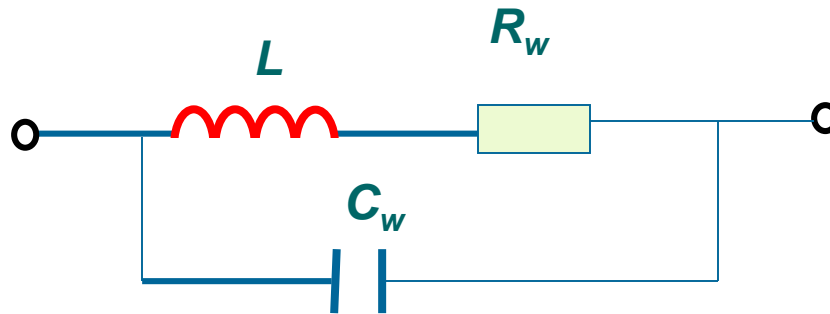

**Winding resistance  $R_w$  is usually very small**

**Winding capacitance  $C_w$  is usually very small except at high frequencies.**