

## 9.4 Kirchhoff's Laws in the Frequency Domain (频域中的基尔霍夫定律)

### 9.4.1 KCL

time domain

$$\sum_{k=1}^n i_k(t) = 0$$

$$\sum_{k=1}^n \operatorname{Re}\{\dot{I}_{km} e^{j\omega t}\} = 0$$

frequency domain

$$\sum_{k=1}^n \dot{I}_{km} = 0 \quad \sum_{k=1}^n \dot{I}_k = 0$$

\*

**Example 1.**  $i_1(t) = 5\sqrt{2} \cos(\omega t + 53.1^\circ)$   $i_2(t) = 10\sqrt{2} \cos(\omega t - 36.9^\circ)$

Find  $i(t) = i_1(t) + i_2(t)$


Solution:

$$\dot{I}_1 = 5\angle 53.1^\circ = 3 + j4$$

$$\dot{I}_2 = 10\angle -36.9^\circ = 8 - j6$$

$$\dot{I} = \dot{I}_1 + \dot{I}_2 = 11 - j2 = 11.18\angle -10.3^\circ$$
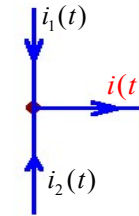
$$\therefore i(t) = 11.18\sqrt{2} \cos(\omega t - 10.3^\circ)$$



\*

### 9.4.2 KVL

time domain

$$\sum_{k=1}^n u_k(t) = 0$$

$$\sum_{k=1}^n \operatorname{Re}\{\dot{U}_{km} e^{j\omega t}\} = 0$$

frequency domain

$$\sum_{k=1}^n \dot{U}_{km} = 0 \quad \sum_{k=1}^n \dot{U}_k = 0$$

Amplitude phasor    Effective value phasor

\*

**Example 2.** In the right circuit,

$$u_1(t) = 6\sqrt{2} \cos(\omega t + 30^\circ)$$

$$u_2(t) = 4\sqrt{2} \cos(\omega t + 60^\circ)$$


Find  $u_3(t)$

$$\text{Solution: } \dot{U}_1 = 6\angle 30^\circ$$

$$\dot{U}_2 = 4\angle 60^\circ$$

$$\begin{aligned} \dot{U}_3 &= \dot{U}_1 - \dot{U}_2 = (5.19 + j3) - (2 + j3.45) \\ &= 3.19 - j0.45 = 3.22\angle -8.03^\circ \end{aligned}$$
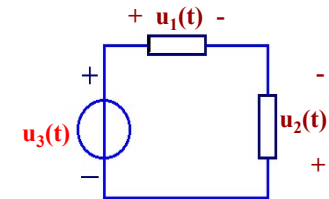
$$\therefore u_3(t) = 3.22\sqrt{2} \cos(\omega t - 8.03^\circ)$$




\*

## 9.5 The Passive Circuit Elements in the Frequency Domain

Establish the relationship between the phasor current and voltage at the terminals of the resistor, inductor, and capacitor.
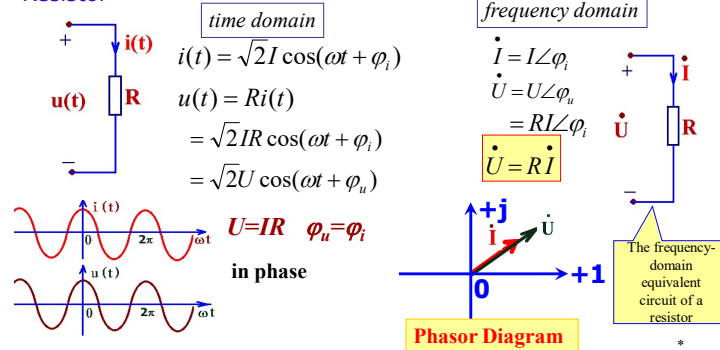
### 9.5.1 The V-I Characteristic for a Resistor



### Instantaneous power(瞬时功率)

$$p(t) = u(t)i(t)$$

$$i(t) = \sqrt{2}I \cos(\omega t + \varphi_i)$$

$$u(t) = \sqrt{2}U \cos(\omega t + \varphi_u)$$


$$p(t) = \sqrt{2}U \cos(\omega t + \varphi) \sqrt{2}I \cos(\omega t + \varphi)$$

$$= UI + UI \cos[2(\omega t + \varphi)] \quad p(t) \geq 0$$


### Average power (平均功率、有功功率)

$$P = \frac{1}{T} \int_0^T p(t) dt = UI$$

$$= RI^2 = \frac{U^2}{R} (W)$$

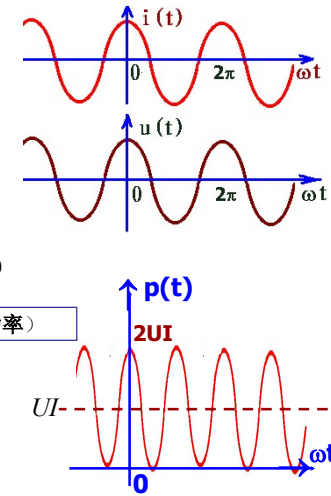
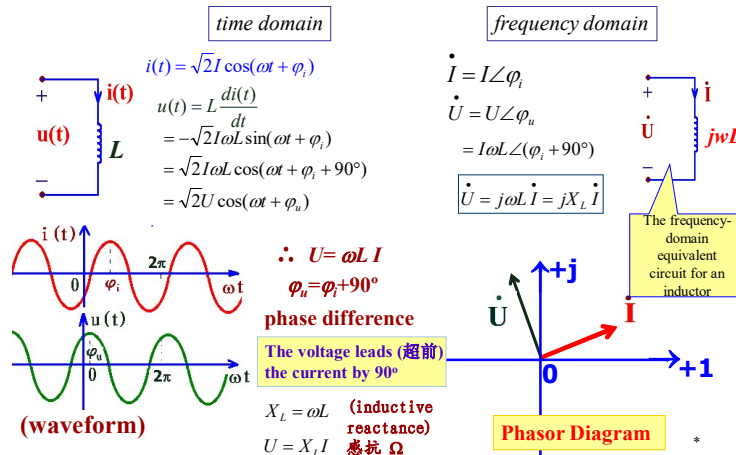
### 9.5.2 The V-I Characteristic for an Inductor



### Instantaneous power

$$p(t) = u(t)i(t)$$

$$i(t) = \sqrt{2}I \cos(\omega t + \varphi_i)$$


$$u(t) = \sqrt{2}U \cos(\omega t + \varphi_u)$$

$$p(t) = \sqrt{2}U \cos(\omega t + \varphi_u) \sqrt{2}I \cos(\omega t + \varphi_i)$$

$$= UI \cos(2\omega t + 2\varphi_i + 90^\circ)$$

### Average power

$$P = \frac{1}{T} \int_0^T p(t) dt = 0$$

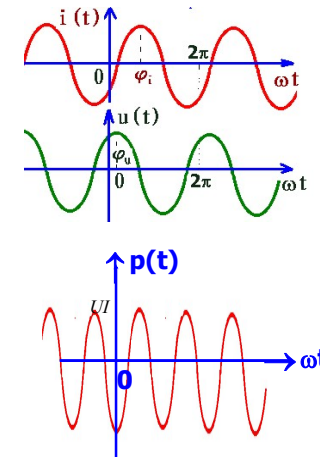

Example 3. In the model of a real inductor,  $R=10\ \Omega$ ,  $L=50\text{ mH}$ ,

$$i(t) = 10\sqrt{2} \cos(314t + 36.9^\circ) \text{ A}$$

Find  $u_R(t)$ ,  $u_L(t)$  and  $u(t)$ .

**Solution**

$$\dot{I} = 10\angle 36.9^\circ \quad \dot{U}_R = \dot{I} R = 100\angle 36.9^\circ = 80 + j60$$


$$\dot{U}_L = jX_L \dot{I} = j\omega L \dot{I} = 157\angle 126.9^\circ = -94.27 + j125.55$$

$$\dot{U} = \dot{U}_R + \dot{U}_L = -14.27 + j185.55 = 186.1\angle 94.4^\circ$$


$$\therefore u(t) = 186.1\sqrt{2} \cos(\omega t + 94.4^\circ) \text{ V}$$

$$u_R(t) = 100\sqrt{2} \cos(\omega t + 36.9^\circ) \text{ V}$$
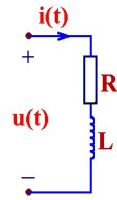
$$u_L(t) = 157\sqrt{2} \cos(\omega t + 126.9^\circ) \text{ V}$$


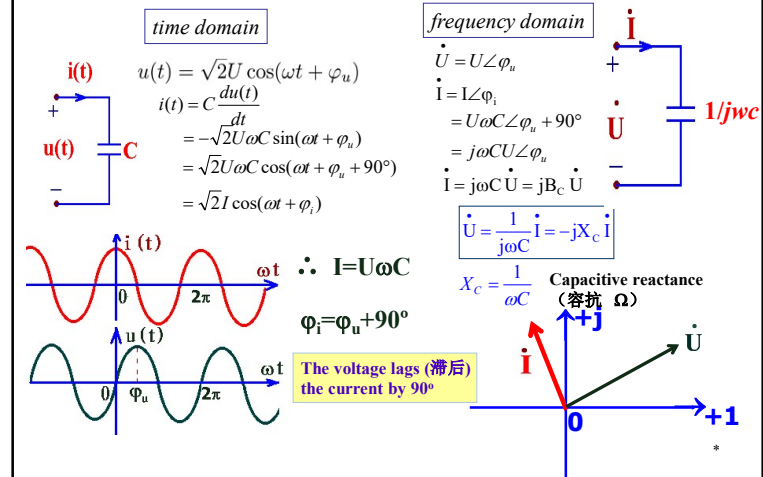
### 9.5.3 The V-I Characteristic for a Capacitor



**Instantaneous power**

$$p(t) = u(t)i(t)$$

$$i(t) = \sqrt{2}I \cos(\omega t + \varphi_i)$$


$$u(t) = \sqrt{2}U \cos(\omega t + \varphi_u)$$

$$p(t) = \sqrt{2}U \cos(\omega t + \varphi_u) \sqrt{2}I \cos(\omega t + \varphi_i)$$

$$= UI \cos(2\omega t + 2\varphi_u + 90^\circ)$$

**Average power**

$$P = \frac{1}{T} \int_0^T p(t) dt = 0$$

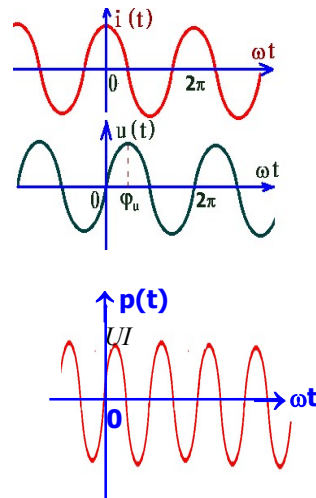

### Kirchhoff's Laws in the Frequency Domain (频域中的基尔霍夫定律)


$$\sum_{k=1}^n \dot{I}_{km} = 0$$


$$\sum_{k=1}^n \dot{I}_k = 0$$

$$\sum_{k=1}^n \dot{U}_{km} = 0$$

$$\sum_{k=1}^n \dot{U}_k = 0$$

The V-I Characteristic for a Resistor

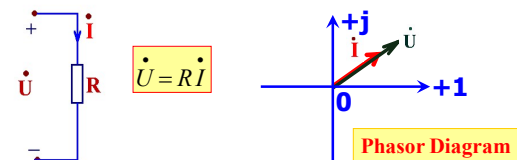

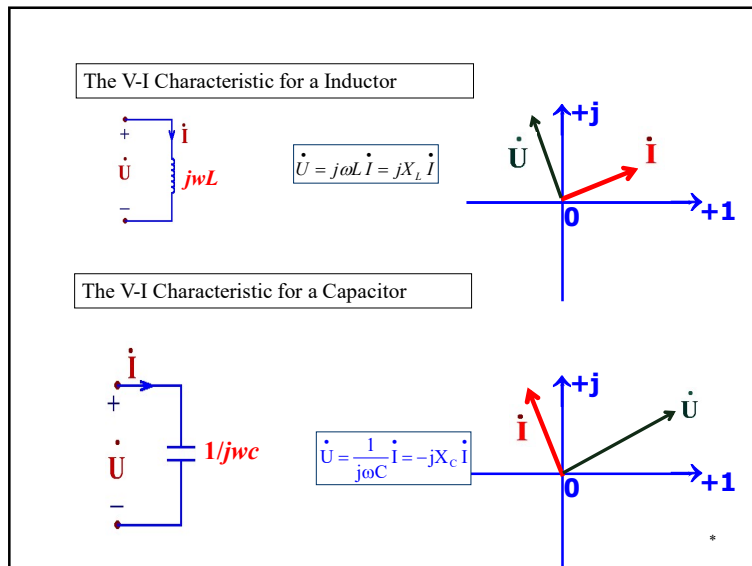

Exercise 3. In the following circuit,  $U_R = 6\text{ V}$ ,  $U_L = 18\text{ V}$ ,  $U_C = 10\text{ V}$ .

Find  $U = ?$

解: 设  $\dot{I} = I \angle 0^\circ$  (reference phasor)

$$\dot{U}_R = 6 \angle 0^\circ \quad \dot{U}_L = 18 \angle 90^\circ \quad \dot{U}_C = 10 \angle -90^\circ$$


$$\dot{U} = \dot{U}_R + \dot{U}_L + \dot{U}_C$$

$$= 6 + j18 - j10$$

$$= 6 + j8$$

$$= 10 \angle 53.1^\circ \text{ V}$$

$$\therefore U = 10 \text{ V}$$

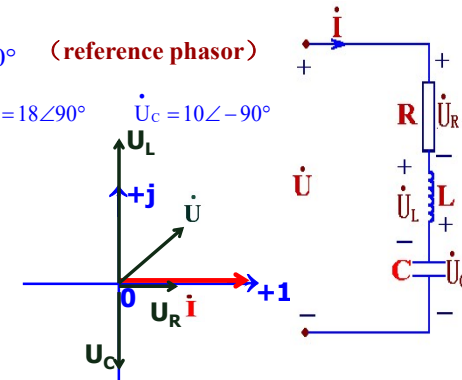

Example 4. In the circuit, the value of  $A_1$ ,  $A_2$  are both  $10\text{ A}$ .


Find the value of the  $I$ .

**Solution**

Assume  $\dot{U} = U \angle 0^\circ$   $\dot{I}_2 = 10 \angle 90^\circ$

$$\dot{I}_1 = 10 \angle -90^\circ$$

$$\dot{I} = \dot{I}_1 + \dot{I}_2 = 0$$

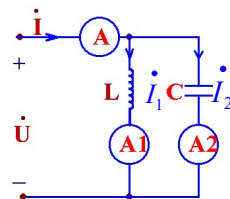


## Brief summary

元件	$u, i$ 关系	相量关系	大小关系	相位	$P(W)$
	$u = Ri$	$\dot{U} = R\dot{I}$	$U = RI$	$\dot{U}$ 与 $\dot{I}$ 同相	$PR$
	$u = L \frac{di}{dt}$	$\dot{U} = j\omega L \dot{I}$	$U = \omega LI$	$\dot{U}$ 超前 $\dot{I}$ $90^\circ$	0
	$i = C \frac{du}{dt}$	$\dot{U} = -j \frac{1}{\omega C} \dot{I}$	$U = \frac{1}{\omega C} I$	$\dot{U}$ 滞后 $\dot{I}$ $90^\circ$	0

49

## Impedance (阻抗) and Admittance (导纳)

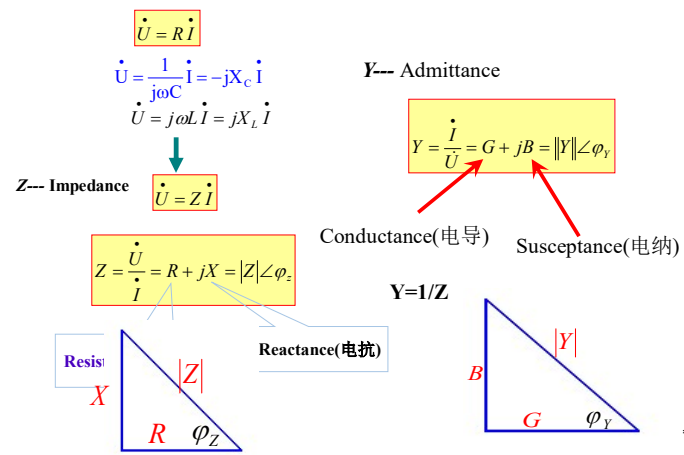

## 符号约定

瞬时值 --- 小写  $u$ 、 $i$   
 有效值 --- 大写  $U$ 、 $I$   
 最大值 --- 大写+下标  $U_m$   
 复数、相量 --- 大写 + “.”  $\dot{U}$

51

$$u = 100 \cos \omega t \neq \dot{U}$$

瞬时值 (pointing to  $u$ )  
 复数 (pointing to  $\dot{U}$ )

52