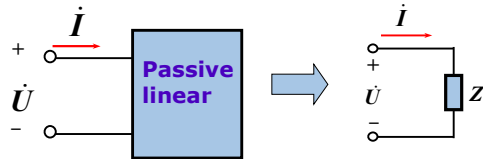


Impedance (阻抗) and Admittance (导纳)

1. Impedance (阻抗)



$$Z \stackrel{\text{def}}{=} \frac{\dot{U}}{\dot{I}} = |Z| \angle \varphi = R + jX$$

$$(\varphi = \psi_u - \psi_i)$$

{	Resistor	$Z=R$	
	Inductor	$Z=j\omega L=jX_L$	$X_L=\omega L$
	Capacitor	$Z=1/j\omega C=jX_C$	$X_C=-\frac{1}{\omega C}$

53

$$Z = \frac{\dot{U}}{\dot{I}} = \frac{\dot{U}_R + \dot{U}_L + \dot{U}_C}{\dot{I}}$$

KVL

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$= R + j(\omega L - \frac{1}{\omega C}) \quad X_L = \omega L \quad X_C = -\frac{1}{\omega C}$$

$$= R + j(X_L + X_C)$$

$$= R + jX$$

$$Z = \frac{\dot{U}}{\dot{I}} = R + jX = |Z| \angle \varphi$$

$$|Z| = \sqrt{R^2 + X^2} = \frac{U}{I} \quad \Omega$$

$$\varphi = \arctg \frac{X}{R} = \varphi_u - \varphi_i$$

impedance angle (阻抗角)

$\varphi > 0$

Resistance (电阻)

$\varphi < 0$

Reactance (电抗)

impedance triangle (阻抗三角形) 54

$(\omega L > 1/\omega C)$

$\varphi > 0$

For R, L, and C series circuits
 $Z = R + j(\omega L - 1/\omega C) = |Z| \angle \varphi$

(1) $\omega L > 1/\omega C, \varphi > 0$
inductive circuit

(2) $\omega L < 1/\omega C, \varphi < 0$
capacitive circuit

(3) $\omega L = 1/\omega C, \varphi = 0$
resistance circuit

similar triangles

Example 5

$R=15 \Omega, L=12 \text{ mH}, C=5 \mu\text{F}$

$u(t) = 100\sqrt{2} \cos(5000t) \text{ V}$

Find $Z, \dot{I}, \dot{U}_R, \dot{U}_L, \dot{U}_C$, and draw the phase diagram

Solution: $\dot{U} = 100 \angle 0^\circ \text{ V}$

$j\omega L = j60 \Omega \quad -j\frac{1}{\omega C} = -j40 \Omega$

$Z = R + j\omega L - j\frac{1}{\omega C} = 25 \angle 53.1^\circ \Omega$


$\dot{I} = \frac{\dot{U}}{Z} = 4 \angle -53.1^\circ \text{ A}$

$\dot{U}_R = \dot{I} R = 60 \angle -53.1^\circ \text{ V}$

$\dot{U}_L = j\omega L \dot{I} = 240 \angle 36.87^\circ \text{ V}$

$\dot{U}_C = -j\frac{1}{\omega C} \dot{I} = 160 \angle -143.13^\circ \text{ V}$


56

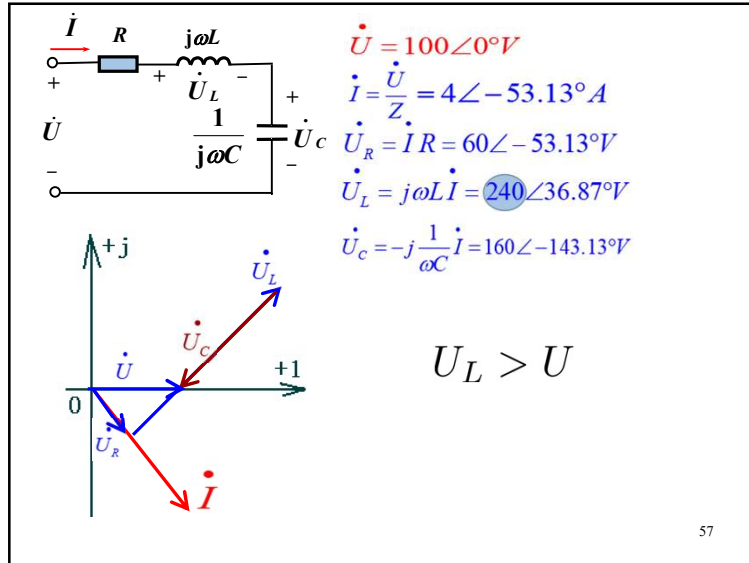

57

Impedance (阻抗) and Admittance (导纳)

2. Admittance (导纳)

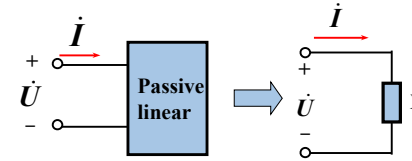


$$Y \stackrel{\text{def}}{=} \frac{\dot{I}}{\dot{U}} = G + jB = |Y| \angle \varphi' \quad (\varphi' = \psi_i - \psi_u)$$


{	Resistor	$Y_R = 1/R$	$B_L = -\frac{1}{\omega L}$	$Y = \frac{1}{Z}$
	Inductor	$Y_L = \frac{1}{j\omega L} = jB_L$		
	Capacitor	$Y_C = j\omega C = jB_C$		

$B_C = \omega C$

58

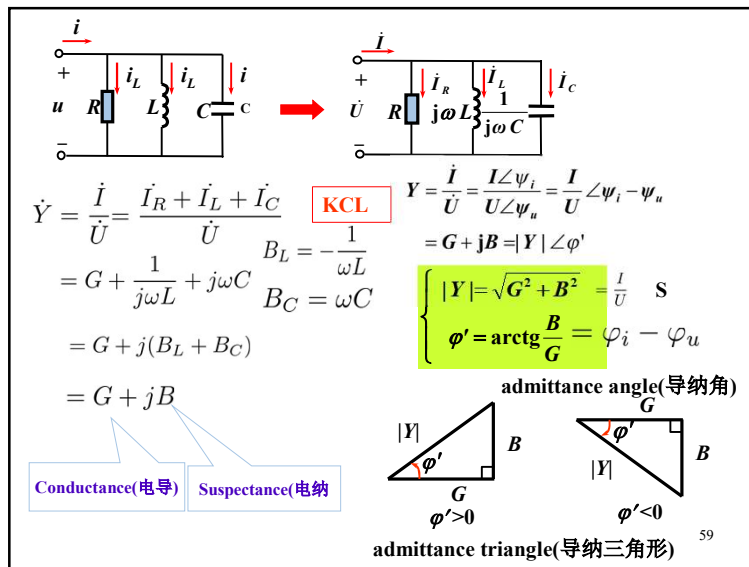

59

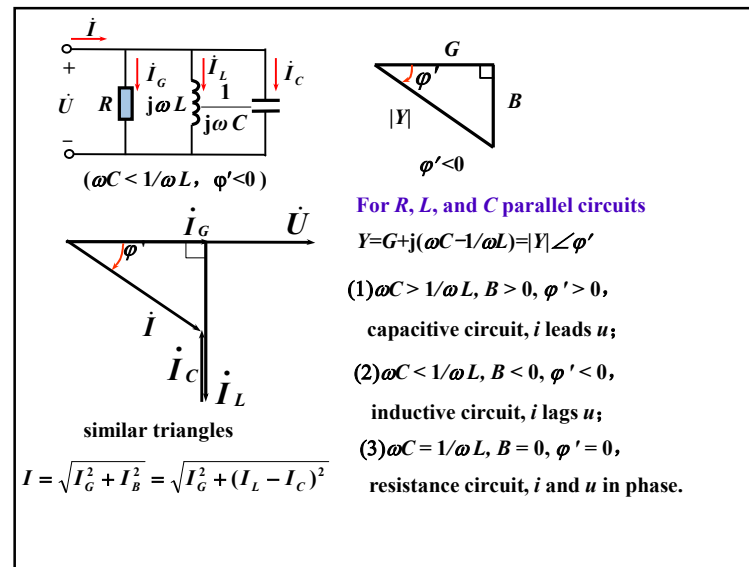

Impedance (阻抗) and Admittance (导纳)

3. Equivalent relation between Impedance and Admittance



$$Z = R + jX = |Z| \angle \varphi \Rightarrow Y = G + jB = |Y| \angle \varphi'$$


$$Y = \frac{1}{Z} = \frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2} = G + jB$$

$$\therefore G = \frac{R}{R^2 + X^2}, \quad B = \frac{-X}{R^2 + X^2}$$

$$|Y| = \frac{1}{|Z|}, \quad \varphi' = -\varphi$$

- (1) $G \neq 1/R, \quad B \neq 1/X$
(2) inductive circuit, $X > 0, \quad B < 0$

61

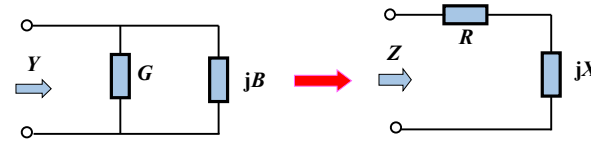

$$Y = G + jB = |Y| \angle \varphi', \quad Z = R + jX = |Z| \angle \varphi$$

$$Z = \frac{1}{Y} = \frac{1}{G + jB} = \frac{G - jB}{G^2 + B^2} = R + jX$$



$$\therefore R = \frac{G}{G^2 + B^2}, \quad X = \frac{-B}{G^2 + B^2}$$

$$|Y| = \frac{1}{|Z|}, \quad \varphi = -\varphi'$$

62

Impedance (阻抗) and Admittance (导纳)

4. Series and parallel impedances

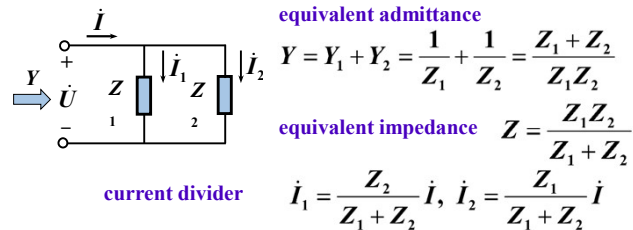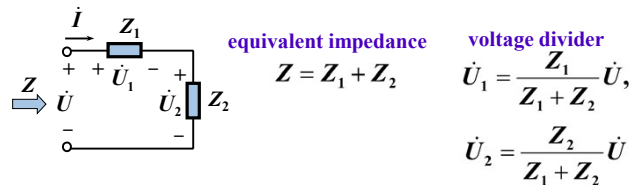

63

Impedance (阻抗) and Admittance (导纳)

4. Series and parallel impedances

(1) A series combination of N impedances

equivalent impedance $Z = \sum_{k=1}^n Z_k$

voltage divider $\dot{U}_k = \frac{Z_k}{\sum_{k=1}^n Z_k} \dot{U} \quad (k = 1, 2, \dots, n)$

(2) A parallel combination of N impedances

equivalent admittance $Y = \sum_{k=1}^n Y_k$


current divider $\dot{I}_k = \frac{Y_k}{\sum_{k=1}^n Y_k} \dot{I} \quad (k = 1, 2, \dots, n)$

64

Example 6. $R=6\Omega$, $X=8\Omega$, $f=50\text{Hz}$.

(1) Find G and B .

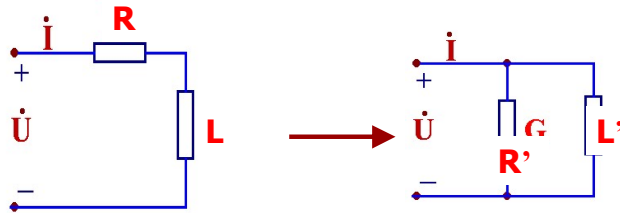(2) Find element parameters in series and parallel structures.



Solution: $Z = 6 + j8 = 10\angle 53.13^\circ$

$R = 6\Omega$ $L = 25.48\text{mH}$

$Y = \frac{1}{Z} = 0.1\angle -53.13^\circ$
 $= 0.06 - j0.08$

$R' = \frac{1}{G} = 16.67\Omega$
 $L' = 39.8\text{mH}$

$Y = G + jB$ $G = 0.06\text{S}$ $B = -0.08\text{S}$

65

Exercise.

$u(t) = 2\sqrt{2} \cos(10^4 t + 30^\circ)\text{V}$

$i(t) = 100\sqrt{2} \cos(10^4 t + 60^\circ)\text{mA}$


Find Z , Y and equivalent element param

Solution:

$\dot{U} = 2\angle 30^\circ\text{V}$ $\dot{I} = 100\angle 60^\circ\text{mA}$

$Z = \frac{\dot{U}}{\dot{I}} = 20\angle -30^\circ = 17.32 - j10(\Omega)$

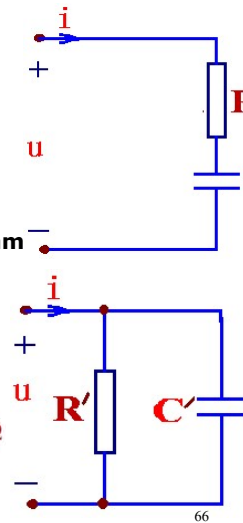
$R = 17.32\Omega$ $C = 10\mu\text{F}$
 $Y = \frac{\dot{I}}{\dot{U}} = 0.05\angle 30^\circ$ $R' = \frac{1}{G'} = 23.1\Omega$
 $= 0.0433 + j0.025(\text{S})$ $C' = \frac{B'}{\omega} = 2.5\mu\text{F}$



66

Example $Z_1=10+j6.28\Omega$, $Z_2=20-j31.9\Omega$, $Z_3=15+j15.7\Omega$

Find Z_{ab}

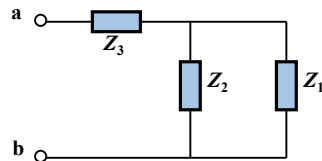

Solution: $Z = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(10 + j6.28)(20 - j31.9)}{10 + j6.28 + 20 - j31.9}$
 $= \frac{11.81\angle 32.13^\circ \times 37.65\angle -57.61^\circ}{39.45\angle -40.5^\circ}$

$= 10.89 + j2.86\Omega$

$\therefore Z_{ab} = Z_3 + Z = 15 + j15.7 + 10.89 + j2.86$
 $= 25.89 + j18.56 = 31.9\angle 35.6^\circ \Omega$

答题规范：
 写出表达式
 →代入数值
 →得到结果
 →写上单位

67

Brief summary

(1) $\dot{U} = \dot{I}Z$ $\dot{U} = \dot{I}Z$ 相量形式
 $Y = \frac{\dot{I}}{\dot{U}}$ $\dot{I} = Y\dot{U}$ 欧姆定理



(2) Sinusoidal Steady-State Analysis Steps

- ① Transform the circuit to the phasor or frequency domain.
 Transform all independent sources to their phasor equivalent.
 $u \ i \longrightarrow \dot{U} \ \dot{I}$
 Calculate the impedance (Z) of all passive circuit elements.
 $R, L, C \longrightarrow Z, Y$
- ② Apply analysis method in the frequency domain.
- ③ Transform the resulting phasor to the time domain.

68

9.6 Nodal and Mesh Analysis

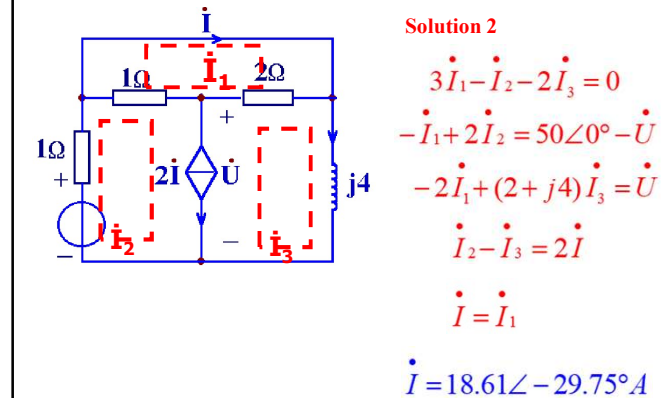
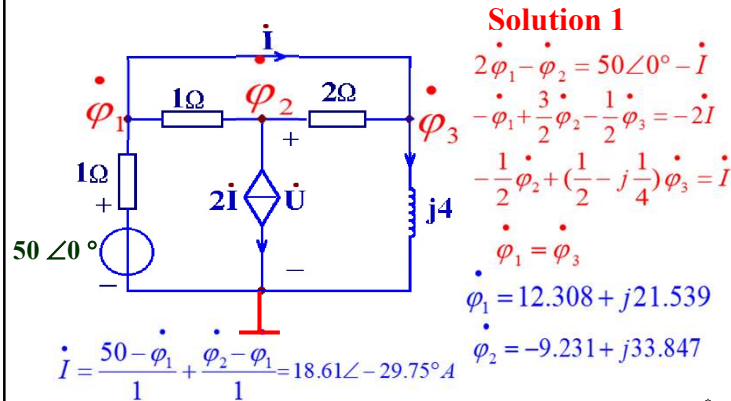
Example 6: Find I in the following circuit.



9.7 Superposition, Source Transformations, and Thevenin's theorem

Circuits containing inductors and capacitors were still linear, so the benefits of linearity were again available. Included among these were all above theorems.


Example 7. In the following circuit, $u(t) = 60\sqrt{2}\cos(10^4 t)V$. Calculate $i(t)$ when (1) $R = 75\Omega$ (2) $R = 25\Omega$.

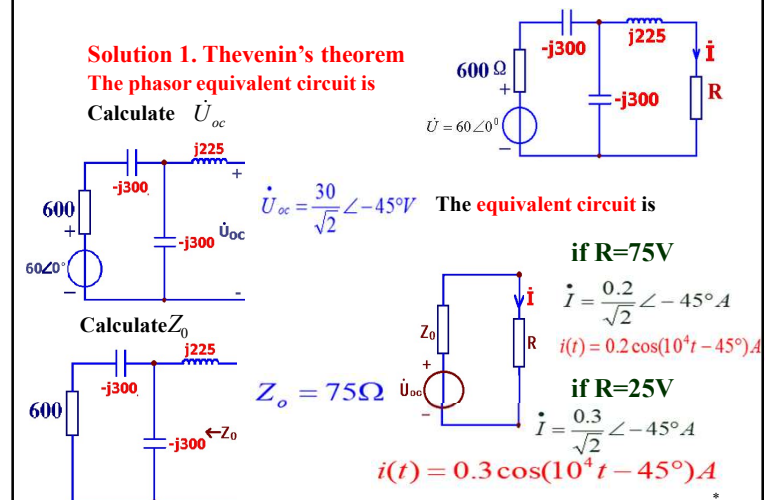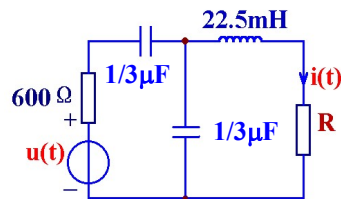


Solution 2.

Source Transformations

The phasor equivalent circuit is

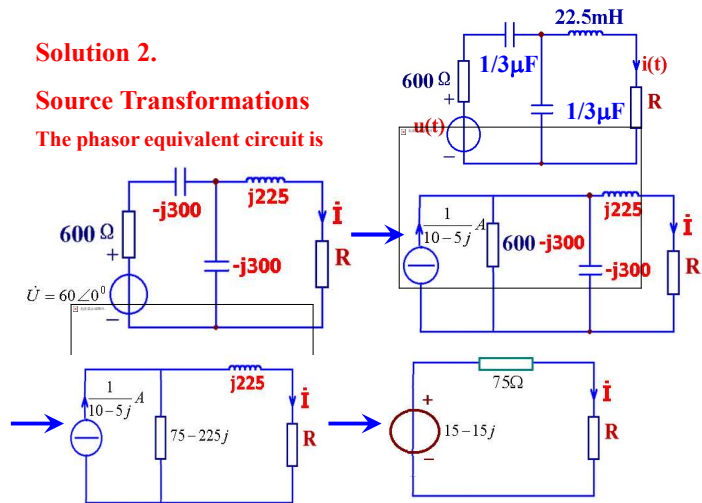

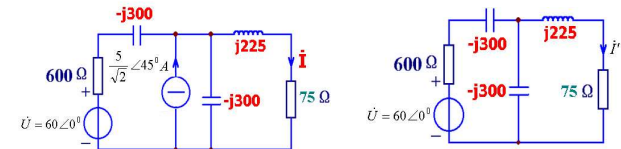Example 8. In the following circuit, use superposition to find I .




Solution: Let voltage source acts alone

$$\dot{I}' = 0.2 - 0.2j \text{ A}$$

Let current source acts alone

$$\dot{I}'' = -2.5 + 5j \text{ A}$$
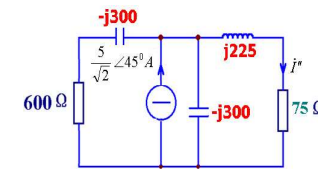
$$\dot{I} = \dot{I}' + \dot{I}'' = -2.3 + 4.8j \text{ A}$$



Brief summary

Sinusoidal Steady-State Analysis Steps

- ① Transform the **circuit** to the phasor or frequency domain.
Transform all independent **sources to their phasor equivalent**.
 $u \ i \longrightarrow \dot{U} \ \dot{I}$
Calculate the **impedance (Z)** of all passive circuit elements.
 $R, L, C \longrightarrow Z, Y$
- ② Apply analysis method in the frequency domain.
- ③ Transform the resulting phasor to the time domain.

Nodal and Mesh Analysis, Superposition, Source Transformations, and Thevenin's theorem...

75

$$\dot{U} = 50e^{j15^\circ} \neq 50\sqrt{2} \cos(\omega t + 15^\circ)$$

复数

瞬时值

76

已知: $i = 10 \cos(\omega t + 45^\circ)$

$I \neq \frac{10}{\sqrt{2}} \angle 45^\circ$

有效值

$\dot{I} \neq 10e^{j45^\circ}$

77

已知: $u = 10\sqrt{2} \cos(\omega t - 15^\circ)$

则: $U \neq 10$

$\dot{U} \neq 10e^{j15^\circ}$

78

已知: $\dot{I} = 100 \angle 50^\circ$

则: $i \neq 100 \cos(\omega t + 50^\circ)$

最大值

$I_m = \sqrt{2}I = 100\sqrt{2}$

79