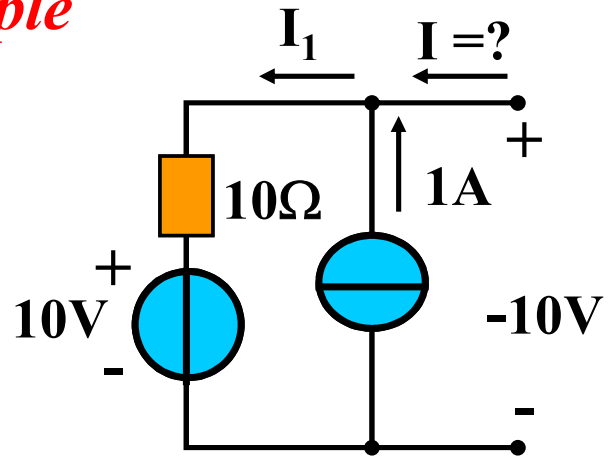


*Example*




**Solution**

$$10I_1 + 10 - (-10) = 0$$

$$I_1 = -2A$$

$$I = I_1 - 1 = -2 - 1 = -3A$$

*Example*

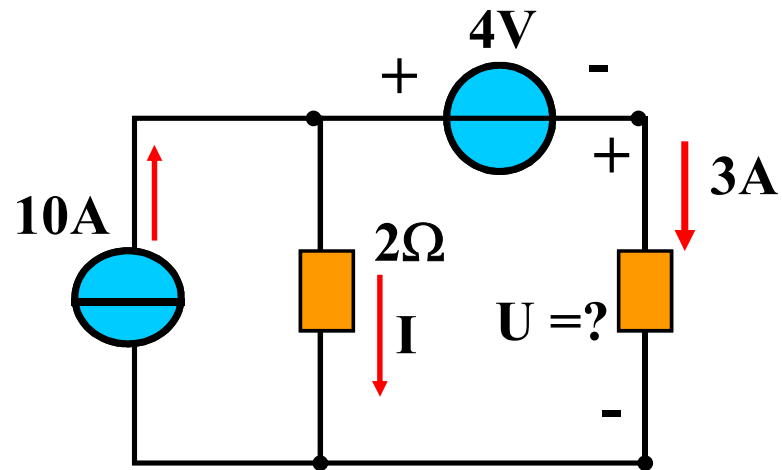


**Solution**

$$I = 10 - 3 = 7A$$

$$4 + U - 2I = 0$$

$$U = 2I - 4 = 14 - 4 = 10V$$


*Example*

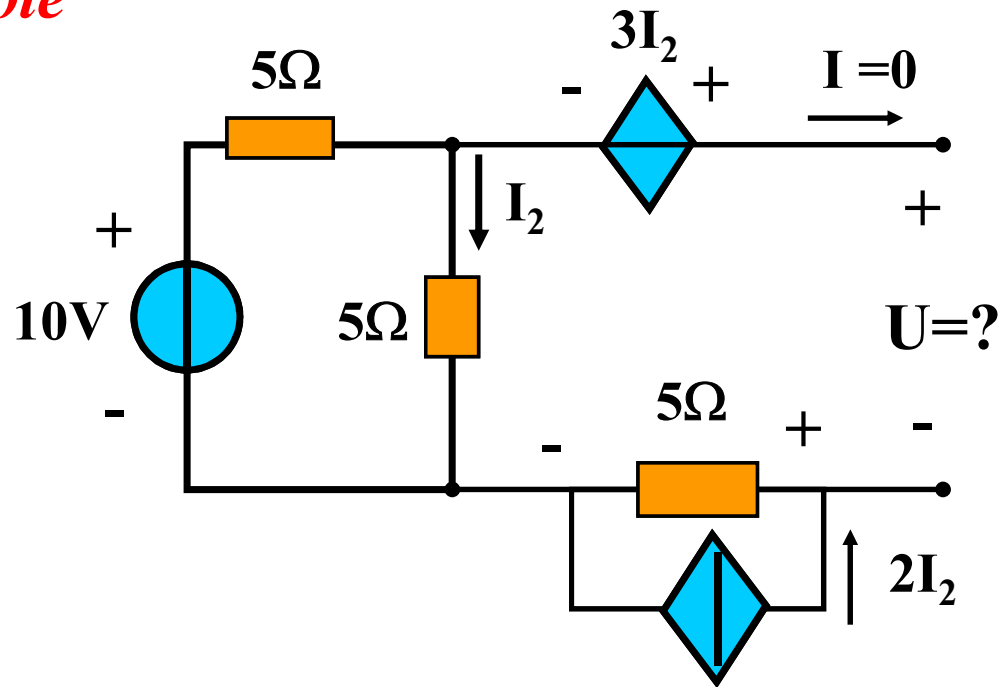

**Solution**

$$I_2 = \frac{10}{5+5} = 1A$$

### Example

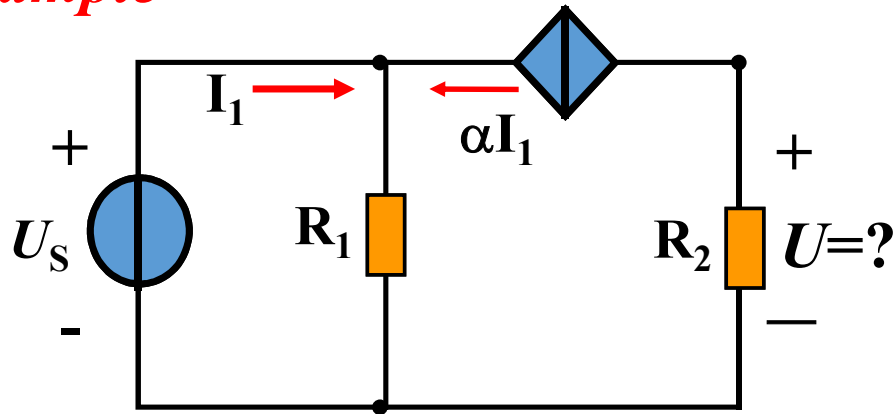

### Solution

$$U = -R_2 \alpha I_1$$

$$I_1 + \alpha I_1 = U_s / R_1$$

$$\rightarrow I_1 = \frac{U_s}{R_1(1 + \alpha)}$$

$$\rightarrow U = -\frac{\alpha R_2 U_s}{R_1(1 + \alpha)}$$


$$P_s = U_s I_1 = \frac{U_s^2}{R_1(1 + \alpha)}$$

$$P_o = R_2 \alpha^2 \frac{U_s^2}{R_1^2(1 + \alpha)^2}$$

$$\left| \frac{U}{U_s} \right| = \frac{R_2}{R_1} \frac{\alpha}{(1 + \alpha)}$$

$$\left| \frac{P_o}{P_s} \right| = \frac{R_2}{R_1} \frac{\alpha^2}{(1 + \alpha)}$$

选择参数可以得到电压和功率放大

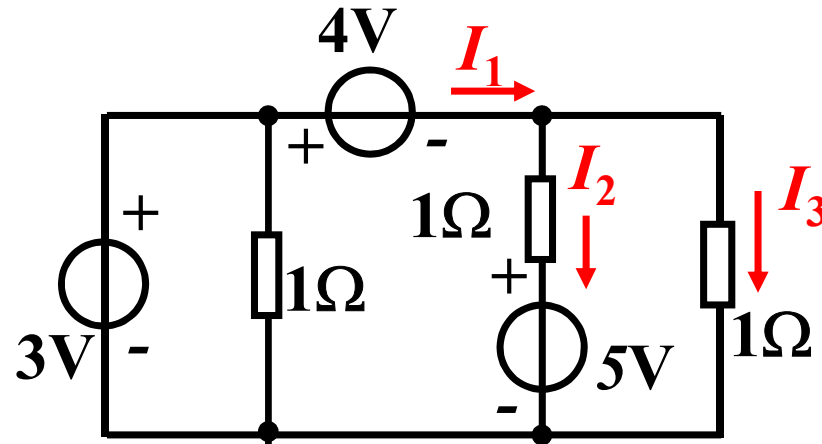

Find:  $I_1$ 、 $I_2$ 、 $I_3$

?

$$I_3 = \frac{3 - 4}{1} = -1 \text{ A}$$


$$I_2 = \frac{3 - 4 - 5}{1} = -6 \text{ A}$$

$$I_1 = I_2 + I_3 = -7 \text{ A}$$

## Example 4

For the circuit in Fig. 2.5a, compute the current through resistor  $R_3$  if it is known that the voltage source supplies a current of 3 A.

Fig. 2.5

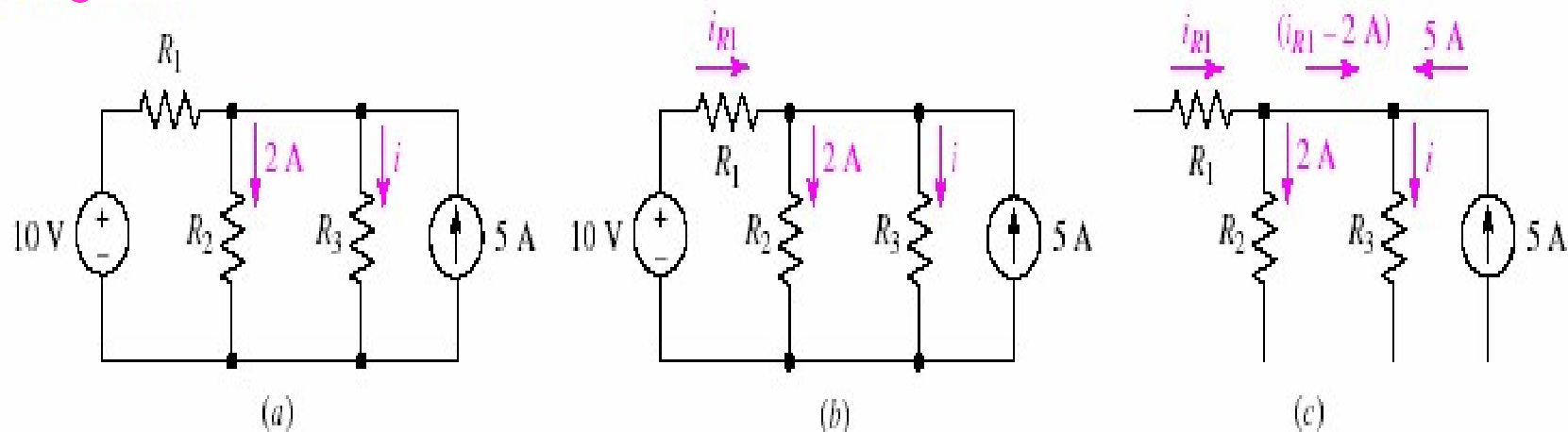

(a) Simple circuit for which the current through resistor  $R_3$  is desired. (b) The current through resistor  $R_1$  is labeled so that a KCL equation can be written. (c) The currents into the top node of  $R_3$  are redrawn for clarity.

## Example 6

Find the current  $I_T$  in Fig. 2.7(a)

Solution


Applying KCL to node  $a$  yields

$$I_T + I_2 = I_1 + I_3$$


or

$$I_T = I_1 - I_2 + I_3$$

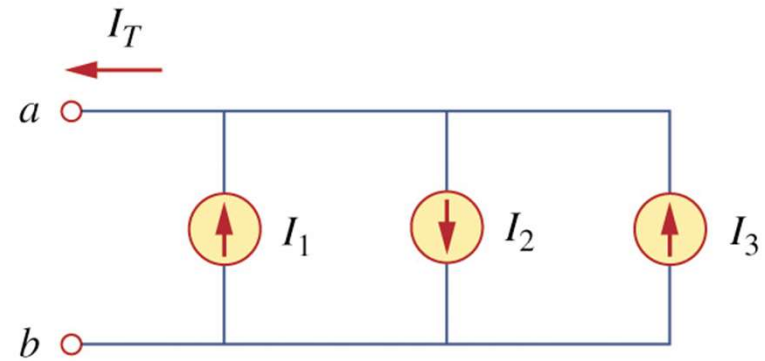**Note:** a circuit cannot contain two different currents,  $I_1$  and  $I_2$ , in series, unless  $I_1 = I_2$ ; otherwise KCL will be violated



(a)

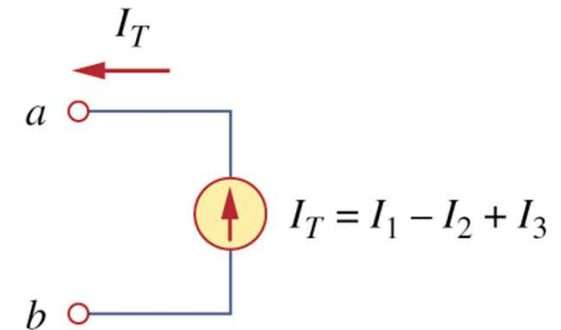

(b)

Fig. 2.7

## Example 7

Determine the voltage  $v_{ab}$  in Fig. 2.8(a)

Solution

By applying KVL , we obtain

$$-V_{ab} + V_1 + V_2 - V_3 = 0$$

or

$$V_{ab} = V_1 + V_2 - V_3$$

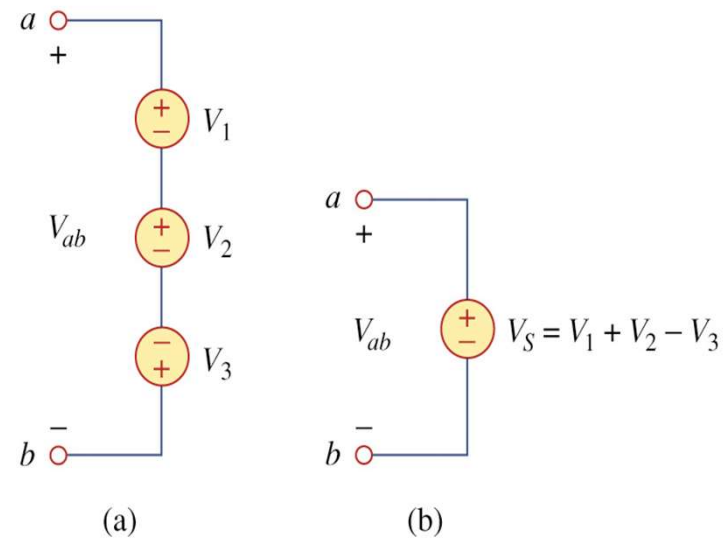


Fig. 2.8

To avoid violating KVL, a circuit cannot contain two different voltages  $V_1$  and  $V_2$  in parallel unless  $V_1 = V_2$ .



## Example 8

For the circuit in Fig. 2.9(a), find voltages  $v_1$  and  $v_2$ .

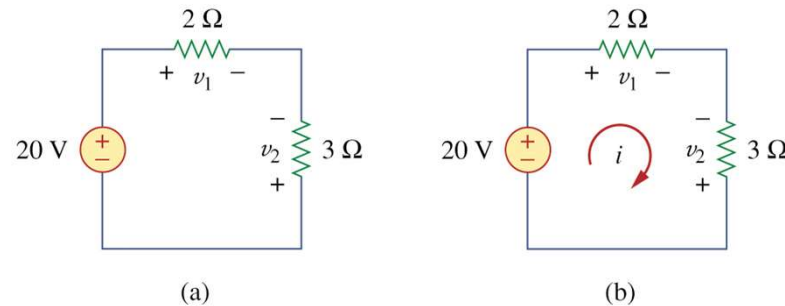


Fig. 2.9

Solution:

To find  $v_1$  and  $v_2$ , we apply Ohm's law and Kirchhoff's voltage law. Assume that current  $i$  flows through the loop as shown in Fig. 2.9(b).

From Ohm's law,

$$v_1 = 2i, \quad v_2 = -3i$$

Applying KVL around the loop gives

$$-20 + v_1 - v_2 = 0$$

Substituting  $v_1$  and  $v_2$  into above equation, we obtain

$$-20 + 2i + 3i = 0 \quad \text{or} \quad 5i = 20 \quad \Rightarrow \quad i = 4\text{A}$$

Substituting  $i$  into the equations of the  $v_1$  and  $v_2$  finally gives


$$v_1 = 8\text{V}, \quad v_2 = -12\text{V}$$

---

### Example 9

Determine  $v_0$  and  $i$

In the circuit shown in Fig.2.10

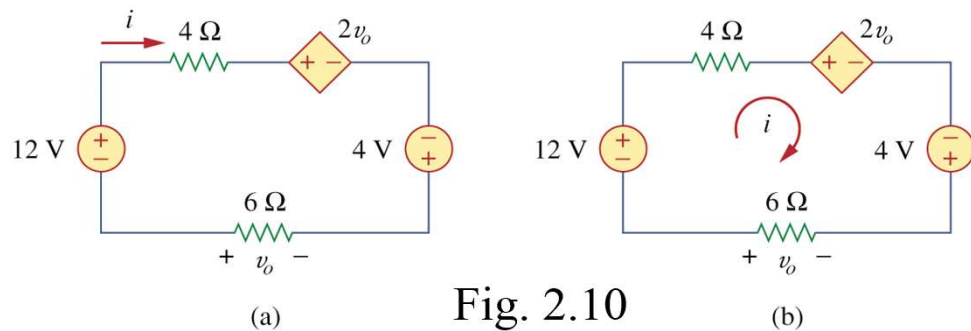

**Solution:**

We apply KVL around the loop as shown in Fig. 2.10(b). The results is

$$-12 + 4i + 2v_0 - 4 + 6i = 0 \quad (*)$$

Applying Ohm's law to the 6-Ω resistor gives

$$v_0 = -6i$$

Substituting  $v_o$  into Eq.(\*) yields

$$-16 + 10i - 12i = 0 \Rightarrow i = -8 \text{ A}$$

---

### Example 10

Determine current  $i_o$  and voltage  $v_o$  and in the circuit shown in Fig. 2.11

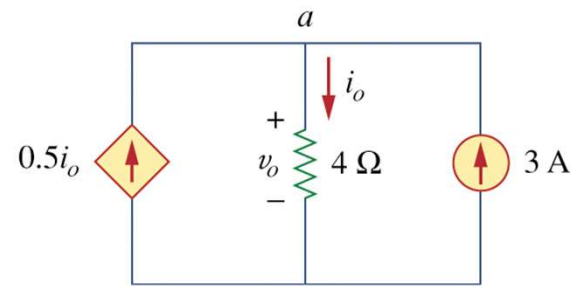


Fig. 2.11

Solution:

Applying KCL to node a, we obtain

$$3 + 0.5i_o - i_o = 0 \Rightarrow i_o = 6 \text{ A} \quad v_o = 24 \text{ V}$$

## Example 11

Find the currents and voltages in the circuit shown in Fig. 2.12(a).

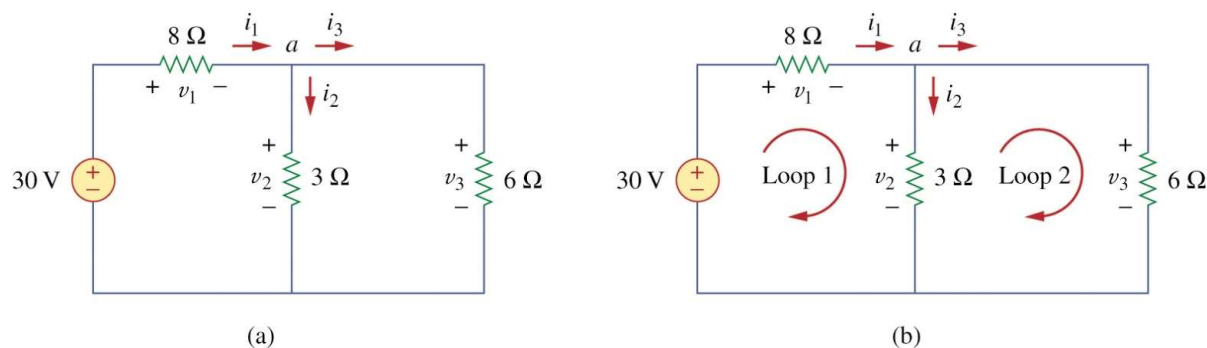


Fig. 2.12

Solution

We apply Ohm's law and Kirchhoff's laws. By Ohm's law,

$$v_1 = 8i_1, \quad v_2 = 3i_2, \quad v_3 = 6i_3 \quad (2-1)$$

Since the voltage and current of each resistor are related by Ohm's law as shown, we are really looking for three things:  $(v_1, v_2, v_3)$  or  $(i_1, i_2, i_3)$ .

At node  $a$ , KCL gives

$$i_1 - i_2 - i_3 = 0 \quad (2-2)$$

Applying KVL to loop 1 as in Fig. 2.12(b),

$$-30 + v_1 + v_2 = 0 \quad (2-3)$$

We express this in terms of  $i_1$  and  $i_2$  as in Eq.(2-1) to obtain

$$-30 + 8i_1 + 3i_2 = 0 \quad (2-4)$$

or

$$i_1 = \frac{(30 - 3i_2)}{8}$$

Applying KVL to loop 2,

$$-v_2 + v_3 = 0 \quad \Rightarrow \quad v_3 = v_2$$

as expected since the two resistors are in parallel. We express  $v_1$  and  $v_2$  in terms of  $i_1$  and  $i_2$  as in Eq.(2-1). Equation (2-4) becomes

$$6i_3 = 3i_2 \quad \Rightarrow \quad i_3 = \frac{i_2}{2} \quad (2-5)$$

Substituting Eqs.(2-3) and (2-3) into (2-2) gives

$$\frac{30-3i_2}{8} - i_2 - \frac{i_2}{2} = 0$$

or  $i_2=2\text{A}$ . From the value of  $i_2$ , we now use Eqs. .(2-1) and (2-5) to obtain

$$i_1 = 3\text{A} , i_3 = 1\text{A}, \quad v_1 = 24\text{V}, \quad v_2 = 6\text{V}, \quad v_3 = 6\text{V}$$