

Fundamentals of Electric Circuit

2020. 05-06

Chapter 9

Sinusoidal Steady-State Analysis

Chapter 9 Sinusoidal Steady-State Analysis

9.1 The Sinusoidal Source

~~9.2 The Sinusoidal Response~~

9.3 Phasor

9.4 Kirchhoff's Laws in the Frequency Domain

9.5 The Passive Circuit Elements in the Frequency Domain

9.6 Nodal and Mesh Analysis


Chapter 9 Sinusoidal Steady-State Analysis

9.7 Superposition, Source Transformations, and Thevenin's theorem

9.8 Phasor Diagrams


9.9 AC Circuit Power Analysis

DC or AC ?

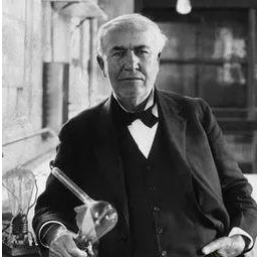

Thomas Edison
(1847.02.11-1931.10.18)

DC

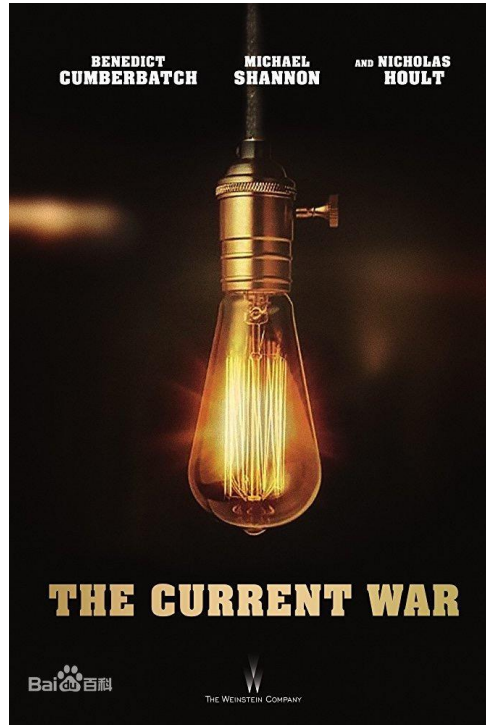

Nikola Tesla
(1856.07.10-1943.01.07)

AC

Transmission ✓
Transformer ✓

Tesla Coil



Wardenclyffe Tower



Magnetic flux density
 $1 \text{ Tesla} = 10000 \text{ Gs}$



Chapter 9 Sinusoidal Steady-State Analysis (正弦稳态分析)

AC Analysis

DC Analysis: voltage and current are constant with respect to time.


AC Analysis: voltage and current vary with time.

AC can be sinusoidal, square waves, or arbitrary periodic waveforms.

Sinusoidal is particularly important

- ✓ Commonly used, e.g., power systems, communications, etc.
- ✓ Simple periodic function (e.g., derivative and anti-derivative of a sinusoidal is also a sinusoidal)
- ✓ Any periodic function can be represented as the sum of sinusoidal function
=> **Fourier Series**

Steady-State Analysis

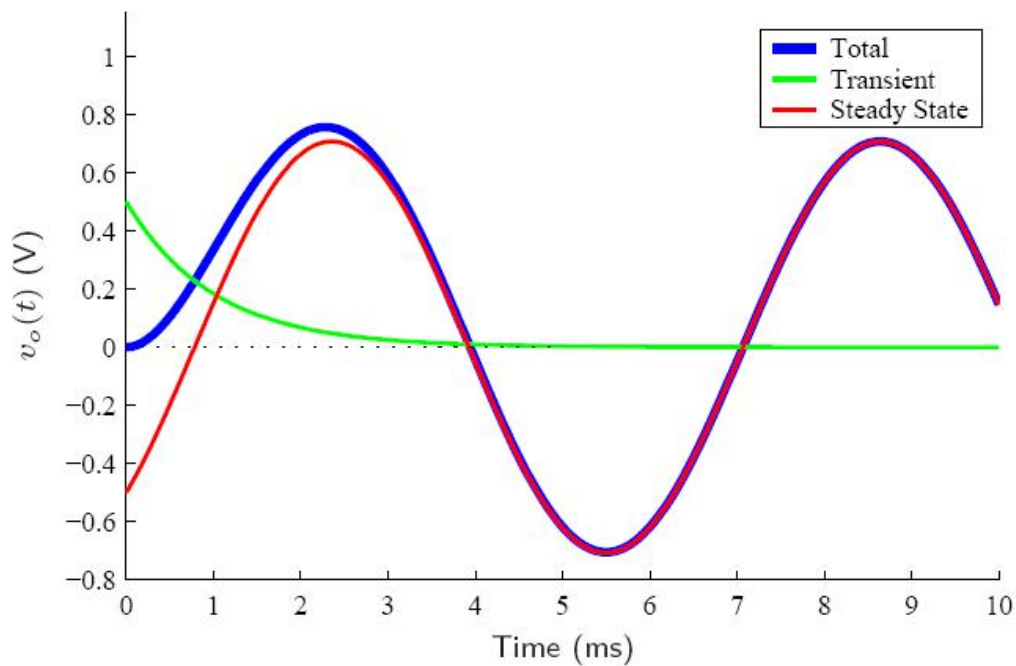

9.1 The Sinusoidal Source

Sinusoidal Sources: voltage or current sources that vary sinusoidally with time.

The sinusoidal voltage may be written as

$$u(t) = U_m \cos(\omega t + \varphi_u)$$

U_m : amplitude 幅值
 ω : angular frequency 角频率
 φ_u : initial phase angle 初相位
 phase angle

$$\omega = 2\pi f = 2\pi/T \quad \text{Unit: rad/s}$$

Initial phase angle $\varphi_u \Rightarrow$ time shift


$$\cos(\omega t_1 + \varphi_u) = 1$$

$$\omega t_1 + \varphi_u = 0$$

$$\varphi_u = -\omega t_1$$

if $\varphi_u > 0$, function shifts to the left.

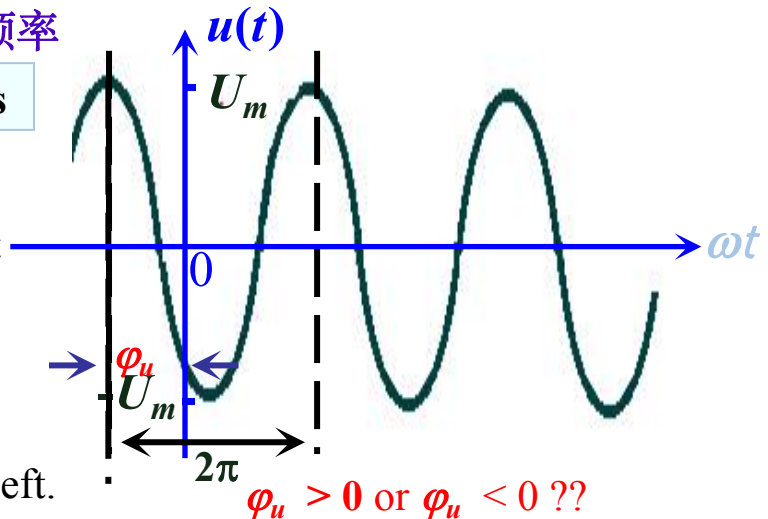if $\varphi_u < 0$, function shifts to the right.



$$|\varphi_u| \leq \pi$$

Unit: rad


*

Phase angle difference (相位差)

$$u(t)=U_m\cos(\omega t+\varphi_u), \quad i(t)=I_m\cos(\omega t+\varphi_i)$$


$$\varphi = (\omega t + \varphi_u) - (\omega t + \varphi_i) = \varphi_u - \varphi_i \quad |\varphi| \leq \pi$$

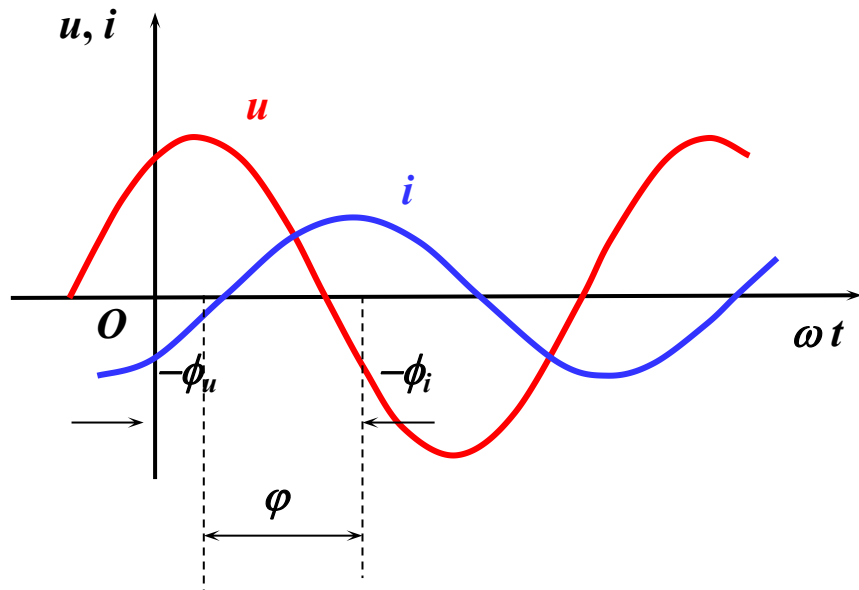- $\varphi > 0$, u **leads** (超前) i by φ , 或 i **lags** (滞后) u by φ (u 比 i 先到达最大值);




$$\varphi = \varphi_u - \varphi_i$$

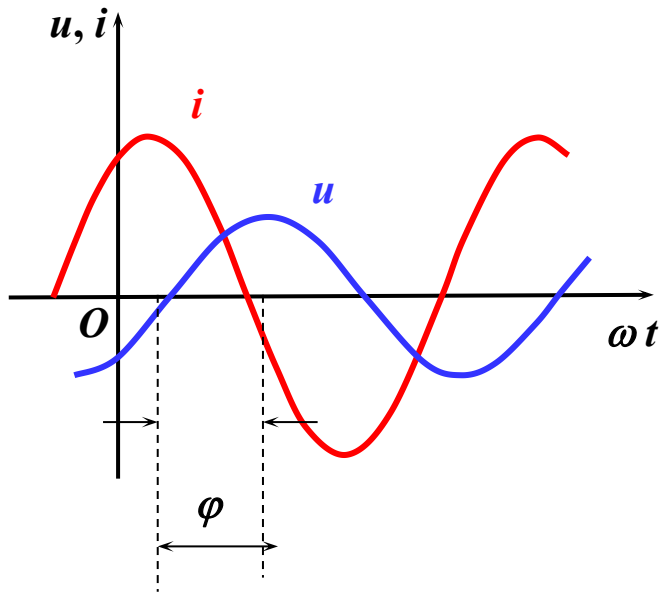- $\varphi < 0$, u **lags** (滞后) i by φ , 或 i **leads** (超前) u by φ




$$\varphi = \varphi_u - \varphi_i$$

$\varphi = 0$, in phase (同相) :

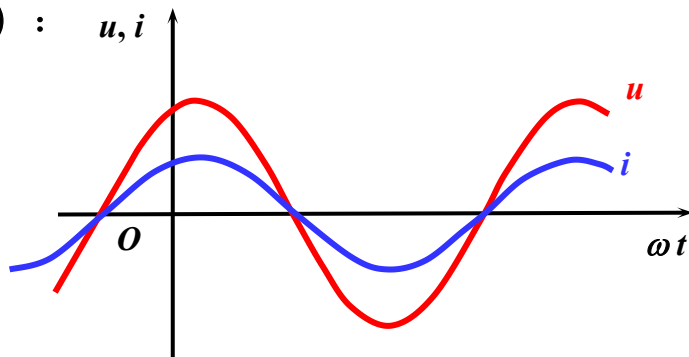


$\varphi = \pi$, out of phase (反相) :

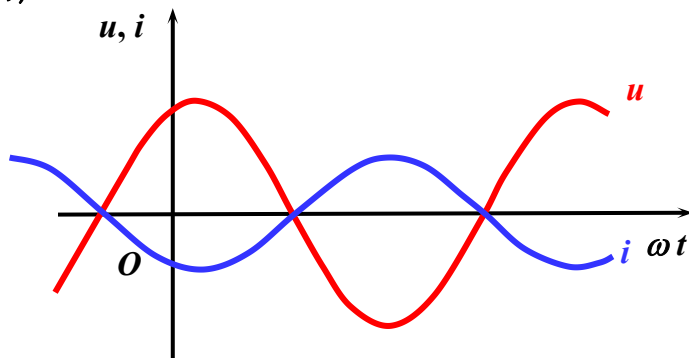


$$\varphi = \varphi_u - \varphi_i$$

$$\varphi = \pi/2 \text{ (正交)}$$

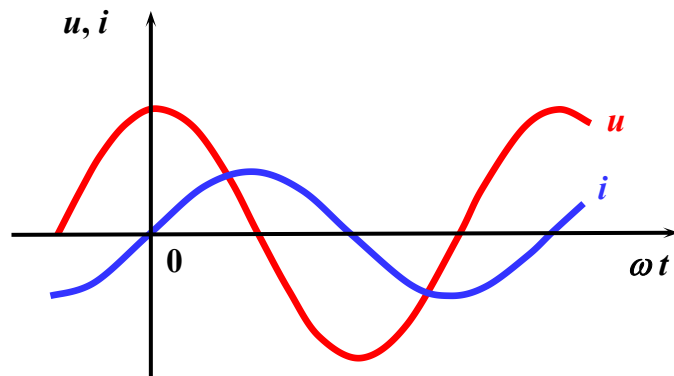


$$|\varphi| \leq \pi$$

Root mean square, RMS (有效值/方均根值)

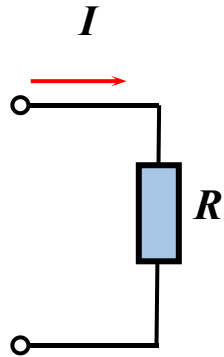

$$W = I^2 R T$$

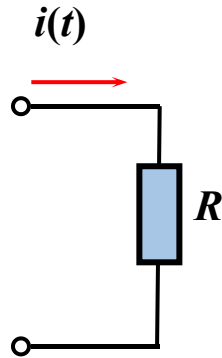


$$W_{\text{交}} = \int_0^T i^2(t) R dt$$

$$I^2 R T = \int_0^T i^2(t) R dt$$

$$I = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$U \stackrel{\text{def}}{=} \sqrt{\frac{1}{T} \int_0^T u^2(t) dt}$$

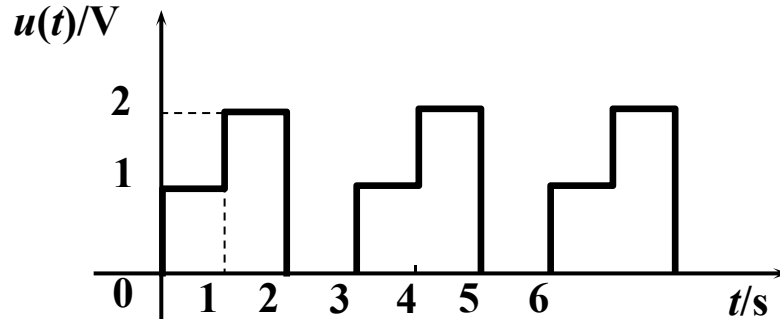Example: Calculate the RMS of the periodic function shown below



Solution: According to the definition of RMS,

$$\begin{aligned} U &= \sqrt{\frac{1}{T} \int_0^T u^2(t) dt} \\ &= \sqrt{\frac{1}{3} \left(\int_0^1 1^2 dt + \int_1^2 2^2 dt + \int_2^3 0^2 dt \right)} = 1.29 \text{ V} \end{aligned}$$

Root mean square for sinusoidal quantities

For $i(t)=I_m \cos(\omega t + \varphi_i)$

$$\begin{aligned} I &= \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \varphi_i) dt} \\ &= \sqrt{\frac{1}{T} \int_0^T I_m^2 \frac{1 + \cos[2(\omega t + \varphi_i)]}{2} dt} \end{aligned}$$

$$\therefore I = \sqrt{\frac{1}{T} I_m^2 \cdot \frac{T}{2}} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

$$\text{或} \quad I_m = \sqrt{2} I$$

$$u \quad i \quad U \quad I \quad U_m \quad I_m$$

Brief summary


(1) amplitude(幅值),angular frequency(角频率),
initial phase angle(初相位)

(2) Phase angle difference(相位差)

(3) Root mean square, RMS(有效值/方均根值)

$$u \quad i \quad U \quad I \quad U_m \quad I_m$$

9.3 Phasor (相量)

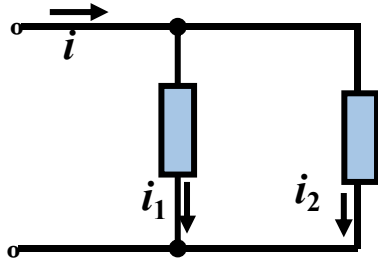

$$i_1 = 10\sqrt{2} \cos(314t - 60^\circ) A$$

$$i_2 = 22\sqrt{2} \cos(314t - 150^\circ) A$$

$$i = i_1 + i_2$$

$$i = 24.16\sqrt{2} \cos(314t - 125.55^\circ) A$$

amplitude(幅值), initial phase angle(初相位)

Complex number

9.3.1 Representation of Complex Numbers

Complex number = real number + imaginary number

$$z = x + jy$$

(1) Rectangular form



(2) Polar Form

$$z = x + jy = r \angle \theta \quad z = |z| \angle \theta$$

where

$$r = |z| = \sqrt{x^2 + y^2}$$


$$\theta = \tan^{-1}(y/x)$$

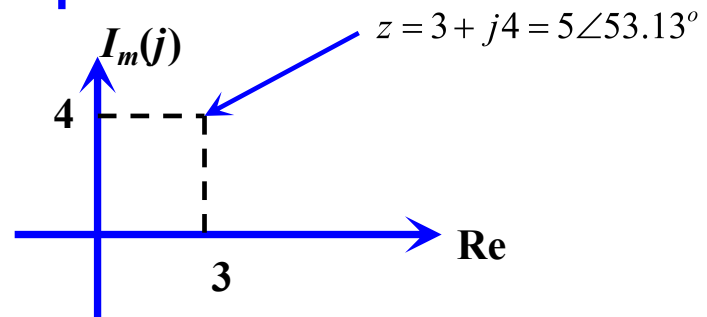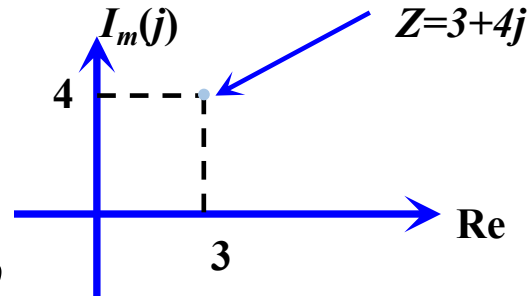

(3) Exponential form $z = re^{j\theta}$

$$z = r \angle \theta \quad \begin{cases} x = \operatorname{Re}\{z\} = r \cos(\theta) \\ y = \operatorname{Im}\{z\} = r \sin(\theta) \end{cases}$$

(projections)

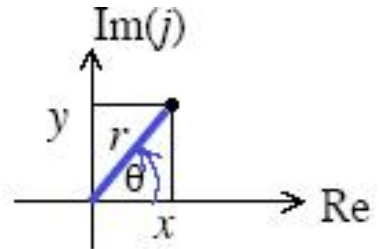

$$z = x + jy = r \cos(\theta) + jr \sin(\theta) = r (\cos(\theta) + j \sin(\theta)) = re^{j\theta} \quad \checkmark$$

Euler identity: $e^{\pm j\theta} = \cos\theta \pm j \sin\theta$

(1) Addition and subtraction: **Rectangular form**

$$A_1 = a_1 + jb_1, \quad A_2 = a_2 + jb_2$$


$$A_1 \pm A_2 = (a_1 \pm a_2) + j(b_1 \pm b_2)$$

(2) Multiplication and division: **Polar Form**

$$A_1 = |A_1| \angle \theta_1, \quad A_2 = |A_2| \angle \theta_2$$

$$A_1 A_2 = |A_1| |A_2| \angle \theta_1 + \theta_2$$

$$\frac{A_1}{A_2} = \frac{|A_1| \angle \theta_1}{|A_2| \angle \theta_2} = \frac{|A_1| e^{j\theta_1}}{|A_2| e^{j\theta_2}} = \frac{|A_1|}{|A_2|} e^{j(\theta_1 - \theta_2)} = \frac{|A_1|}{|A_2|} \angle \theta_1 - \theta_2$$

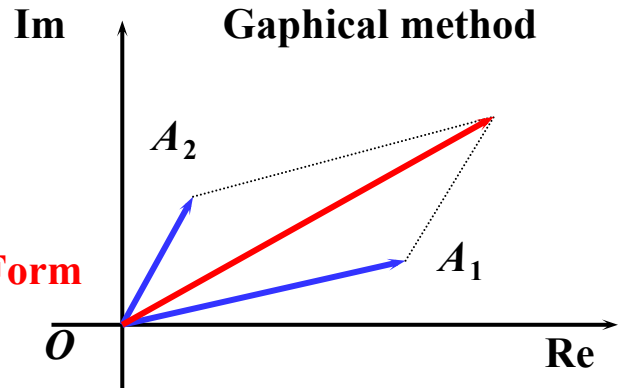


Example

$$\begin{aligned} & \frac{(10 + j6.28)(20 - j31.9)}{10 + j6.28 + 20 - j31.9} \\ &= \frac{11.81 \angle 32.13^\circ \times 37.65 \angle -57.61^\circ}{39.45 \angle -40.5^\circ} \\ &= 10.89 + j2.86 \end{aligned}$$

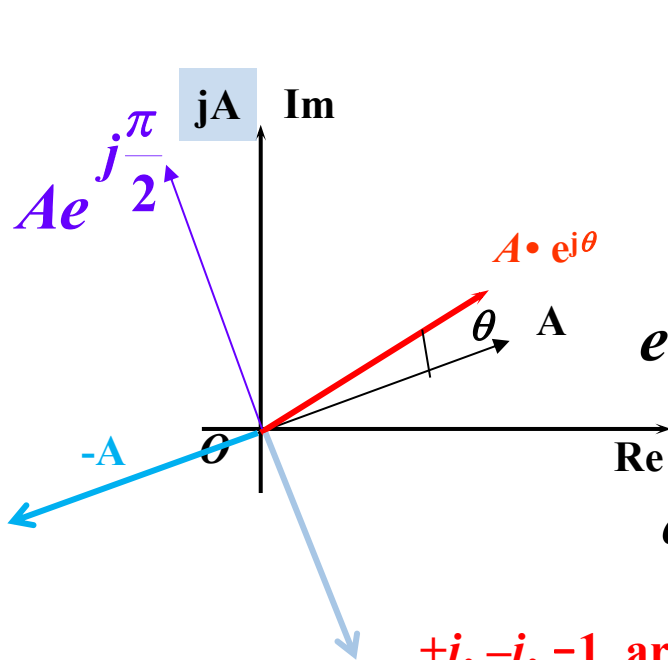(3) Twiddle factor (旋转因子) :

$$e^{j\theta} = 1 \angle \theta$$

Any of the trigonometric constant coefficients that are multiplied by the data in the course of the algorithm.



Euler's Identity

$$e^{j\frac{\pi}{2}} = \cos \frac{\pi}{2} + j \sin \frac{\pi}{2} = j$$

$$e^{-j\frac{\pi}{2}} = \cos \frac{\pi}{2} - j \sin \frac{\pi}{2} = -j$$

$$e^{j\pi} = \cos \pi + j \sin \pi = -1$$

$+j, -j, -1$ are all twiddle factors.

9.3.2 Phasor Notation


Suppose a sinusoidal voltage source:

$$\begin{aligned}
 u(t) &= U_m \cos(\omega t + \varphi_u) & \longleftrightarrow & A(t) = \sqrt{2}U e^{j(\omega t + \varphi_u)} & \text{Euler's Identity} \\
 & & & = \sqrt{2}U \cos(\omega t + \varphi_u) + j\sqrt{2}U \sin(\omega t + \varphi_u) \\
 \text{Re}[A(t)] &= \sqrt{2}U \cos(\omega t + \varphi_u) & A(t) &= \sqrt{2}U e^{j(\omega t + \varphi_u)} \\
 & & & = \underbrace{\sqrt{2}U e^{j\varphi_u}}_{\text{Phasor}} e^{j\omega t} = \sqrt{2}\dot{U} e^{j\omega t} \\
 \dot{U} &= \underbrace{U \angle \varphi_u}_{\text{standard polar form}}
 \end{aligned}$$

captures the two unknowns of the response signal (amplitude and phase angle)

standard polar form

9.3.2 Phasor Notation

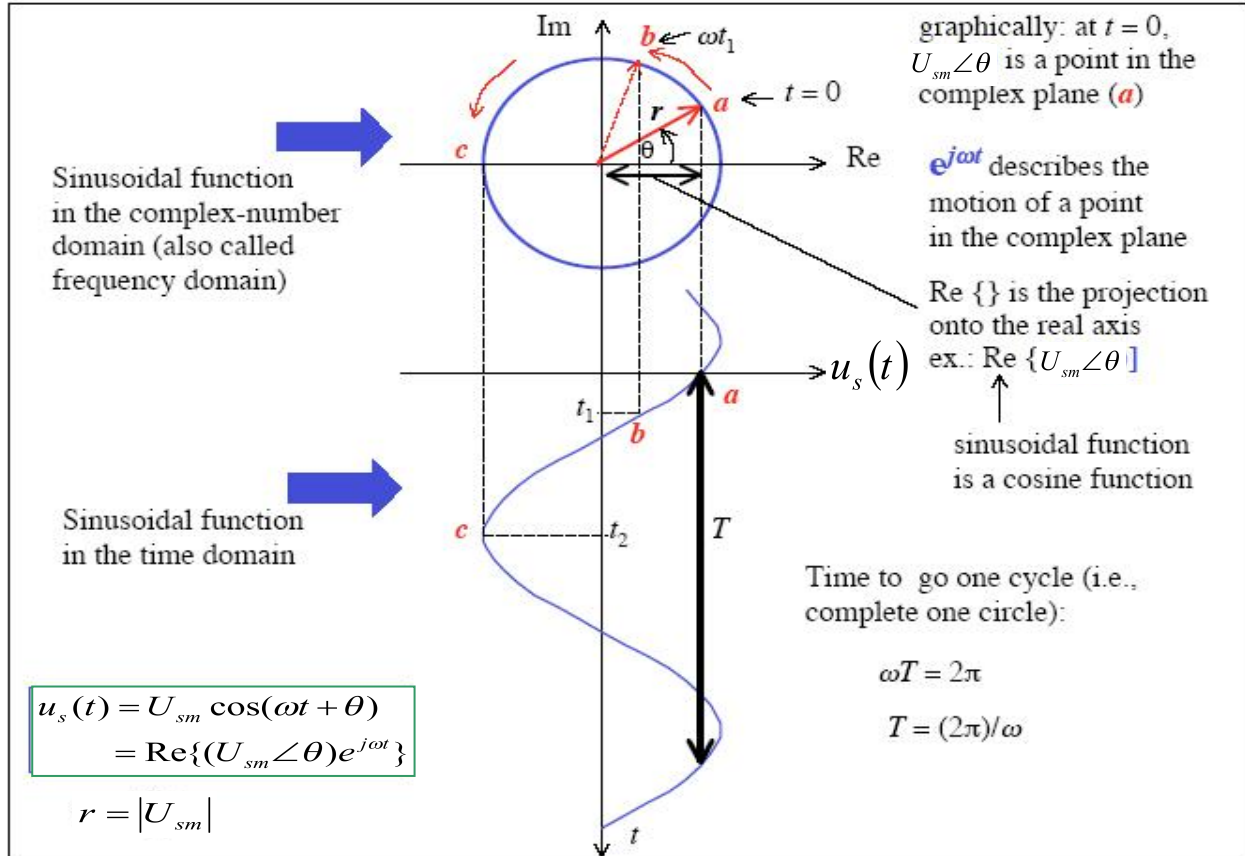

Example

Find the phasors

$$i_1 = 14.14 \cos(314t + 30^\circ) A$$

$$i_2 = -14.14 \sin(10^3 t - 60^\circ) A$$

Solution

$$\begin{aligned} i_2 &= -14.14 \cos(10^3 t - 60^\circ - 90^\circ) A \\ &= -14.14 \cos(10^3 t - 150^\circ) A \end{aligned}$$

According to the definition of phasor

$$\dot{I}_1 = \frac{14.14}{\sqrt{2}} \angle 30^\circ A = 10 \angle 30^\circ A$$

$$\dot{I}_2 = \frac{-14.14}{\sqrt{2}} \angle -150^\circ A = -10 / \underline{-150^\circ} A = 10 \angle 30^\circ A$$

Example

Find the sinusoidal quantities, $f = 50 \text{ Hz}$

$$\dot{U}_1 = 6/\underline{50^\circ} V \quad \dot{U}_2 = 3/\underline{-60^\circ} V$$

Solution

$$U_1 = 6\sqrt{2} \cos(2\pi ft + 50^\circ) = 6\sqrt{2} \cos(314t + 50^\circ) V$$

$$U_2 = 3\sqrt{2} \cos(314t - 60^\circ) V$$

9.3.3 Definition of Phasor

Phasor for sinusoidal function

$$\begin{aligned}u_s(t) &= U_{sm} \cos(\omega t + \theta) \\&= U_{sm} \operatorname{Re}\{e^{j\theta} e^{j\omega t}\}\end{aligned}$$

phasor transform (transfers the sinusoidal function from the *time domain* to the complex number or *frequency domain*).

$$\dot{U}_s = P\{U_{sm} \cos(\omega t + \theta)\} = U_{sm} e^{j\theta}$$

$$\text{or} \quad \dot{U}_s = U_{sm} \angle \theta \quad \text{or} \quad \dot{U}_s = U_{sm} \cos \theta + j U_{sm} \sin \theta$$

Inverse phasor transform (transfers the sinusoidal function from the *frequency/complex domain* to the *time domain*) (multiply by $e^{j\omega t}$ and extract the real part).

$$P^{-1}\{U_{sm} e^{j\theta}\} = U_{sm} \cos(\omega t + \theta)$$

Phasor Operation (at the same frequency)

(1) Addition and subtraction:


$$\begin{aligned}i_1 &= \sqrt{2}I_1 \cos(\omega t + \varphi_1) & i_2 &= \sqrt{2}I_2 \cos(\omega t + \varphi_2) \\i &= i_1 + i_2 = \sqrt{2}I_1 \cos(\omega t + \varphi_1) + \sqrt{2}I_2 \cos(\omega t + \varphi_2) \\&= \operatorname{Re}[\sqrt{2}\dot{I}_1 e^{j\omega t}] + \operatorname{Re}[\sqrt{2}\dot{I}_2 e^{j\omega t}] \\&= \operatorname{Re}[\sqrt{2}(\dot{I}_1 + \dot{I}_2)e^{j\omega t}]\end{aligned}$$

$$i = \operatorname{Re}[\sqrt{2}\dot{I}e^{j\omega t}]$$


$$\dot{I} = \dot{I}_1 + \dot{I}_2$$

$$\dot{i}_1 \pm \dot{i}_2 = \dot{i}_3$$
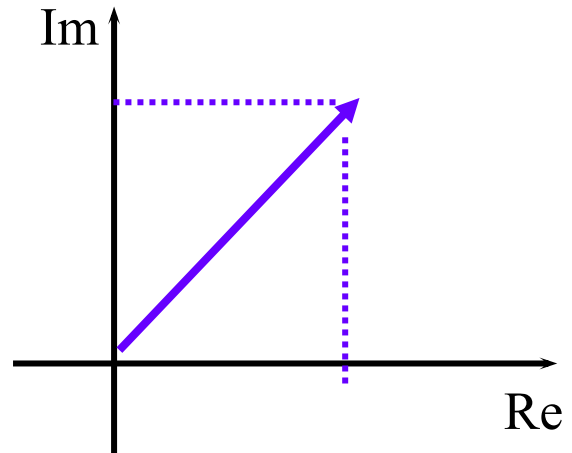
$$\begin{array}{ccc} \downarrow & \downarrow & \uparrow \\ \dot{I}_1 \pm \dot{I}_2 & = & \dot{I}_3 \end{array}$$



Example

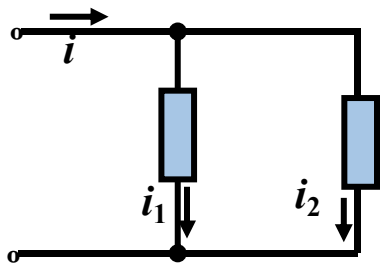

$$i_1 = 10\sqrt{2} \cos(314t - 60^\circ) A$$

$$i_2 = 22\sqrt{2} \cos(314t - 150^\circ) A$$

$$i = i_1 + i_2$$

Solution

$$\dot{I}_1 = 10/\underline{-60^\circ} A \quad \dot{I}_2 = 22/\underline{-150^\circ} A$$

$$\dot{I} = \dot{I}_1 + \dot{I}_2 = 10/\underline{-60^\circ} + 22/\underline{-150^\circ} A$$

$$= 24.16/\underline{-122.55^\circ} A$$

科学计算器

$$i = 24.16\sqrt{2} \cos(314t - 125.55^\circ) A$$

Phasor Operation (at the same frequency)

(2) Differential

$$i = \sqrt{2}I \cos(\omega t + \varphi)$$

$$\frac{di}{dt} = \frac{d}{dt}[\sqrt{2}I \cos(\omega t + \varphi)] = \frac{d}{dt}\{Re[\sqrt{2}\dot{I}e^{j\omega t}]\}$$

$$= Re\left\{\frac{d}{dt}[\sqrt{2}\dot{I}e^{j\omega t}]\right\} = Re[\sqrt{2}\dot{I} \cdot j\omega e^{j\omega t}]$$

$$= Re[\sqrt{2}(j\omega\dot{I})e^{j\omega t}]$$

$$\frac{di}{dt} \leftrightarrow j\omega\dot{I}$$

Phasor Operation (at the same frequency)

(3) Integral

$$i = \sqrt{2}I \cos(\omega t + \varphi)$$


$$\int i dt = \int \operatorname{Re}[\sqrt{2}I \cos(\omega t + \varphi)] dt = \int \operatorname{Re}[\sqrt{2}\dot{I} e^{j\omega t}] dt$$

$$= \operatorname{Re}\left[\int \sqrt{2}\dot{I} e^{j\omega t} dt\right] = \operatorname{Re}\left[\sqrt{2}\dot{I} \cdot \frac{1}{j\omega} e^{j\omega t}\right]$$

$$= \operatorname{Re}\left[\sqrt{2} \frac{\dot{I}}{j\omega} e^{j\omega t}\right]$$

$$\int i dt \leftrightarrow \frac{\dot{I}}{j\omega}$$

Conceptually:

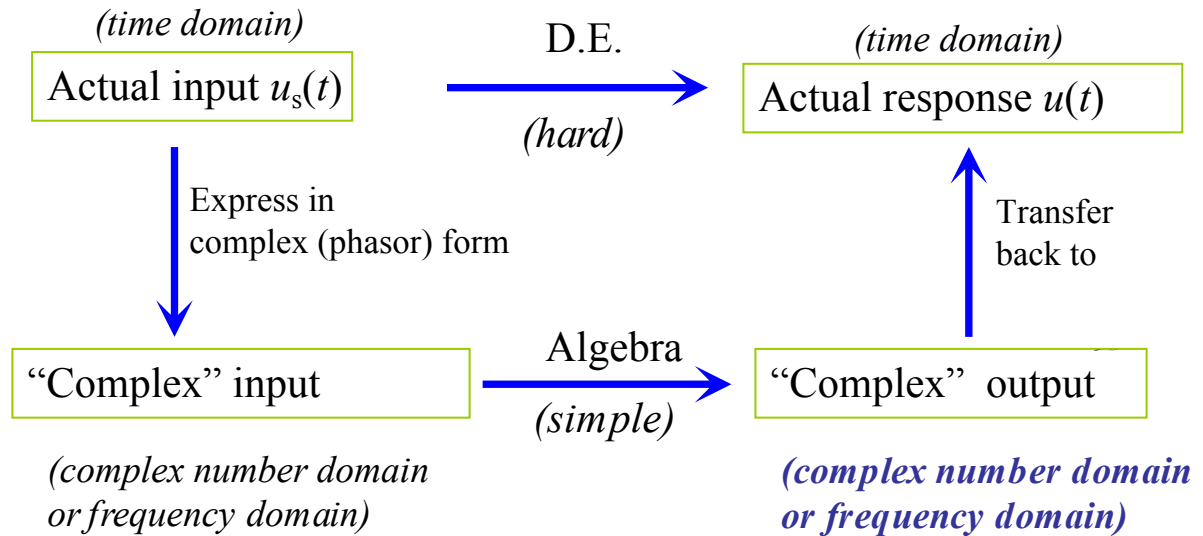

Brief summary

(1) Representation of Complex Numbers (复数)

(2) Definition of Phasor(正弦量的相量表示)

(3) Phasor Operation (at the same frequency)
(同频相量的加减、微积分运算)

$$u \quad i \quad U \quad I \quad U_m \quad I_m \quad \dot{U} \quad \dot{I}$$