

Review

(1) Instantaneous power (瞬时功率)

$$p(t) = u(t) i(t) \text{ W}$$

(2) Average power, active power (有功功率)

$$P = UI \cos \varphi = I^2 R \text{ W}$$

$\cos \varphi$: power factor (功率因数)

(3) Reactive power (无功功率)

$$Q = UI \sin \varphi = I^2 X \text{ Var}$$

(4) Complex Power (复功率)


$$\tilde{S} = P + jQ \text{ VA}$$

103

9.9.5 Apparent Power (视在功率)

$$\text{Apparent Power: } S = \sqrt{P^2 + Q^2} = UI \quad \text{Unit: VA}$$

$$S = |\tilde{S}|$$

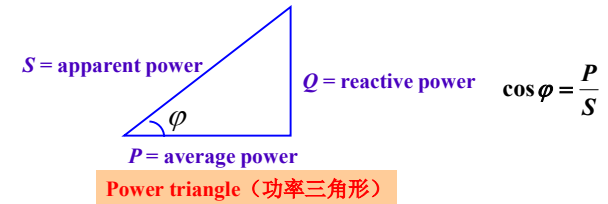

Apparent power represent the volt-amps capacity required to supply the average power. 变压器容量(100kVA, 5000kVA)

104

Transformers



10 kV, 100kVA



500 kV, 450MVA

105

Transformers




750 kV, 400MVA



1000 kV, 250MVA

106


Similar triangles

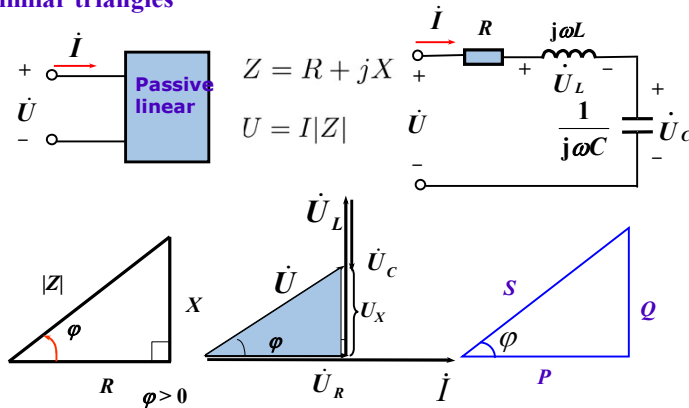

Impedance triangle, voltage triangle and power triangle are similar triangles

107

Apparatus Capacity and average power

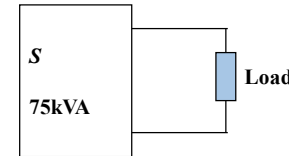

$$P = S \cos \varphi$$

$$\cos \varphi = 1, \quad P = S = 75 \text{ kW}$$

$$\cos \varphi = 0.7, \quad P = 0.7S = 52.5 \text{ kW}$$

$$\cos \varphi = 0, \quad P = 0 \text{ kW}$$

108

Example

An electrical load operates at 240V rms (effective value). The load absorbs an average power of 8kW at a lagging power factor of 0.8.

- Calculate the complex power of the load.
- Calculate the impedance of the load.

Solution: a) The load is inductive, so $\cos \varphi = 0.8$, $\sin \varphi = 0.6$, therefore

$$S = \frac{P}{\cos \varphi} = \frac{8 \text{ kW}}{0.8} = 10 \text{ kVA} \quad Q = S \sin \varphi = 6 \text{ kVAR}$$

and $\tilde{S} = 8 + j6 \text{ kVA}$

b) $P = UI \cos \varphi = 240I(0.8) = 8000W$

Solving for I $I = 41.67 \text{ A}$

$$|Z| = \frac{U}{I} = \frac{240}{41.67} = 5.76$$

$$Z = |Z| \cos \varphi + j|Z| \sin \varphi = 4.608 + j3.456 \Omega$$

109

Example 1) $u = 707 \cos 10\omega t \text{ (V)}$, $i = 1.41 \cos(\omega t - 53.1^\circ) \text{ (A)}$.

Find P , Q , S .


Solution

$$\dot{U} = \frac{707}{\sqrt{2}} \angle 0^\circ = 500V \quad i = \frac{1.414}{\sqrt{2}} \angle -53.1^\circ A$$

So $\tilde{S} = \dot{U} \dot{I}^* = 500 \angle 53.1^\circ = 300 + j400 \text{ VA}$


and $S = |\tilde{S}| = 500 \text{ VA}$

$$P = 300W \quad Q = 400 \text{ VAR}$$

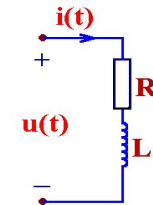

110

2) Find P , Q , S , $\cos\phi$.

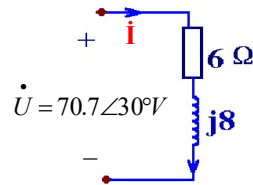

Solution

So $\dot{I} = \frac{\dot{U}}{Z} = 7.07 \angle -23.1^\circ$

$$\tilde{S} = \dot{U} \dot{I}^* = 70.7 \angle 30^\circ \times 7.07 \angle 23.1^\circ$$

$$= 500 \angle 53.1^\circ$$

$$= 300 + j400 \text{ VA}$$


and $S = |\tilde{S}| = 500 \text{ VA}$

$$P = 300 \text{ W} \quad Q = 400 \text{ VAR}$$

$$\cos\phi = \frac{P}{S} = 0.6$$

111

3) Find P , Q , S , $\cos\phi$.

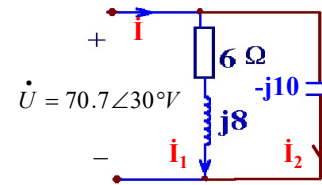

Solution

$$\dot{I}_1 = 7.07 \angle -23.1^\circ$$

$$\dot{I}_2 = 7.07 \angle 120^\circ$$

$$\dot{I} = \dot{I}_1 + \dot{I}_2 = 4.47 \angle 48.43^\circ$$

So

$$\tilde{S} = \dot{U} \dot{I}^* = 70.7 \angle 30^\circ \times 4.47 \angle -48.43^\circ$$

$$= 316 \angle -18.43^\circ \text{ VA}$$

$$= 300 - j100 \text{ VA}$$

and $S = 316 \text{ VA}$, $P = 300 \text{ W}$, $Q = -100 \text{ VAR}$,
 $\cos\phi = P/S = 300/316 = 0.949$.

112

Power Factor Correction (功率因数校正-PFC)

We need higher or lower Power Factor? Why? How?

We need higher **higher** Power Factor, but it is always low for many apparatus.


Motors: no-load $\cos\phi = 0.2 \sim 0.3$
 full-load $\cos\phi = 0.7 \sim 0.85$

Fluorescent lamps: $\cos\phi = 0.45 \sim 0.6$


Benefits: (1) Make full use of equipment capacity; (2) Reduce the current and line loss.

Most industrial loads are inductive, operate at a lagging power factor. So we need to correct the power factor by adding a **parallel capacitor**.

113

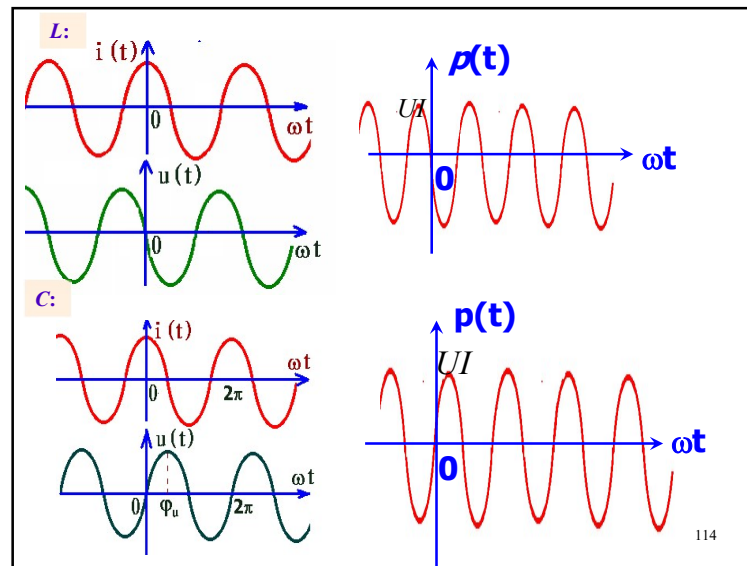

114

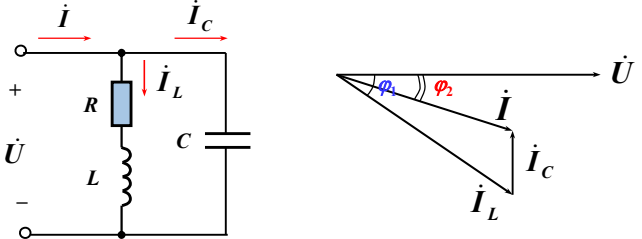

$$UI_L \cos \varphi_1 = UI \cos \varphi_2 \quad P_1 = P_2$$


$$UI_L \sin \varphi_1 > UI \sin \varphi_2 \quad Q_1 > Q_2 \quad S_1 > S_2$$

Increasing C reactive compensation (无功补偿)

- under-compensation (欠补偿) ✓
- full-compensation (全补偿)
- over-compensation (过补偿)

Appropriate value for power factor ~ 0.9.

115

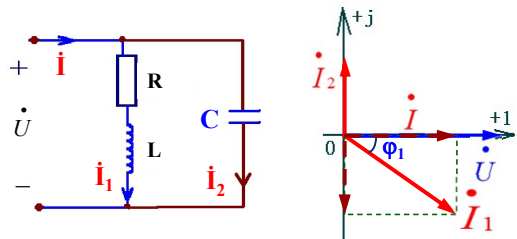

P and U are known. To improve the power factor from $\cos \varphi_1$ to $\cos \varphi_2$, find C.

Before C is connected to the circuit:

$$Q_L = P \tan \varphi_1$$

After C is connected to the circuit:


$$Q = P \tan \varphi_2 \quad Q = Q_L - Q_C \quad Q_C = U^2 \omega C$$

Thus

$$P \tan \varphi_2 = P \tan \varphi_1 - U^2 \omega C \quad C = \frac{P}{\omega U^2} (\tan \varphi_1 - \tan \varphi_2)$$

116

Example: $f=50\text{Hz}$, $U=380\text{V}$, $P=20\text{kW}$, $\cos \varphi_1=0.6$ (lagging). Find C, if the power factor is to be improved to 0.9.

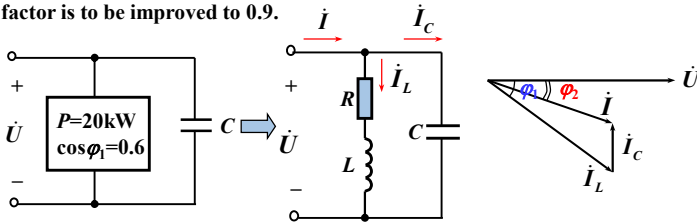

Solution 1

由 $\cos \varphi_1 = 0.6$ 得 $\varphi_1 = 53.13^\circ$

由 $\cos \varphi_2 = 0.9$ 得 $\varphi_2 = 25.84^\circ$

$$I_C = I_L \sin \varphi_1 - I \sin \varphi_2$$


$$I_L = \frac{P}{U \cos \varphi_1} = \frac{20 \times 10^3}{380 \times 0.6} = 87.72$$

117

$$I = \frac{P}{U \cos \varphi} = \frac{20 \times 10^3}{380 \times 0.9} = 58.48$$

$$I_C = I_L \sin \varphi_1 - I \sin \varphi_2 = 44.69 \quad C = \frac{I_C}{\omega U} = 375 \mu\text{F}$$

Solution 2: By using the power triangle

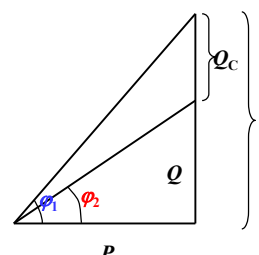

$$|Q_C| = |Q_L - Q| = P(\tan \varphi_1 - \tan \varphi_2)$$

$$|Q_C| = \omega C U^2$$

$$\therefore C = \frac{P}{\omega U^2} (\tan \varphi_1 - \tan \varphi_2)$$

$$C = \frac{20 \times 10^3}{314 \times 380^2} (\tan 53.13^\circ - \tan 25.84^\circ) = 375 \mu\text{F}$$

118

Conservation of AC power (功率的守恒)

Notice: $\tilde{S} = \tilde{S}_1 + \tilde{S}_2 + \tilde{S}_3 + \dots$
 $= \dot{U}_1 \dot{I}_1^* + \dot{U}_2 \dot{I}_2^* + \dot{U}_3 \dot{I}_3^* + \dots$

$Q = Q1 + Q2 + Q3 \dots\dots\dots$

$P = P1 + P2 + P3 \dots\dots\dots$

but $S \neq S1 + S2 + S3 \dots\dots\dots$

119


Brief summary

- (1) Instantaneous power (瞬时功率)
- (2) Average power, active power (有功功率)
- (3) Reactive power (无功功率)
- (4) Complex Power (复功率)
- (5) Apparent Power (视在功率)
- (6) Power Factor Correction (功率因数的提高)
- (7) Maximum power transfer (最大功率传输)

120


Example 10. Illustrate that when ω changes from 0 to ∞ , $U_2 = U_1$, ϕ_2 changes from $180^\circ + \phi_1$ to ϕ_1 .

Solution 1. Assume

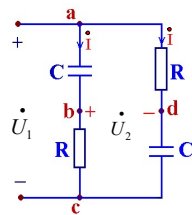

$\dot{U}_1 = U_1 \angle 0^\circ$

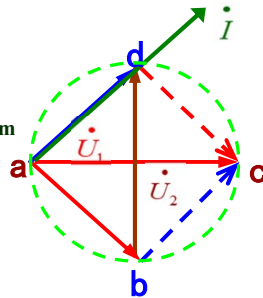When ω changes from 0 to ∞ , the track of d and b is a circle and bd is the diameter, $U_{bd} = U_2 = U_1$



121


Solution 2. Assume

$$\dot{U}_2 = \frac{R}{R + \frac{1}{j\omega C}} \dot{U}_1 - \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \dot{U}_1$$

$$\dot{U}_1 = U_1 \angle \phi_1, \dot{U}_2 = U_2 \angle \phi_2 = \frac{j\omega CR - 1}{j\omega CR + 1} \dot{U}_1$$

$$= \frac{R - \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \dot{U}_1 \therefore \dot{U}_2 = \dot{U}_1 \angle (180^\circ - 2 \arctan CR\omega)$$
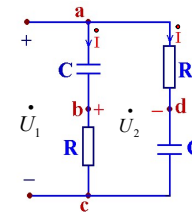
$$= U_1 \angle (\phi_1 + 180^\circ - 2 \arctan CR\omega)$$



122

Exercise 1. $U=100V$,

$$U_c = 100 \sqrt{3}V, X_c = 100 \sqrt{3}\Omega,$$

$$\varphi_Z = 60^\circ \quad \text{Find } Z.$$

Solution

$$I = \frac{U_c}{X_c} = 1A \quad \dot{I} = 1 \angle 0^\circ$$

$$Z = R + jX$$

$$\dot{U} = (-j100\sqrt{3} + R + jX) \cdot 1 \angle 0^\circ = R + j(X - 100\sqrt{3})$$

$$\therefore 100^2 = R^2 + (X - 100\sqrt{3})^2 \quad \therefore R = \begin{cases} 100\Omega \\ 50\Omega \end{cases}$$

$$\frac{X}{R} = \tan 60^\circ = 1.732 \quad X = \begin{cases} 173.2\Omega \\ 86.6\Omega \end{cases}$$

$$Z = \begin{cases} 100 + j173.2\Omega \\ 50 + j86.6\Omega \end{cases}$$

123

Exercise 2. Find the relationship of L 、 C 、 ω , to make I constant when R changes.????


$$\text{If } R=0: \quad \dot{I} = j(\omega C - \frac{1}{\omega L}) \dot{U}$$

$$\text{If } R=\infty: \quad \dot{I} = j\omega C \dot{U}$$

$$\left| \omega C - \frac{1}{\omega L} \right| = \omega C$$


$$\frac{1}{\omega L} - \omega C = \omega C \quad \therefore \omega = \sqrt{\frac{1}{2LC}}$$
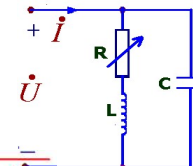
$$\omega C - \frac{1}{\omega L} = \omega C \quad (\text{No solution})$$



124

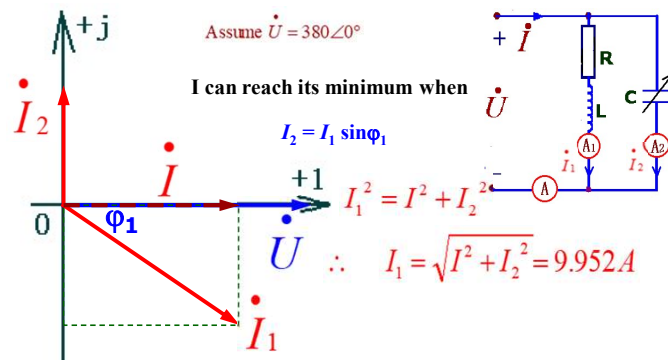Exercise 3. $U=380V$, $f=50Hz$. The minimum reading of the current meter A is $2.59A$ when $C=80.85 \mu F$. Find the reading of current meter A1 and A2.



125

Summary

- (1) amplitude, angular frequency, initial phase angle; Phase angle difference; Root mean square, RMS;
- (2) Definition of Phasor;
- (3) Passive circuit elements in the frequency domain; impedance;
- (4) Sinusoidal steady-state analysis; Phasor diagrams
- (5) AC circuit power analysis

126

What's next?

- (1) Frequency characteristics; Resonance
- (2) Magnetically coupled circuits; Transformers
- (3) Three-Phase circuits;
- (4) Periodic, nonsinusoidal excitations

127

正误判断

在电阻电路中：

$$I \neq \frac{U}{R} \quad i \neq \frac{U}{R} \quad i \neq \frac{u}{R}$$

瞬时值 有效值

128

正误判断

在电感电路中：

$$i \neq \frac{u}{X_L} \quad i \neq \frac{u}{\omega L}$$

$$I \neq \frac{U}{\omega L}$$

$$\frac{U}{I} \neq j\omega L \quad \frac{\dot{U}}{\dot{I}} \neq X_L$$


129

正误判断

在R-L-C串联电路中

$$U \neq U_R + U_L + U_C = IR + I(X_L - X_C)$$

因为交流物理量除有效值外还有相位。

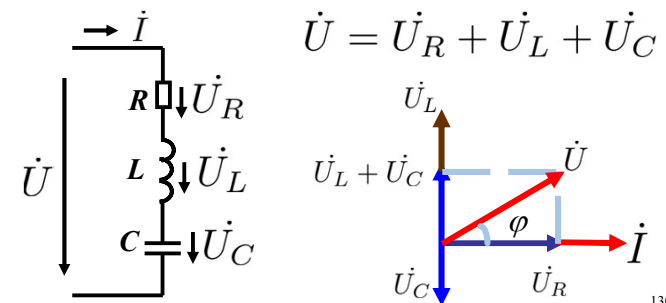

130


正误判断

$$\dot{U} \nRightarrow \dot{I} Z$$

\dot{U}, \dot{I} 反映的是正弦电压或电流，
而复数阻抗只是一个运算符号。 Z 不能加 “•”

131

正误判断 在 $R-L-C$ 正弦交流电路中

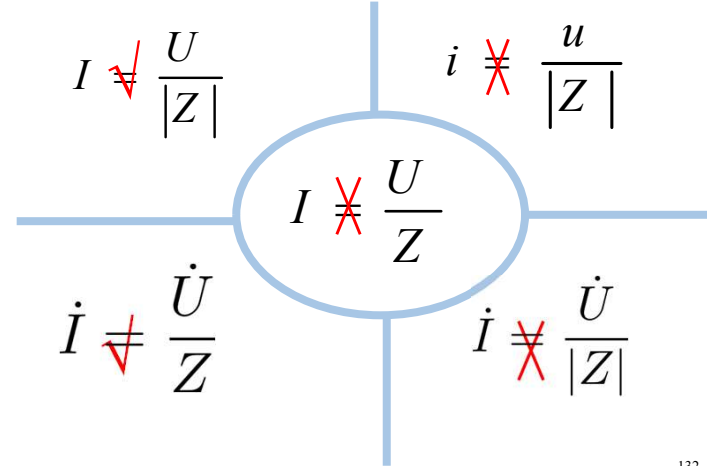

132

正误判断

在 $R-L-C$ 串联电路中，假设 $\dot{I} = I \angle 0^\circ$

$$U \nRightarrow \sqrt{U_R^2 + U_L^2 + U_C^2}$$

$$U \checkmark I \sqrt{R^2 + (X_L - X_C)^2}$$

$$\dot{U} \checkmark \dot{I} [R + j(X_L - X_C)]$$

133

正误判断 在 $R-L-C$ 串联电路中，假设 $\dot{I} = I \angle 0^\circ$

$$\varphi \checkmark \text{tg}^{-1} \frac{X_L - X_C}{R}$$

$$\varphi \nRightarrow \text{tg}^{-1} \frac{U_L - U_C}{U}$$

$$\varphi \checkmark \text{tg}^{-1} \frac{U_L - U_C}{U_R}$$

$$\varphi \nRightarrow \text{tg}^{-1} \frac{\omega L - \omega C}{R}$$

134