

Electric Circuits

$$v_M = \frac{\frac{u_o}{R_4}}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

$$i_2 = \frac{-v_M}{R_2} = i_1 = \frac{u_i}{R_1}$$


$$A_u = \frac{u_o}{u_i} = -\frac{R_2(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4})}{\frac{R_1}{R_4}} = -\frac{R_2(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4})}{\frac{R_1}{R_4}}$$

$$= -\frac{R_2}{R_1}(\frac{R_4}{R_2} + \frac{R_4}{R_3} + 1)$$

该放大电路，在放大倍数较大时，可避免使用大电阻。但 $R_3$ 的存在，削弱了负反馈。

## 5.5 Noninverting Amplifier

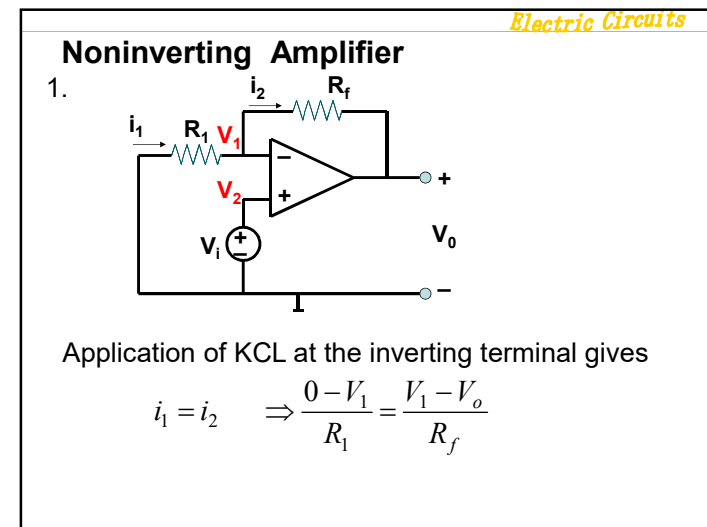1. The figure and property
2. A voltage follower





But  $V_1=V_2=V_i$ . Equation (1) becomes

$$\frac{-V_i}{R_1} = \frac{V_i - V_o}{R_f}$$


$$\therefore V_o = \left(1 + \frac{R_f}{R_1}\right) V_i$$

A noninverting amplifier is an op amp circuit designed to provide **a positive voltage gain**.

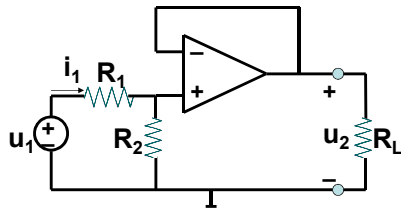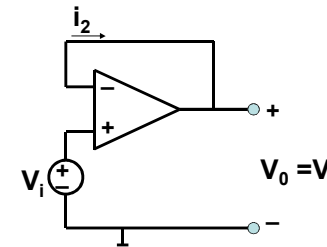2. If feedback resistor  $R_f=0$  (short circuit) or  $R_1=\infty$  (open circuit) or both, the gain becomes 1. Under these conditions ( $R_f=0$  and  $R_1=\infty$ ), the circuit is called **a voltage follower** (or **unity gain amplifier**) because the output follows the input.



$$u_2 = \frac{R_2}{R_1 + R_2} u_1$$

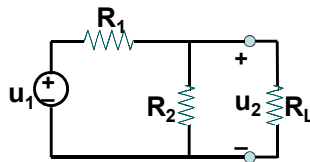


## 5.6 Summing Amplifier

----- The figure and property
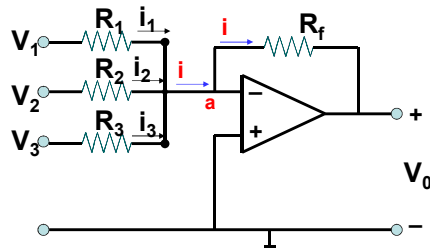
### Summing Amplifier

A summing amplifier is an op amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs.



Applying KCL at node a gives  $i = i_1 + i_2 + i_3$

$$\text{But } \frac{V_a - V_o}{R_f} = \frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} + \frac{V_3 - V_a}{R_3}$$

We note that  $V_a = 0$ , and we get

$$\frac{-V_o}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$V_o = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

If we assume  $R_1 = R_2 = R_3 = R_f$


$$V_o = -(V_1 + V_2 + V_3)$$

## 5.7 Difference Amplifier

1. The figure and property
2. Applications
  - (a) Integrator
  - (b) Differentiator
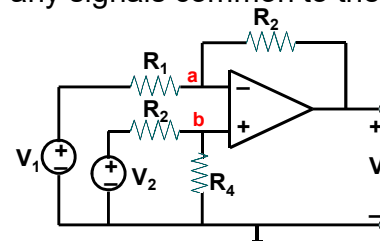
### Difference Amplifier

A difference amplifier is a device that amplifies the difference between two inputs but rejects any signals common to the two inputs.



Applying KCL to node a,  $\frac{V_1 - V_a}{R_1} = \frac{V_a - V_o}{R_2}$

$$\text{or } V_o = \left(\frac{R_2}{R_1} + 1\right)V_a - \frac{R_2}{R_1}V_1 \quad (1)$$

Applying KCL to node b,  $\frac{V_2 - V_b}{R_3} = \frac{V_b - 0}{R_4}$

$$\text{or } V_b = \frac{R_4}{R_3 + R_4}V_2 \quad (2)$$

But  $V_a = V_b$ . Substituting Eq.(2) into Eq.(1) yields

$$V_o = \left(\frac{R_2}{R_1} + 1\right)\frac{R_4}{R_3 + R_4}V_2 - \frac{R_2}{R_1}V_1$$

or

$$V_o = \frac{R_2}{R_1} \cdot \frac{1 + \frac{R_1}{R_2}}{1 + \frac{R_3}{R_4}}V_2 - \frac{R_2}{R_1}V_1$$


Since a difference amplifier must reject a signal common to the two inputs, the amplifier must have the property that  $V_o = 0$  when  $V_1 = V_2$ . This property exists when  $R_1/R_2 = R_3/R_4$ .

$$\therefore V_o = \frac{R_2}{R_1}(V_2 - V_1)$$

If  $R_2 = R_1$  and  $R_3 = R_4$ , the difference amplifier becomes a subtractor, with the output


$$V_o = V_2 - V_1$$

### Integrator 积分器

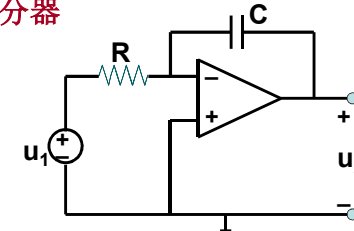

$$\frac{u_1}{R} + C \frac{du_2}{dt} = 0 \Rightarrow \frac{du_2}{dt} = -\frac{1}{RC}u_1$$

$$\Rightarrow u_2 = -\frac{1}{RC} \int_{-\infty}^t u_1 dt$$

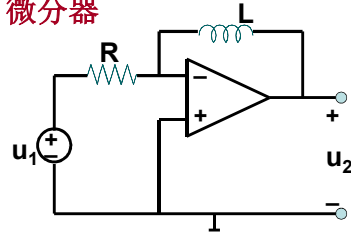**Differentiator 微分器**

$$\frac{u_1}{R} + \frac{1}{L} \int_{-\infty}^t u_2 dt = 0 \quad \text{or} \quad u_2 = -\frac{L}{R} \frac{du_1}{dt}$$