

Fundamentals of Electric Circuits 2020.11



Chapter 15 The Laplace Transform

CHAPTER 15 THE LAPLACE TRANSFORM

The Laplace transform is significant:

1. It can be applied to a *wider variety of inputs*.
2. It provides an easy way to solve circuit problems *involving initial conditions*.
3. It can provide us the complete response *comprising both the natural and forced responses*.

A very useful tool !

CHAPTER 15 THE LAPLACE TRANSFORM

15.1 Definition of the Laplace Transform

15.2 Property of the Laplace Transform

15.3 The Inverse Laplace Transform

15.4 Application to Circuits

15.1 Definition of the Laplace Transform

Given a function $f(t)$, its Laplace transformation, denoted by $F(s)$, is given by

$$F(s) = \int_{0^-}^{+\infty} f(t)e^{-st} dt$$

$$= \int_{0^-}^{0^+} f(t)e^{-st} dt + \int_{0^+}^{+\infty} f(t)e^{-st} dt$$

Where s is a complex variable given by $s = \sigma + j\omega$

1. One_sided Laplace Transform

$$\begin{cases} F(s) = \int_{0^-}^{+\infty} f(t)e^{-st} dt & \text{the direct Laplace transform} \\ f(t) = \frac{1}{2\pi j} \int_{\sigma-j\infty}^{\sigma+j\infty} F(s)e^{st} ds & \text{the inverse Laplace transform} \end{cases}$$

2. Convergence criterion:

$$\int_{0^-}^{\infty} |f(t)e^{-st}| dt < \infty \quad \int_{0^-}^{\infty} |f(t)e^{-\sigma t}| dt < \infty$$

3. A Laplace transform pair:

$$f(t) \longleftrightarrow F(s) \quad \boxed{F(s) = L[f(t)]}$$

4. The Laplace Transform of some typical functions:

$$F(s) = \int_{0^-}^{+\infty} f(t)e^{-st} dt$$

(1) The exponential function(指数函数):

$$L[e^{-at}1(t)] = \int_{0^-}^{\infty} e^{-at}e^{-st} dt = -\frac{1}{s+a} e^{-(s+a)t} \Big|_0^{\infty} = \frac{1}{s+a}$$

(2) The unit step function(单位阶跃函数):

$$L[1(t)] = \int_{0^-}^{\infty} 1(t)e^{-st} dt = \int_{0^+}^{\infty} e^{-st} dt = -\frac{1}{s} e^{-st} \Big|_0^{\infty} = \frac{1}{s}$$

当 $a=0$ 时 $e^{-at}1(t) = 1(t)$

(3) The impulse function(冲激函数):

$$L[\delta(t)] = \int_{0^-}^{\infty} \delta(t)e^{-st} dt = \int_{0^-}^{0^+} \delta(t)e^{-s0} dt = 1$$

15.2 Properties of The Laplace Transform:

1. Linearity:

$$F(S) = \int_0^{\infty} f(t)e^{-st} dt$$

$$\text{if } \mathcal{L}[f_1(t)] = F_1(S), \mathcal{L}[f_2(t)] = F_2(S)$$

$$\text{then } \mathcal{L}[af_1(t) \pm bf_2(t)] = aF_1(S) \pm bF_2(S)$$

$$\text{example1: } \mathcal{L}[U_1(t)] = \frac{U}{S}$$

$$\begin{aligned} \text{example2: } \mathcal{L}[\sin \omega t] &= \mathcal{L}\left[\frac{1}{2j}(e^{j\omega t} - e^{-j\omega t})\right] \\ &= \frac{1}{2j} \left[\frac{1}{S - j\omega} - \frac{1}{S + j\omega} \right] = \frac{\omega}{S^2 + \omega^2} \end{aligned}$$

*Kirchhoff's laws in s domain:

$$KCL \quad \sum i = 0$$

$$\sum I(S) = 0$$

$$KVL \quad \sum u = 0$$

$$\sum U(S) = 0$$

*Circuit elements in s domain:

$$\begin{array}{lcl} R: & \begin{array}{c} i \\ \xrightarrow{\quad} \boxed{R} \\ + \quad u \quad - \end{array} & \begin{array}{l} u = Ri \\ U(S) = RI(S) \\ I(S) = GU(S) \end{array} \end{array}$$

$$\begin{array}{lcl} & \begin{array}{c} I(S) \\ \xrightarrow{\quad} \boxed{R} \\ + \quad U(S) \quad - \end{array} & \begin{array}{l} Z(s) = R \\ Y(s) = G \end{array} \end{array}$$

2. scaling:

$$F(S) = \int_0^{\infty} f(t)e^{-st} dt$$

$$\mathcal{L}[f(at)] = \frac{1}{a} F\left(\frac{s}{a}\right)$$

Example:

$$\mathcal{L}[\sin \omega t] = \frac{\omega}{s^2 + \omega^2}$$

$$\mathcal{L}[\sin 2\omega t] = \frac{1}{2} \frac{\omega}{\left(\frac{s}{2}\right)^2 + \omega^2}$$

3. Differentiation

$$\text{If } \mathcal{L}[f(t)] = F(s)$$

$$(1) \text{ Time Differentiation } \mathcal{L}\left[\frac{df(t)}{dt}\right] = sF(s) - f(0^-)$$

$$\begin{aligned} \text{example1: } \mathcal{L}[\cos \omega t] &= \mathcal{L}\left[\frac{1}{\omega} \frac{d}{dt}(\sin \omega t)\right] \\ &= \frac{s}{\omega} \frac{\omega}{s^2 + \omega^2} - 0 = \frac{s}{s^2 + \omega^2} \end{aligned}$$

$$\text{example2: } \mathcal{L}[\delta(t)] = \mathcal{L}\left[\frac{d}{dt}1(t)\right] = s \frac{1}{s} = 1$$

$$\mathcal{L}\left[\frac{df(t)}{dt}\right] = sF(s) - f(0^-)$$

$$\begin{aligned} \mathcal{L}\left[\frac{d^2 f(t)}{dt^2}\right] &= s[sF(s) - f(0^-)] - f'(0^-) \\ &= s^2 F(s) - sf(0^-) - f'(0^-) \end{aligned}$$

$$\mathcal{L}\left[\frac{d^n f(t)}{dt^n}\right] = s^n F(s) - s^{n-1} f(0^-) - \dots - f^{(n-1)}(0^-)$$

L:

$$\begin{array}{c} i \\ \xrightarrow{\quad} \boxed{L} \\ + \quad u \quad - \end{array}$$

$$u = L \frac{di}{dt}$$


$$\begin{array}{c} I(s) \xrightarrow{\quad} \boxed{sL} \quad \boxed{Li(0^-)} \\ + \quad U(s) \quad - \end{array}$$

$$\begin{aligned} U(S) &= L(SI(S) - i(0^-)) \\ &= SLI(S) - Li(0^-) \end{aligned}$$

$$\begin{array}{c} \boxed{sL} \\ \uparrow \quad \downarrow \\ I(s) \quad \boxed{i(0^-)/s} \\ + \quad U(s) \quad - \end{array}$$

$$I(S) = \frac{U(S)}{sL} + \frac{i(0^-)}{s}$$
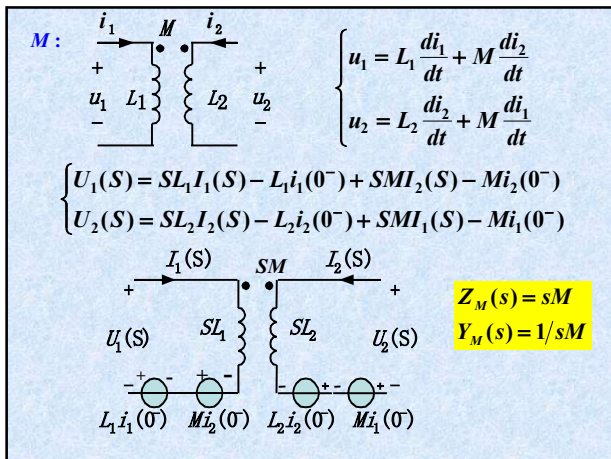
$$\begin{array}{l} Z(s) = sL \\ Y(s) = 1/sL \end{array}$$



(2). Frequency Differentiation:

$$\text{If } L[f(t)] = F(S)$$

$$L[-t f(t)] = \frac{dF(S)}{dS}$$

$$1: L[t f(t)] = -\frac{d}{dS} \left(\frac{1}{S} \right) = \left(\frac{1}{S^2} \right)$$

$$2: L[t^n f(t)] = (-1)^n \frac{d^n}{dS^n} \left(\frac{1}{S} \right) = \left(\frac{n!}{S^{n+1}} \right)$$

$$3: L[t e^{-\alpha t}] = -\frac{d}{dS} \left(\frac{1}{S + \alpha} \right) = \frac{1}{(S + \alpha)^2}$$

4. Integration:

(1) Time Integration:

$$\text{if } L[f(t)] = F(S)$$

$$L\left[\int_0^t f(\tau) d\tau\right] = \frac{1}{S} F(S)$$

$$\text{example1: } L[t f(t)] = L\left[\int_0^t 1(\tau) d\tau\right] = \frac{1}{S} \times \frac{1}{S}$$

$$\text{example2: } L[t^2 f(t)] = \frac{2}{S^3} \quad \because [t^2 f(t)] = 2 \int_0^t \tau f(\tau) d\tau$$

C:

$$u_c = u_c(0^-) + \frac{1}{C} \int_0^t i_c dt$$

$$U_c(S) = \frac{1}{sC} I_c(S) + \frac{u_c(0^-)}{S}$$

$$I_c(S) = sC U_c(S) - C u_c(0^-)$$

$$Z(s) = 1/sC$$

$$Y(s) = sC$$

4. Shift

(1). Frequency shift

$$\text{if: } L[f(t)] = F(S)$$

$$L[e^{-\alpha t} f(t)] = F(S + \alpha) \quad F(S + \alpha) = L[e^{-\alpha t} f(t)]$$

$$1: L[t e^{-\alpha t} f(t)] = \frac{1}{(S + \alpha)^2} \quad L[t f(t)] = \frac{1}{S^2}$$


$$L[\cos \omega t] = \frac{s}{s^2 + \omega^2}$$

$$2: L[e^{-\alpha t} \cos \omega t f(t)] = \frac{S + \alpha}{(S + \alpha)^2 + \omega^2}$$



4. Shift

$$\text{设: } L[f(t)] = F(S)$$


(2). Time shift (延迟定理)

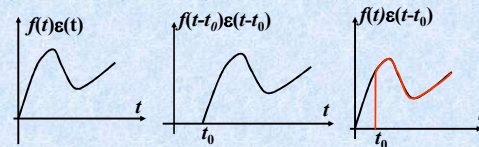

$$L[f(t - t_0) \epsilon(t - t_0)] = e^{-st_0} F(S)$$

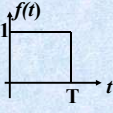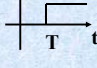e.g 1:  $f(t) = \varepsilon(t) - \varepsilon(t - T)$ 

$$F(S) = \frac{1}{S} - \frac{1}{S} e^{-ST}$$

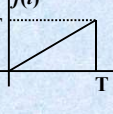e.g 2:  $f(t) = t[\varepsilon(t) - \varepsilon(t - T)]$


$$F(S) = \frac{1}{S^2} - \frac{e^{-ST}}{S^2}$$

$$f(t) = t\varepsilon(t) - (t - T)\varepsilon(t - T) - T\varepsilon(t - T)$$

$$F(S) = \frac{1}{S^2} - \frac{1}{S^2} e^{-ST} - \frac{T}{S} e^{-ST}$$

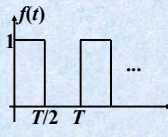5. Time periodicity

If $f(t)$ ($f_1(t) \in (0, T)$) is a periodic function



$$L[f_1(t)] = F_1(S)$$

then: $L[f(t)] = \frac{1}{1 - e^{-ST}} F_1(S)$

证: $f(t) = f_1(t) + f_1(t - T)\varepsilon(t - T) + f_1(t - 2T)\varepsilon(t - 2T) + \dots$

$$L[f(t)] = F_1(S) + e^{-ST} F_1(S) + e^{-2ST} F_1(S) + \dots$$

$$= F_1(S)[e^{-ST} + e^{-2ST} + e^{-3ST} + \dots]$$

$$= \frac{1}{1 - e^{-ST}} F_1(S)$$

6. Initial and Final Values:

Initial_value theorem:

$f(t)$ 在 $t = 0$ 处无冲激则

$$f(0^+) = \lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} sF(S)$$

Final_value theorem:


$\lim_{t \rightarrow \infty} f(t)$ 存在时

$$\lim_{s \rightarrow 0} sF(S) = \lim_{t \rightarrow \infty} f(t) = f(\infty)$$

Example.1: Given $F(S) = \frac{3S^2 + 4S + 5}{S(S^2 + 2S + 3)}$, Find $f(0^+)$

$$f(0^+) = \lim_{s \rightarrow \infty} \frac{3S^2 + 4S + 5}{(S^2 + 2S + 3)} = 3$$

$$f(0^+) = \lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} sF(S)$$

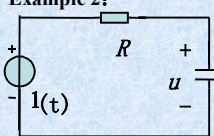Example 2: 

$u_c(0^-) = 0$

$$RC \frac{du}{dt} + u = 1(t)$$

$$SRCU(S) + U(S) = \frac{1}{S}$$

$$U(S) = \frac{1}{S(1 + SRC)}$$

Then:

$$u(0^+) = \lim_{s \rightarrow \infty} s \frac{1}{S(1 + SRC)} = \lim_{s \rightarrow \infty} \frac{1}{(1 + SRC)} = 0$$

$$u(\infty) = \lim_{s \rightarrow 0} \frac{1}{(1 + SRC)} = 1$$

15.3. The Inverse Laplace Transform

Given $F(s)$, how to obtain the corresponding $f(t)$:

(1) The inverse Laplace transform

$$f(t) = \frac{1}{2\pi j} \int_{\sigma - j\infty}^{\sigma + j\infty} F(S) e^{st} ds$$

(2) Matching entries in Table 15.2:

$$F(S) = F_1(S) + F_2(S) + \dots + F_n(S)$$

$$f(t) = f_1(t) + f_2(t) + \dots + f_n(t)$$

(3) Partial fraction expansion to break $F(s)$ down into simple terms whose inverse transform can be got from Table 15.2

$$F(S) = \frac{F_1(S)}{F_2(S)} = \frac{a_0 S^m + a_1 S^{m-1} + \dots + a_m}{b_0 S^n + b_1 S^{n-1} + \dots + b_n} \quad (n > m)$$

1. Simple poles:

1. $F_2(S)=0$ 的根为不等实根 $S_1 \dots S_n$

Use partial fraction expansion to decompose $F(s)$:

$$(S-S_1)F(S) = \frac{(S-S_1)k_1}{S-S_1} + \frac{(S-S_1)k_2}{S-S_2} + \dots + \frac{(S-S_1)k_n}{S-S_n}$$

$$f(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t} + \dots + k_n e^{s_n t}$$

$$k_1 = (S-S_1)F(S) \Big|_{S=S_1}$$

$$k_2 = (S-S_2)F(S) \Big|_{S=S_2}$$

$$\dots k_n = (S-S_n)F(S) \Big|_{S=S_n}$$

$$\text{例: } F(S) = \frac{4S+5}{S^2+5S+6} = \frac{4S+5}{(S+2)(S+3)} = \frac{K_1}{S+2} + \frac{K_2}{S+3}$$

$$S_1 = -2, S_2 = -3$$

$$K_1 = \frac{4S+5}{S+3} \Big|_{S=-2} = -3 \quad K_2 = \frac{4S+5}{S+2} \Big|_{S=-3} = 7$$

$$f(t) = -3e^{-2t}\varepsilon(t) + 7e^{-3t}\varepsilon(t)$$

$$k_i = \lim_{s \rightarrow s_i} \frac{F_1(S)(S-S_i)}{F_2(S)}$$

(洛比达法则)

$$= \lim_{s \rightarrow s_i} \frac{F_1'(S)(S-S_i) + F_1(S)}{F_2'(S)} = \frac{F_1(S_i)}{F_2'(S_i)} \quad k_i = \frac{F_1(S_i)}{F_2'(S_i)}$$

(分解定理)

上例:

$$F(S) = \frac{4S+5}{S^2+5S+6} \quad \left\{ \begin{array}{l} k_1 = \frac{4S+5}{S+2} \Big|_{S=-2} = -3 \\ k_2 = \frac{4S+5}{S+3} \Big|_{S=-3} = 7 \end{array} \right.$$

2. Complex poles:

2. $F_2(S)$ 有共轭复根

一对共轭复根为 $S_{1,2} = -\alpha \pm j\omega$

$$F(S) = \frac{F_1(S)}{F_2(S)} = \frac{F_1(S)}{|S - (-\alpha + j\omega)||S - (-\alpha - j\omega)|}$$

$$= \frac{k_1}{S + \alpha - j\omega} + \frac{k_2}{S + \alpha + j\omega}$$

k_1, k_2 也是一对共轭复根 设 $k_1 = |k| \angle \theta$ $k_2 = |k| \angle -\theta$

$$f(t) = (|k|e^{j\theta}e^{-(\alpha-j\omega)t} + |k|e^{-j\theta}e^{-(\alpha+j\omega)t})\varepsilon(t)$$

$$= |k|e^{-\alpha t}[e^{j(\omega t + \theta)} + e^{-j(\omega t + \theta)}]\varepsilon(t)$$

$$= 2|k|e^{-\alpha t}\cos(\omega t + \theta)\varepsilon(t)$$

$$\text{例: } F(S) = \frac{S}{S^2+2S+5} \quad S = -1 \pm j2$$

$$k_1 = \frac{S}{S - (-1 - j2)} \Big|_{S=-1+j2} = 0.559 \angle 26.6^\circ$$

$$k_2 = \frac{S}{S - (-1 + j2)} \Big|_{S=-1-j2} = 0.559 \angle -26.6^\circ$$

$$f(t) = 2 \times 0.559 e^{-t} \cos(2t + 26.6^\circ) \varepsilon(t)$$

$$= 1.118 e^{-t} \cos(2t + 26.6^\circ) \varepsilon(t)$$

method2: completing the square(配方)

$$L[\sin \omega t \varepsilon(t)] = \frac{\omega}{S^2 + \omega^2}$$

$$\frac{S}{S^2+2S+5} = \frac{S+1-1}{(S+1)^2+2^2} = \frac{S+1}{(S+1)^2+2^2} - \frac{1}{(S+1)^2+2^2}$$

$$f(t) = e^{-t} \cos 2t - \frac{1}{2} e^{-t} \sin 2t = 1.118 e^{-t} \cos(2t + 26.6^\circ) \varepsilon(t)$$

3. Repeated poles:

3. $F_2(S)$ 有相等的实根 (重根)

$$F(S) = \frac{a_0 S^m + a_1 S^{m-1} + \dots + a_m}{(S-S_1)^n}$$

$$F(S) = \frac{k_{11}}{S-S_1} + \frac{k_{12}}{(S-S_1)^2} + \dots + \frac{k_{1n-1}}{(S-S_1)^{n-1}} + \frac{k_{1n}}{(S-S_1)^n}$$

$$k_{1n} = [(S-S_1)^n F(S)] \Big|_{S=S_1}$$

$$k_{1n-1} = \frac{d}{ds} [(S-S_1)^n F(S)] \Big|_{S=S_1}$$

$$k_{1n-2} = \frac{1}{2!} \times \frac{d^2}{ds^2} [(S-S_1)^n F(S)] \Big|_{S=S_1}$$

⋮

$$k_{11} = \frac{1}{(n-1)!} \times \frac{d^{n-1}}{ds^{n-1}} [(S-S_1)^n F(S)] \Big|_{S=S_1}$$

$$\text{例: } \frac{S+4}{S(S+1)^2} = \frac{K_1}{S} + \frac{K_{21}}{S+1} + \frac{K_{22}}{(S+1)^2} \quad \text{频域延迟}$$

$$K_1 = \frac{S+4}{(S+1)^2} \Big|_{S=0} = 4 \quad K_{22} = \frac{S+4}{S} \Big|_{S=-1} = -3$$

$$K_{21} = \frac{d}{ds} [(S+1)^2 F(S)] \Big|_{S=-1} = \frac{d}{ds} \left[\frac{S+4}{S} \right] \Big|_{S=-1} = -4$$

$$f(t) = 4 - 4e^{-t} - 3te^{-t}$$

小结: 由 $F(S)$ 求 $f(t)$ 的步骤

1.) 将 $F(S)$ 化成最简真分式


$$\begin{aligned} \text{例: } F(S) &= \frac{S^2 + 9S + 11}{S^2 + 5S + 6} = 1 + \frac{4S + 5}{S^2 + 5S + 6} \\ &= 1 + \frac{-3}{S+2} + \frac{7}{S+3} \\ f(t) &= \delta(t) + (7e^{-3t} - 3e^{-2t})\varepsilon(t) \end{aligned}$$

2.) 求 $F(S)$ 分母多项式等于零的根, 将 $F(S)$ 分解成部分分式之和

3.) 求各部分分式的系数

4.) 对每个部分分式和多项式逐项求拉氏反变换。

Example 2:

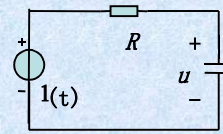

$$u_c(0^-) = 0$$

$$RC \frac{du}{dt} + u = 1(t)$$

$$SRCU(S) + U(S) = \frac{1}{S}$$

$$U(S) = \frac{1}{S(1 + SRC)}$$

then:

$$u(0^+) = \lim_{s \rightarrow \infty} s \frac{1}{s(1 + SRC)} = \lim_{s \rightarrow \infty} \frac{1}{(1 + SRC)} = 0$$

$$u(\infty) = \lim_{s \rightarrow 0} \frac{1}{(1 + SRC)} = 1$$

15.4 Application to Circuits

Steps in applying the Laplace transform:

1. Transform the circuit from the **time domain** to the **s domain**.
2. **Solve the circuit** using nodal analysis, mesh analysis, source transformation, superposition, or any circuit analysis technique with which we are familiar.
3. **Take the inverse transform** of the solution and thus obtain the solution in the time domain.

1. Kirchhoff's laws in s domain:

$$KCL \quad \Sigma i = 0$$

$$\Sigma I(S) = 0$$

$$KVL \quad \Sigma u = 0$$

$$\Sigma U(S) = 0$$

2. Circuit elements in s domain:

$$R: \quad \begin{array}{c} i \\ \text{---} \boxed{R} \text{---} \\ + \quad u \quad - \end{array} \quad u = Ri \quad \begin{array}{l} U(S) = RI(S) \\ I(S) = GU(S) \end{array}$$

$$\begin{array}{c} I(S) \\ \text{---} \boxed{R} \text{---} \\ + \quad U(S) \quad - \end{array} \quad \begin{array}{l} Z(s) = R \\ Y(s) = G \end{array}$$

$$L: \quad \begin{array}{c} i \\ \text{---} \boxed{L} \text{---} \\ + \quad u \quad - \end{array} \quad u = L \frac{di}{dt}$$


$$\begin{array}{c} I(s) \\ \text{---} \boxed{sL} \text{---} \end{array} \quad \begin{array}{c} Li(0^-) \\ \text{---} \boxed{} \text{---} \\ + \quad U(s) \quad - \end{array} \quad \begin{array}{l} U(S) = L(SI(S) - i(0^-)) \\ = SLI(S) - Li(0^-) \end{array}$$

$$\begin{array}{c} sL \\ \text{---} \boxed{} \text{---} \\ + \quad U(s) \quad - \end{array} \quad \begin{array}{c} i(0^-)/s \\ \text{---} \boxed{} \text{---} \end{array} \quad \begin{array}{l} I(S) = \frac{U(S)}{SL} + \frac{i(0^-)}{S} \\ Z(s) = sL \\ Y(s) = 1/sL \end{array}$$



$$C: \quad \begin{array}{c} i \\ \text{---} \boxed{} \text{---} \\ + \quad u \quad - \end{array} \quad u_c = u_c(0^-) + \frac{1}{C} \int_{0^-}^t i_c dt$$

$$\begin{array}{c} I_c(s) \\ \text{---} \boxed{1/sC} \text{---} \end{array} \quad \begin{array}{c} u_c(0^-)/S \\ \text{---} \boxed{} \text{---} \\ + \quad U_c(s) \quad - \end{array} \quad \begin{array}{l} U_c(S) = \frac{1}{SC} I_c(S) + \frac{u_c(0^-)}{S} \\ I_c(S) = SCU_c(S) - Cu_c(0^-) \end{array}$$

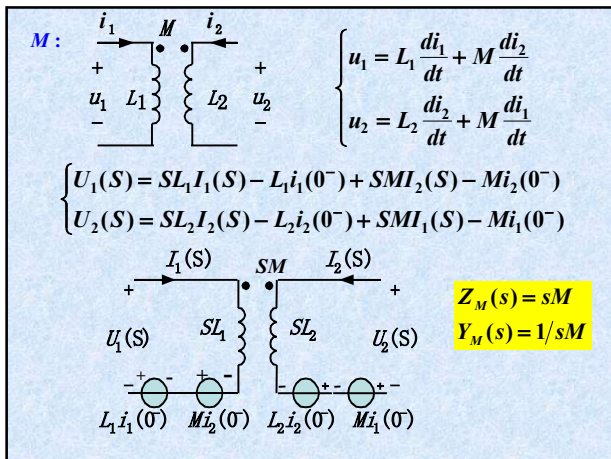
$$\begin{array}{c} 1/sC \\ \text{---} \boxed{} \text{---} \\ + \quad U_c(s) \quad - \end{array} \quad \begin{array}{c} Cu_c(0^-) \\ \text{---} \boxed{} \text{---} \end{array} \quad \begin{array}{l} Z(s) = 1/sC \\ Y(s) = sC \end{array}$$




Dependent sources:

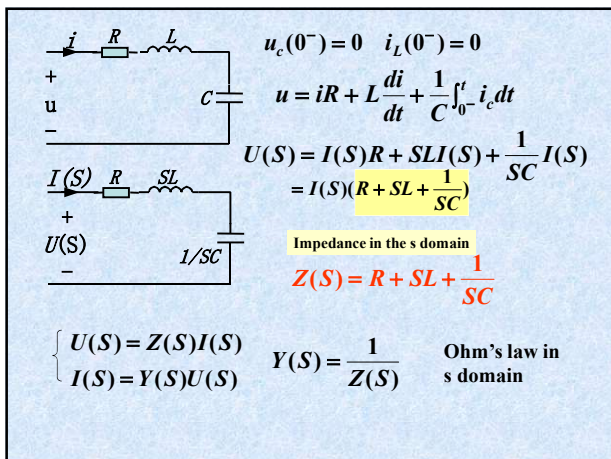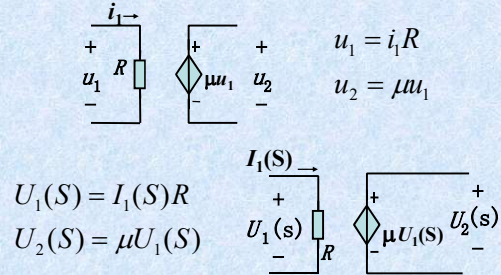

3.A circuit model in s domain:

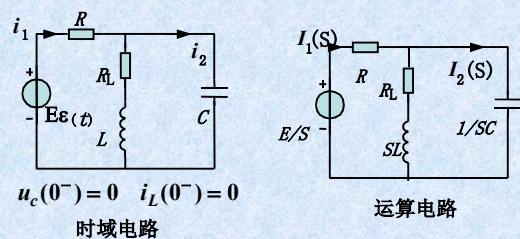

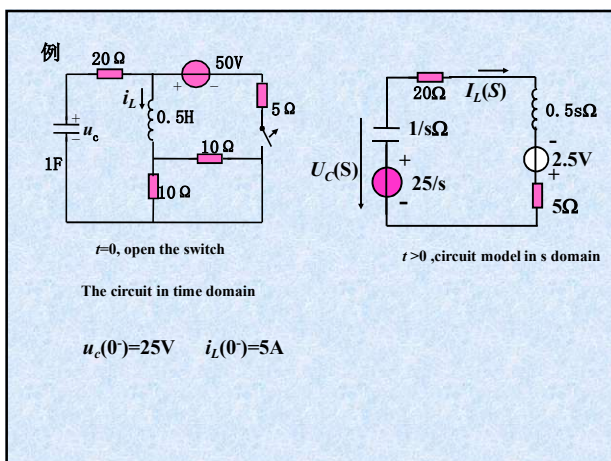
1. Transform the sources into s domain.
2. Transform the circuit elements into s domain.
3. Consider the initial condition of the storage elements.



4.Laplace transform application in circuits



- Steps:
1. Determine $u_c(0^-)$, $i_L(0^-)$.
 2. Set up a circuit model in s domain.
 3. Solve the circuit.
 4. Take the inverse transform of the solution.

Example 1:

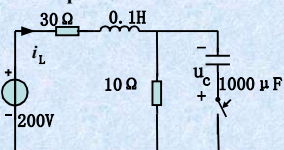

$$u_c(0^-) = 100V$$

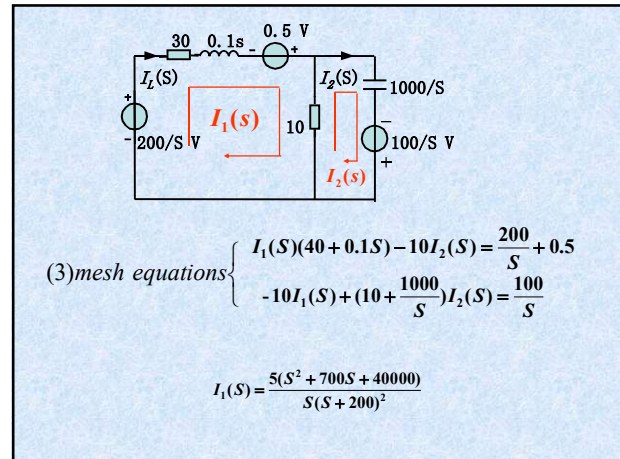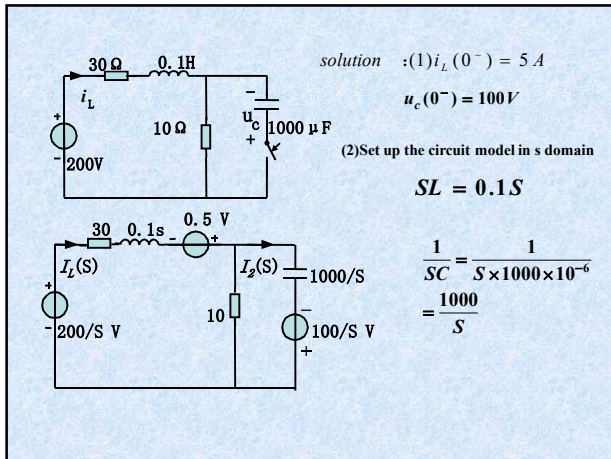When $t = 0$, k closes,
Calculate i_L , u_L .



$$I_1(S) = \frac{5(S^2 + 700S + 40000)}{S(S + 200)^2}$$

$$i(0^+) = \lim_{s \rightarrow \infty} SF(S) = \lim_{s \rightarrow \infty} \frac{5(S^2 + 700S + 40000)}{S^2 + 400S + 200^2} = 5$$

$$i(\infty) = \lim_{s \rightarrow 0} SF(S) = \lim_{s \rightarrow 0} \frac{5(S^2 + 700S + 40000)}{S^2 + 400S + 200^2} = 5$$

(4) Inverse transformation:

$$I_1(S) = \frac{K_1}{S} + \frac{K_{21}}{S + 200} + \frac{K_{22}}{(S + 200)^2}$$

$$I_1(S) = \frac{K_1}{S} + \frac{K_{21}}{S + 200} + \frac{K_{22}}{(S + 200)^2}$$



$$K_1 = F(S)S|_{S=0} = \frac{5(S^2 + 700S + 40000)}{S^2 + 400S + 200^2}|_{S=0} = 5$$


$$K_{22} = F(S)(S + 200)^2|_{S=-200} = 1500$$

$$K_{21} = \frac{d}{ds}(S + 200)^2 F(S)|_{S=-200} = 0$$


$$I_1(S) = \frac{5}{S} + \frac{0}{(S + 200)} + \frac{1500}{(S + 200)^2}$$
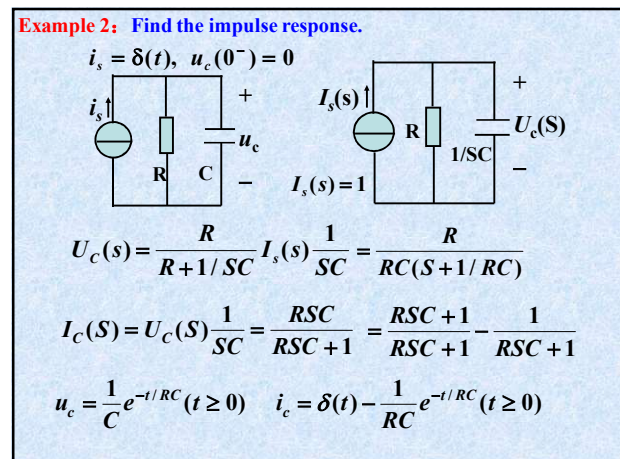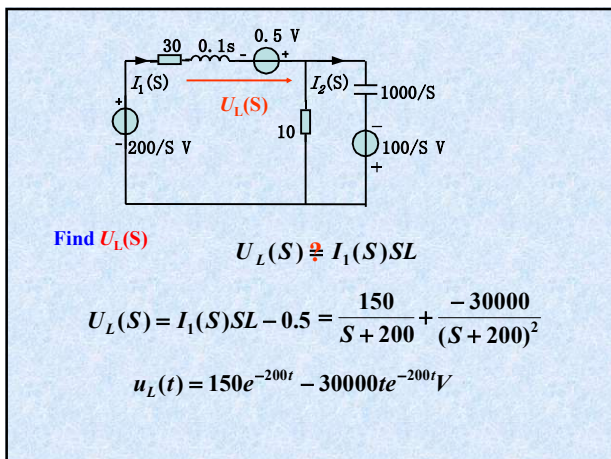
$$i_1(t) = (5 + 1500te^{-200t})\varepsilon(t)\text{ A}$$



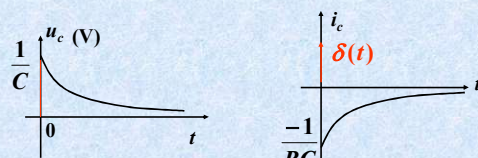

Ex:

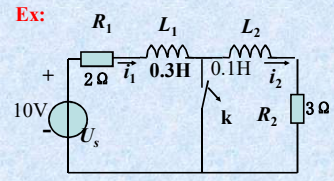


$t = 0$, k open,
Find: i_1, i_2 .
 $i_1(0^-) = 5A$
 $i_2(0^-) = 0$

Review


Laplace transform application in circuits

- steps:
1. Determine $u_c(0^-), i_L(0^-)$.
 2. Set up a circuit model in s domain.
 3. Solve the circuit.
 4. Take the inverse transform of the solution.

Ex:

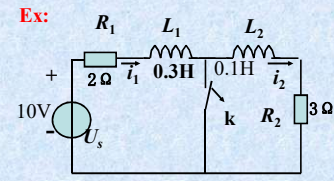


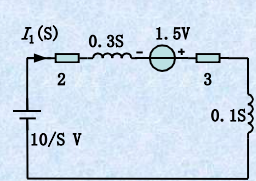$t = 0$, k open,
Find: i_1, i_2 .
 $i_1(0^-) = 5A$
 $i_2(0^-) = 0$




$$I_1(S) = \frac{\frac{10}{S} + 1.5}{\frac{2}{S} + 0.3S} = \frac{10 + 1.5S}{(5 + 0.4S)S}$$

$$= \frac{25 + 3.75S}{(S + 12.5)S} = \frac{2}{S} + \frac{1.75}{S + 12.5}$$
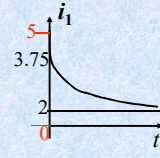
$$i_1 = 2 + 1.75e^{-12.5t} = i_2$$

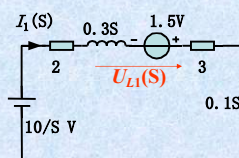
$i_1(0^+) \neq i_1(0^-)$
 $i_2(0^+) \neq i_2(0^-)$



$$U_{L1}(S) = 0.3SI(S) - 1.5$$

$$U_{L1}(S) = -\frac{6.56}{S + 12.5} - 0.375$$


$$u_{L1} = -0.375\delta(t) - 6.56e^{-12.5t}$$

$$U_{L2}(S) = 0.1SI(S)$$

$$U_{L2}(S) = 0.375 - \frac{2.19}{S + 12.5}$$

$$u_{L2} = +0.375\delta(t) - 2.19e^{-12.5t}$$

$$u_{L1} = -0.375\delta(t) - 6.56e^{-12.5t}$$
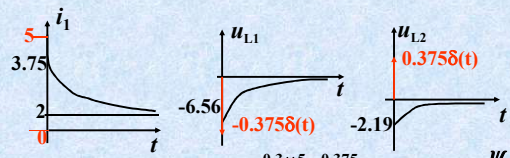
$$u_{L2} = +0.375\delta(t) - 2.19e^{-12.5t}$$


$$i_2(0^+) = i_2(0^-) + \frac{0.375}{0.1} = 3.75A$$



$$i_1(0^+) = \frac{0.3 \times 5 - 0.375}{0.3} = 3.75A$$

$$L = \frac{\psi}{i}$$


磁链守恒: $L_1 i_1(0^-) + L_2 i_2(0^-) = (L_1 + L_2) i(0^+)$

$$0.3 \times 5 + 0 = 0.4 \times 3.75$$

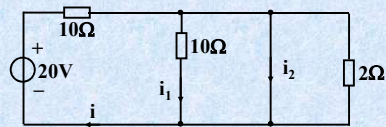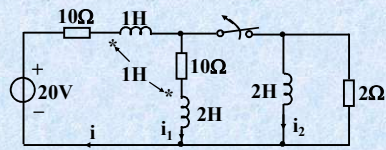
The circuit is shown in the Fig., when $t=0$, the switch is open, calculate i .


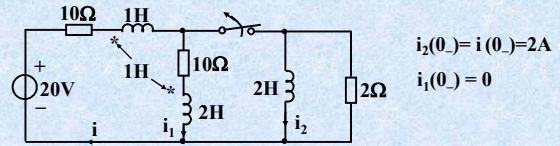
$$i_1(0_-) = 0 \quad i_2(0_-) = i(0_-) = 2A$$


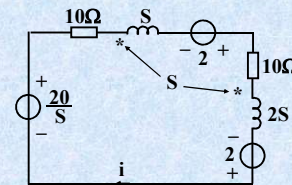
$$i_2(0_-) = i(0_-) = 2A \\ i_1(0_-) = 0$$



$$I(S) = \frac{\frac{20}{S} + 4}{5S + 20}$$

$$I(S) = \frac{4S + 20}{5S(S + 4)}$$

$$I(S) = \frac{1}{S} - \frac{0.2}{S + 4}$$

$$i(t) = 1 - 0.2e^{-4t}$$

- 小结:
- 1、运算法直接求得全响应
 - 2、用 0^- 初始条件，跳变情况自动包含在响应中
 - 3、运算法分析动态电路的步骤
 - 1). 由换路前电路计算 $u_c(0^-)$, $i_L(0^-)$ 。
 - 2). 画运算电路图
 - 3). 应用电路分析方法求象函数。
 - 4). 反变换求原函数。

15.5 TRANSFER FUNCTIONS

$$\text{Voltage gain} = \frac{\dot{V}_o(s)}{\dot{V}_i(s)}$$

$$\text{Current gain} = \frac{\dot{I}_o(s)}{\dot{I}_i(s)}$$

$$\text{Transfer impedance} = \frac{\dot{V}_o(s)}{\dot{I}_i(s)}$$


$$\text{Transfer admittance} = \frac{\dot{I}_o(s)}{\dot{V}_i(s)}$$

The transfer function $H(s)$ is the ratio of the output response $Y(s)$ to the input excitation $X(s)$, assuming all initial conditions are zero.


$$H(S) \rightleftharpoons H(j\omega)$$

$$H(s) = \frac{Y(s)}{X(s)}$$

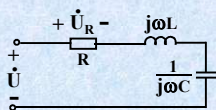与对应正弦稳态响应的关系 $H(S) \rightleftharpoons H(j\omega)$



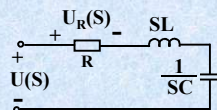
$$H(j\omega) = \frac{\dot{U}_R}{\dot{U}} \\ = \frac{R}{R + j\omega L + \frac{1}{j\omega C}}$$



$$H(S) = \frac{U_R(S)}{U(S)} \\ = \frac{R}{R + SL + \frac{1}{SC}}$$


A DISCUSSION: PHASOR DOMAIN AND S DOMAIN

1. Sinusoidal response:

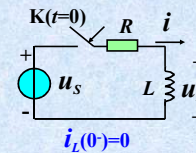

$$u_s = U_m \sin(\omega t + \psi_u)$$

$$i(0) = 0$$

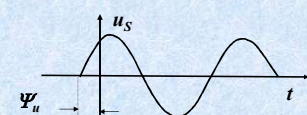

calculate: $i(t)$

$K(t=0)$ R i $u_s = U_m \sin(\omega t + \psi_u)$
 u_s L u_L $Ri + L \frac{di}{dt} = U_m \sin(\omega t + \psi_u)$
 $i_L(0^-)=0$ **强制分量(稳态分量)**
 $i = i' + i''$ **自由分量(暂态分量)** $i'' = Ae^{-\frac{t}{\tau}}$
 Particular solution: i'
 $I_m = \frac{U_m}{\sqrt{R^2 + (\omega L)^2}}$
 $\varphi = \arctg \frac{\omega L}{R}$
 $i' = I_m \sin(\omega t + \psi_u - \varphi)$

$K(t=0)$ R i $u_s = U_m \sin(\omega t + \psi_u)$
 u_s L u_L $i_L(0^-)=0$
 $i = i' + i'' = I_m \sin(\omega t + \psi_u - \varphi) + Ae^{-\frac{t}{\tau}}$
 由 $i(0^+) = 0 = I_m \sin(\psi_u - \varphi) + A$ 定积分常数 A
 $A = -I_m \sin(\psi_u - \varphi)$
 $i = I_m \sin(\omega t + \psi_u - \varphi) - I_m \sin(\psi_u - \varphi)e^{-\frac{t}{\tau}}$

$K(t=0)$ R $I(s)$ $u_s(s)$ SL $u_L(s)$ $i_L(0^-)=0$
 $RI(S) + SLI(S) = \frac{S \sin \psi_u + \omega \cos \psi_u}{S^2 + \omega^2} U_m$
 $I(S) = \frac{S \sin \psi_u + \omega \cos \psi_u}{(S^2 + \omega^2)(R + SL)} U_m$
 $= (\frac{K_1}{S + R/L} + \frac{K_2}{S + j\omega} + \frac{K_3}{S - j\omega}) U_m$
 $K_1 = \frac{S \sin \psi_u + \omega \cos \psi_u}{(S^2 + \omega^2)(R + SL)} (S + R/L) |_{S=-R/L}$
 $= \frac{\omega L \cos \psi_u - R \sin \psi_u}{R^2 + (\omega L)^2}$
 $= \frac{1}{\sqrt{R^2 + (\omega L)^2}} [\frac{\omega L}{\sqrt{R^2 + (\omega L)^2}} \cos \psi_u - \frac{R}{\sqrt{R^2 + (\omega L)^2}} \sin \psi_u]$
 $= \frac{1}{\sqrt{R^2 + (\omega L)^2}} \sin(\psi_u - \varphi)$
 $\varphi = \arctg \frac{\omega L}{R}$

$K_2 = \frac{S \sin \psi_u + \omega \cos \psi_u}{(S^2 + \omega^2)(R + SL)} U_m (S + j\omega) |_{S=j\omega}$
 $= \frac{-\cos \psi_u + j \sin \psi_u}{2Rj + 2\omega L} U_m$
 $K_3 = \frac{S \sin \psi_u + \omega \cos \psi_u}{(S^2 + \omega^2)(R + SL)} U_m (S - j\omega) |_{S=-j\omega}$
 $= \frac{\cos \psi_u + j \sin \psi_u}{2Rj - 2\omega L} U_m$
 $\frac{K_2}{S + j\omega} + \frac{K_3}{S - j\omega} = \frac{(R \sin \psi_u - \omega L \cos \psi_u)S - (\omega L \sin \psi_u + R \cos \psi_u)\omega}{[R^2 + (\omega L)^2](S^2 + \omega^2)}$
 $= \frac{1}{\sqrt{R^2 + (\omega L)^2}} \frac{(\frac{R}{\sqrt{R^2 + (\omega L)^2}} \sin \psi_u - \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}} \cos \psi_u)S + (\frac{\omega L}{\sqrt{R^2 + (\omega L)^2}} \sin \psi_u + \frac{R}{\sqrt{R^2 + (\omega L)^2}} \cos \psi_u)\omega}{S^2 + \omega^2}$
 $\varphi = \arctg \frac{\omega L}{R}$

$\frac{K_2}{S + j\omega} + \frac{K_3}{S - j\omega} = \frac{S \sin(\psi_u - \varphi) + \omega \cos(\psi_u - \varphi)}{S^2 + \omega^2} \frac{1}{\sqrt{R^2 + (\omega L)^2}}$
 $I(S) = \frac{S \sin \psi_u + \omega \cos \psi_u}{(S^2 + \omega^2)(R + SL)} U_m$
 $= (\frac{K_1}{S + R/L} + \frac{K_2}{S + j\omega} + \frac{K_3}{S - j\omega}) U_m$
 $K_1 = \frac{1}{\sqrt{R^2 + (\omega L)^2}} \sin(\psi_u - \varphi)$
 $\varphi = \arctg \frac{\omega L}{R}$
 $I(S) = \frac{U_m}{\sqrt{R^2 + (\omega L)^2}} [\sin(\psi_u - \varphi) \frac{1}{S + R/L} + \frac{\sin(\psi_u - \varphi)S + \cos(\psi_u - \varphi)\omega}{S^2 + \omega^2}]$
 $\varphi = \arctg \frac{\omega L}{R}$ $I_m = \frac{U_m}{\sqrt{R^2 + (\omega L)^2}}$
 $i = I_m \sin(\omega t + \psi_u - \varphi) - I_m \sin(\psi_u - \varphi)e^{-\frac{t}{\tau}}$

Phasor method:
 It's a convenient way to get the sinusoidal steady_state response.
Laplace transform:
 A powerful tool to analyze dynamics of the higher_order circuits.
 It can provide us the complete response of an arbitrary input.
 a complex variable $s = \sigma + j\omega$
 If $\sigma=0$, natural response is beyond consideration
 $H(S) \longleftrightarrow H(j\omega)$

We know the circuit equations:

$$\begin{cases} \frac{d^2 y}{dt^2} + 3 \frac{dy}{dt} + 2y = 2 \frac{dx}{dt} + x \\ y(0_-) = 0, \left. \frac{dy}{dt} \right|_{t=0_-} = 0 \end{cases}$$

Where, y is the output response, x is the excitation. Calculate $H(s)$ and the unit impulse response $h(t)$.

Solution:


$$s^2 Y(s) + 3s Y(s) + 2Y(s) = 2s X(s) + 3X(s)$$

$$(s^2 + 3s + 2)Y(s) = (2s + 3)X(s)$$

$$H(s) = \frac{Y(s)}{X(s)} = \frac{2s + 3}{s^2 + 3s + 2} = \frac{1}{s + 1} + \frac{1}{s + 2}$$

$$h(t) = \mathcal{L}^{-1}[H(s)] = \mathcal{L}^{-1}\left[\frac{1}{s + 1} + \frac{1}{s + 2}\right] = (e^{-t} + e^{-2t})1(t)$$

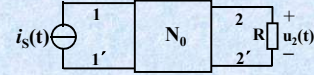Example: N_0 is a linear passive network, if $i_s(t) = 1(t)$ A, zero_state response $u_2(t) = 2 \cdot 1(t) (1 - e^{-2t})$ V, when $i_s(t) = 10 \sin 2t$ A, calculate the sinusoidal steady_state response $u_2(t)$.



$$H(s) = \frac{\mathcal{F}[u_2(t)]}{\mathcal{F}[i_s(t)]} = \frac{2(\frac{1}{s} - \frac{1}{s+2})}{\frac{1}{s}} = \frac{4}{s+2}$$

$$\dot{U}_2 = H(j2) \dot{I}_s = \frac{4}{2+j2} \times 10 = 14.1 \angle -45^\circ$$

$$u_2(t) = 14.1 \sin(2t - 45^\circ)$$

The transfer function $H(s)$ is the ratio of the output response $Y(s)$ to the input excitation $X(s)$, assuming all initial conditions are zero.

$$H(s) = \frac{Y(s)}{X(s)}$$

A special case is when the input is the unit impulse function,

$$x(t) = \delta(t)$$

so that $X(s) = 1$.

For this case, $Y(s) = H(s)$ or $y(t) = h(t)$ where

$$h(t) = \mathcal{L}^{-1}[H(s)]$$

The term $h(t)$ represents the unit impulse response—it is the time-domain response of the network to a unit impulse.

Example1: The transfer function

$H(j\omega) = (2j\omega + 3)/(-\omega^2 + 3j\omega + 2)$, when the input excitation is e^{-t} , find the zero-state response.

Solution :

We use s instead of $j\omega$, and we obtain the network function of complex frequency domain.

$$H(s) = \frac{2s + 3}{s^2 + 3s + 2} \quad Y(s) = H(s)X(s) = \frac{2s + 3}{s^2 + 3s + 2} \cdot \frac{1}{s + 1}$$

$$= \frac{-1}{s + 2} + \frac{1}{(s + 1)^2} + \frac{1}{s + 1}$$

$$\therefore y(t) = -e^{-2t} + te^{-t} + e^{-t} \quad t \geq 0$$

Example2: The transfer function

$H(s) = (2s + 3)/(s^2 + 3s + 2)$, when the input excitation is $\sin t$, find the sinusoidal steady-state response.

Solution : We use $j\omega$ instead of s , we obtain the network function of frequency domain:

$$H(j\omega) = \frac{3 + 2j\omega}{-\omega^2 + 3j\omega + 2} \quad \because \omega = 1 \text{ rad/s}$$

If we assume Y_m is the phasor of the input sinusoidal steady-state response,

$$Y_m = 1 \angle 0^\circ \cdot \frac{3 + 2j\omega}{-\omega^2 + 3j\omega + 2} \Big|_{\omega=1}$$

$$Y_m = 1 \angle 0^\circ \cdot \frac{3 + 2j\omega}{-\omega^2 + 3j\omega + 2} \Big|_{\omega=1}$$

$$= \frac{3 + j2}{1 + j3} = 0.9 - j0.7 = 1.14 \angle -37.87^\circ$$

\therefore The steady-state response is

$$y(t) = 1.14 \sin(t - 37.87^\circ)$$

Example3: The network's zero-state response of unit step function is $(1 - e^{-t})$, then find the network function $H(s)$.

Solution : $\because s(t) = (1 - e^{-t})\varepsilon(t)$

The unit impulse function

$$h(t) = \frac{ds(t)}{dt} = e^{-t}\varepsilon(t) + (1 - e^{-t})\delta(t) = e^{-t}\varepsilon(t)$$

$$\therefore H(s) = L[h(t)] = L[e^{-t}\varepsilon(t)] = \frac{1}{s+1}$$

Example4: The input impedance

$$Z(s) = \frac{6s^3 + 3s^2 + 3s + 1}{6s^3 + 3s}$$

Try to construct the network.

Solution: (method1:)

$$Z(s) = 1 + \frac{3s^2 + 1}{6s^3 + 3s} = 1 + \frac{1}{2s + \frac{s}{3s^2 + 1}}$$

$$= 1 + \frac{1}{2s + \frac{1}{3s + \frac{1}{s}}} \quad \text{As in Fig.}$$

(method2:)

$$Z(s) = 1 + \frac{3s^2 + 1}{6s^3 + 3s} = 1 + \frac{1}{3s} + \frac{s}{6s^2 + 3}$$

$$= 1 + \frac{1}{3s} + \frac{1}{6s + \frac{3}{s}}$$

As in Fig.