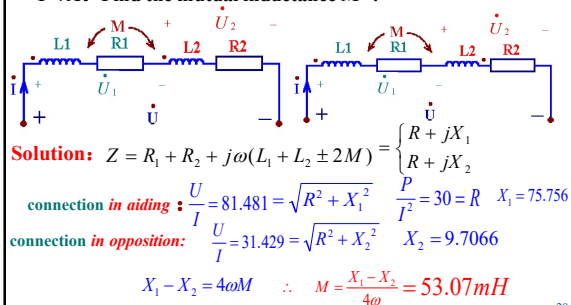


Example 2. Two coupled inductors are connected to a sinusoidal source with an effective value of 220V and the frequency of 50Hz. If the two inductors are connected **in aiding**, $I=2.7A, P=218.7W$; if they are connected **in opposition**, $I=7A$. Find the mutual inductance M =?



28

Example 3. $\omega=4rad/s, C = 5F, M=3H$. 1) Find the input impedance Z ; 2) What value should the capacitor C be to make Z be a pure resistance?

Solution: The mutual inductance are connected in aiding parallel, so

$$L = \frac{4 \times 6 - 3^2}{4 + 6 - 2 \times 3} = \frac{15}{4} H$$


And the equivalent circuit is as follows

Thus

$$Z = 10 - j0.05 + j15 = 10 + j14.95(\Omega)$$


To assure Z be a pure resistance,
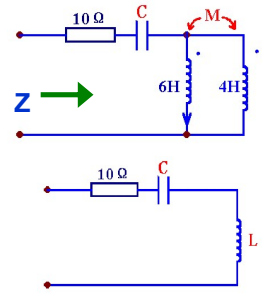
$$\frac{1}{\omega C} = 15 \therefore C = \frac{1}{60} F$$




29

3. T-connection (T型联接)

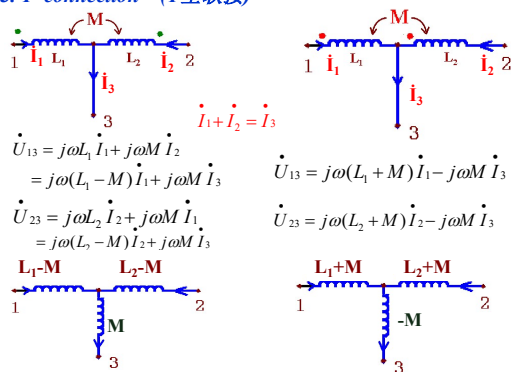


30

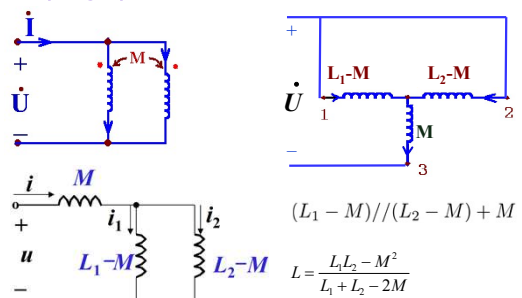Decoupling Equivalent Circuit of Parallel-aiding Connection



31

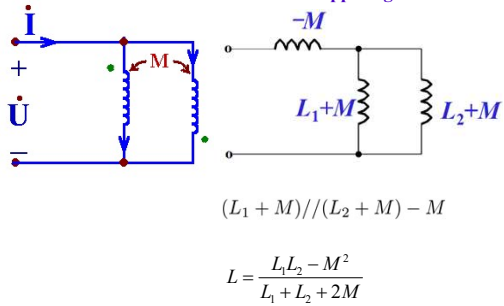Decoupling Equivalent Circuit of Parallel-opposing Connection



32

Example 3. $\omega=4\text{rad/s}$, $C = 5\text{F}$, $M=3\text{H}$. 1) Find the input impedance Z ; 2) What value should the capacitor C be to make Z be a pure resistance?

Solution: The mutual inductance are connected in aiding parallel, so

$$L = \frac{3}{4} + 4 = \frac{15}{4} \text{ H}$$

And the equivalent circuit is as follows


Thus

$$Z = 10 - j0.05 + j15$$

$$= 10 + j14.95(\Omega)$$


To assure Z be a pure resistance,
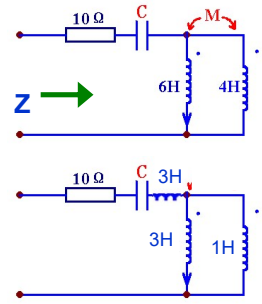
$$\frac{1}{\omega C} = 15 \quad \therefore C = \frac{1}{60} \text{ F}$$




33

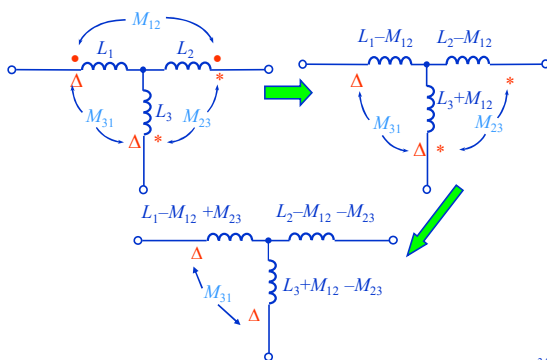Exercise: Find the decoupling circuit of the following three-coupled inductance.




34

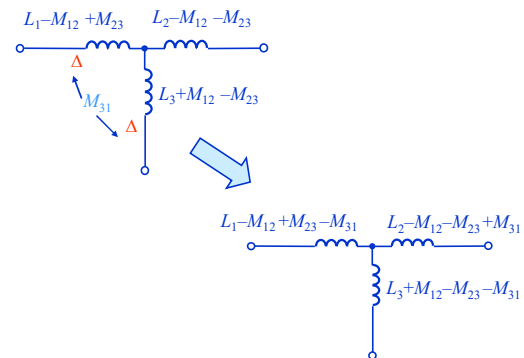

35

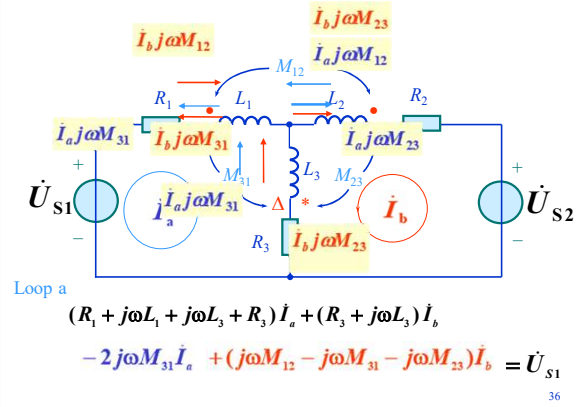Example 4 Write the mesh-current equation



Loop b:


$$(R_2 + j\omega L_2 + j\omega L_3 + R_3) \dot{I}_b + (R_3 + j\omega L_3) \dot{I}_a - 2j\omega M_{23} \dot{I}_b + (j\omega M_{12} - j\omega M_{31} - j\omega M_{23}) \dot{I}_a = \dot{U}_{S2}$$

Obtained:


$$\begin{cases} (R_1 + j\omega L_1 - j2\omega M_{31} + j\omega L_3 + R_3) \dot{I}_a + (R_3 + j\omega L_3 + j\omega M_{12} - j\omega M_{31} - j\omega M_{23}) \dot{I}_b = \dot{U}_{S1} \\ (R_3 + j\omega L_3 + j\omega M_{12} - j\omega M_{31} - j\omega M_{23}) \dot{I}_a + (R_2 + j\omega L_2 - j2\omega M_{23} + j\omega L_3 + R_3) \dot{I}_b = \dot{U}_{S2} \end{cases}$$

4、Decoupling Equivalent Circuit with CCVS

(受控源等效电路)

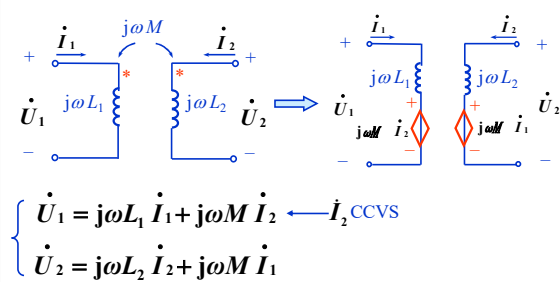

Example 5. Let $\omega=10\text{rad/s}$, $R=10\Omega$. Find \dot{I}_1 , \dot{I}_2 and the power absorbed by R if 1) $k=0.5$; 2) $k=1$.

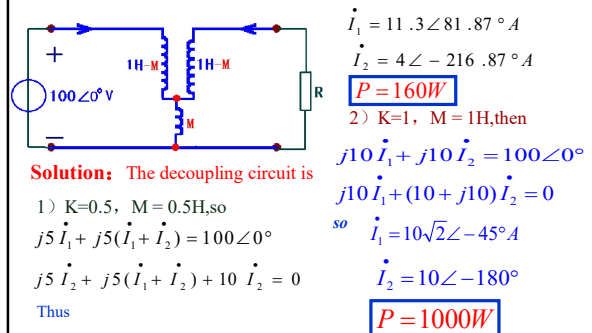

Example 6. Assume that Z obtained the maximum power, calculate the value of Z . Where


$$u(t) = 10\sqrt{2} \cos(10^4 t + 53.1^\circ) V$$

Solution: Labeled the dotted terminals and draw this circuit's diagram

The decoupling equivalent circuit is


Find open-circuit voltage $U_{oc} = \frac{8+j4}{14+j4} 10\angle 0^\circ = 6.11\angle 10.61^\circ V$

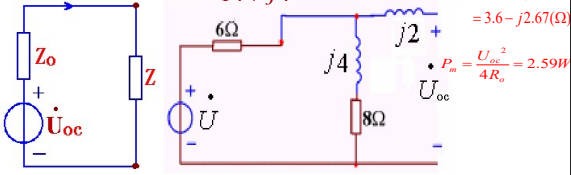Find Z_0 $Z_o = j2 + \frac{6(8+j4)}{14+j4} = 3.6 + j2.67 \therefore Z = Z_o^* = 3.6 - j2.67(\Omega)$




40

Example 7 $\omega L_1 = \omega L_2 = 10\Omega$, $\omega M = 5\Omega$, $R_1 = R_2 = 6\Omega$, $U_s = 6V$, Find Thevenin equivalent circuit.

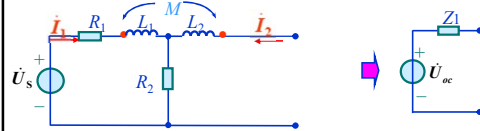


Solution 1:

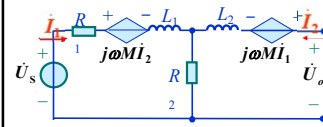

41

Find \dot{U}_{oc} $I_2 = 0$

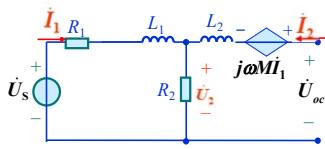


$$\dot{I}_1 = \frac{\dot{U}_s}{R_1 + j\omega L_1 + R_2} = \frac{6\angle 0^\circ}{12 + j10} = \frac{6\angle 0^\circ}{15.62\angle 39.8^\circ} = 0.384\angle -39.8^\circ A$$

$$\dot{U}_{oc} = j\omega M \dot{I}_1 + R_2 \dot{I}_1 = (6 + j5) \times 0.384\angle -39.8^\circ = 3\angle 0^\circ V$$

42

Find Z_i 加压求流

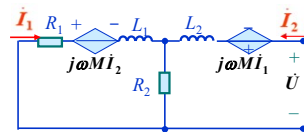


$$(R_1 + R_2 + j\omega L_1) \dot{I}_1 + R_2 \dot{I}_2 + j\omega M \dot{I}_2 = 0$$

$$(R_2 + j\omega L_2) \dot{I}_2 + R_2 \dot{I}_1 + j\omega M \dot{I}_1 = \dot{U}$$

$$\dot{I}_2 = \frac{\dot{U}}{3 + j7.5}, \quad Z_i = \frac{\dot{U}}{\dot{I}_2} = 3 + j7.5 = 8.08\angle 68.2^\circ \Omega$$

43

Solution 2:

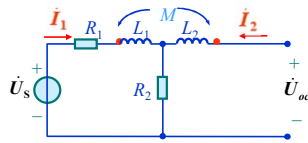


Find \dot{U}_{oc} $\dot{I}_2 = 0$

$$\dot{I} = \frac{\dot{U}_s}{R_1 + j\omega L_1 + R_2} = \frac{6\angle 0^\circ}{12 + j10} = \frac{6\angle 0^\circ}{15.62\angle 39.8^\circ} = 0.384\angle -39.8^\circ \text{ A}$$

$$\begin{aligned}\dot{U}_{oc} &= j\omega M \dot{I}_1 + R_2 \dot{I}_1 \\ &= (6 + j5) \times 0.384\angle -39.8^\circ = 3\angle 0^\circ \text{ V}\end{aligned}$$

44

Find Z_i

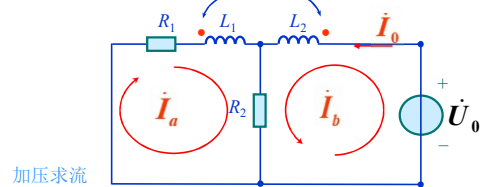


加压求流

$$\begin{cases} (R_1 + R_2 + j\omega L_1) \dot{I}_a + R_2 \dot{I}_b + j\omega M \dot{I}_b = 0 \\ (R_2 + j\omega L_2) \dot{I}_b + R_2 \dot{I}_a + j\omega M \dot{I}_a = \dot{U}_0 \end{cases}$$

$$\dot{I}_0 = \dot{I}_b = \frac{\dot{U}_0}{3 + j7.5}, \quad Z_i = \frac{\dot{U}_0}{\dot{I}_0} = 3 + j7.5 = 8.08\angle 68.2^\circ \Omega$$

45

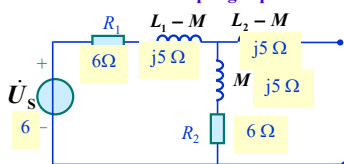
Solution 3: Decoupling Equivalent Circuit



$$\begin{aligned}\dot{U}_0 &= \frac{6 + j5}{6 + j5 + j5 + 6} = 3\angle 0^\circ \\ Z_i &= 5 + \frac{(6 + j5)(6 + j5)}{(6 + j5) + (6 + j5)} \\ &= j5 + \frac{6 + j5}{2} = j5 + 3 + j2.5 \\ &= 3 + j7.5 = 8.08\angle 68.2^\circ \Omega\end{aligned}$$

46

13.4 The Linear Transformer (空芯变压器)

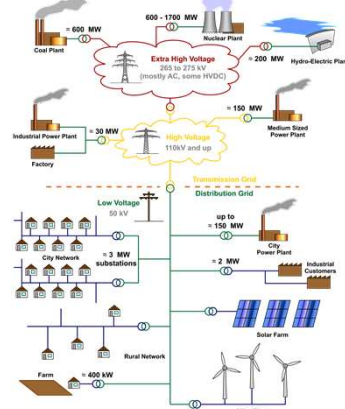

47

13.4 The Linear Transformer (空芯变压器)




48

13.4 The Linear Transformer (空芯变压器)



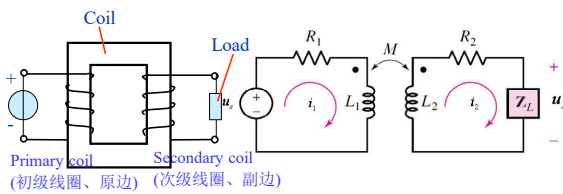13.4 The Linear Transformer (空芯变压器)


A Transformer is generally a four-terminal device comprising two (or more) magnetically coupled coils.




Coil {
Air, plastic
silicon steel sheet, amorphous alloy

A linear transformer containing a source in the primary circuit and a load in the secondary circuit. Resistance is also included in both the primary and the secondary.

50

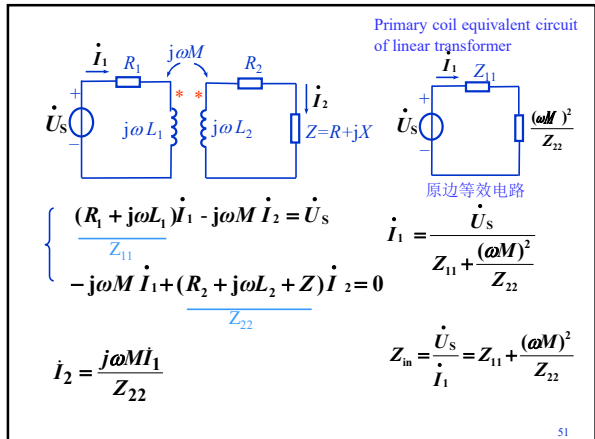

51

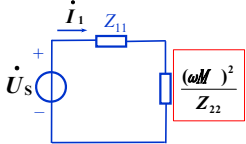

reflected impedance (Z_l)
副边对原边的引入阻抗、反射阻抗

$$Z_l = \frac{(\omega M)^2}{Z_{22}} = \frac{\omega^2 M^2}{R_{22} + jX_{22}} = \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} - \frac{j\omega^2 M^2 X_{22}}{R_{22}^2 + X_{22}^2}$$

$$= R_l + jX_l$$

reflected resistance (R_l) $i_2 = 0, Z_{in} = Z_{11}$
 $i_2 \neq 0, Z_l = Z_{11} + Z_l$

$$R_l = \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2}$$

reflected reactance (X_l)

$$X_l = -\frac{\omega^2 M^2 X_{22}}{R_{22}^2 + X_{22}^2}$$

The reactance which the secondary reflects into the primary circuit has a sign which is opposite to that of X_{22}

52

Transmission of energy(传送功率)

$$Z_l = \frac{(\omega M)^2}{Z_{22}} = \frac{\omega^2 M^2}{R_{22} + jX_{22}} = \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} - \frac{j\omega^2 M^2 X_{22}}{R_{22}^2 + X_{22}^2}$$

$$= R_l + jX_l$$

$$R_l = \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} \quad R_l > 0, \text{ absorbing power, providing by primary coil}$$

Power developed by source = Power absorbed by load
 $= I_1^2 R_1 + I_1^2 R_l$

absorbing by primary coil
absorbing by secondary coil, transferring by mutual inductance

$$I_1^2 R_l^2 = I_2^2 R_{22}$$

53