


What's next?

- (1) Frequency characteristics; Resonance
- (2) Magnetically coupled circuits; Transformers
- (3) Three-Phase circuits;
- (4) Periodic, nonsinusoidal excitations

1

Frequency response(频率响应)

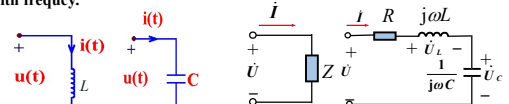The frequency response of a circuit is the variation in its behavior with change in signal frequency, usually the variation of **amplitude** and **phase** with frequency.



$$X_L = \omega L \quad X_C = -\frac{1}{\omega C}$$

$$Z = R + j(\omega L - \frac{1}{\omega C})$$

$$|Z| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

Amplitude and phase of impedance vary with frequency.

amplitude response 幅频特性

$\varphi = \arctan \frac{\omega L - \frac{1}{\omega C}}{R}$
phase response 相频特性

2

RESONANCE (谐振)



虎门大桥 2020




Tacoma Narrows Bridge,
USA, 1940

3

RESONANCE (谐振)

Resonance is a condition in an **RLC circuit** in which the capacitive and inductive reactance are equal in magnitude, thereby resulting in a purely resistive impedance.

1. Series Resonance (串联谐振)

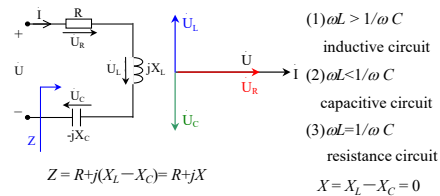

Resonance results when the imaginary part of impedance **Z** is zero.

4

Resonant frequency

$$\omega L = \frac{1}{\omega C} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

Notice the characteristics at Series Resonance:

(1) \dot{U} and \dot{I} in phase, $\cos \varphi = 1$.


(2) $Z = R$, $|Z|$ reaches its minimum.

Characteristic impedance (特征阻抗):

$$\rho = \omega_0 L = \frac{1}{\omega_0 C}, \text{ or } \rho = \sqrt{\frac{L}{C}}, \Omega$$

Quality factor of a series resonant circuit (品质因数):
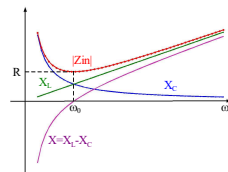
$$Q = \frac{\omega_0 L}{R} = \frac{\rho}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} \quad \text{dimensionless (无量纲)}$$





5

Notice the characteristics at Series Resonance:

(3) I reaches its maximum.

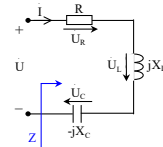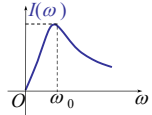(4) The LC series combination acts like a **short circuit**, and the entire voltage is across R.

The inductor voltage and capacitor voltage can be much **more than the source voltage**.



$$Q = \frac{\omega_0 L}{R}$$

$$Q = \frac{1}{\omega_0 C R}$$

$$\dot{U}_L = j\omega_0 L \dot{I}_0, \quad \dot{U}_C = -j\left(\frac{1}{\omega_0 C}\right) \dot{I}_0 \quad \dot{U}_L = j\omega_0 L \dot{I}_0 = j\omega_0 L \frac{\dot{U}}{R} = jQ \dot{U}$$

$$\dot{U}_X = \dot{U}_L + \dot{U}_C = 0 \quad \dot{U}_C = \frac{\dot{I}_0}{j\omega_0 C} = -j \frac{\dot{U}_0}{\omega_0 C R} = -jQ \dot{U}$$

$$\therefore \dot{U} = \dot{U}_R \quad \text{Voltage resonance}$$

6

Notice the characteristics at Series Resonance:

(5) Power at Series Resonance

Power absorbed by load


$$P = RI^2 = U^2/R$$

$$Q_L = \omega_0 LI^2 \quad Q_C = -\frac{1}{\omega_0 C} I^2 \quad Q = Q_L + Q_C = 0$$

Power developed by source

$$P = UI \cos \varphi = RI^2$$

$$Q = UI \sin \varphi = 0$$

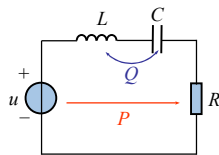

Energy change between inductor and capacitor, but NOT between the source and the reactive loads.

7

Notice the characteristics at Series Resonance:

(6) Energy Storage at Series Resonance

$$u_s(t) = U_{sm} \sin(\omega_0 t) \quad I_0(t) = I_m \sin(\omega_0 t) = \frac{U_{sm}}{R} \sin(\omega_0 t)$$

Electric-field energy $u_C(t) = Qu_s(t-90^\circ) = QU_{sm} \sin(\omega_0 t - 90^\circ)$

$$w_C(t) = \frac{1}{2} C u_C^2(t) = -QRI_m \cos(\omega_0 t)$$

$$= \frac{1}{2} C \left(\sqrt{\frac{L}{C}}\right)^2 I_m^2 \cos^2(\omega_0 t) \quad Q = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{2} LI_m^2 \cos^2(\omega_0 t)$$

Magnetic-field energy

$$w_L(t) = \frac{1}{2} LI_0^2(t) = \frac{1}{2} LI_m^2 \sin^2(\omega_0 t) \quad \therefore W_{Lm} = W_{Cm}$$

$$w_C(t) + w_L(t) = \frac{1}{2} LI_m^2 = \frac{1}{2} CU_{Cm}^2 = CQ^2 U^2$$

8

Notice the characteristics at Series Resonance:

(7) Physical significance of Q

Rate of inductor voltage or capacitor voltage to the source

$$\dot{U}_L = j\omega_0 L \dot{I}_0 = jQ \dot{U}$$

Rate of Electric-field and Magnetic-field energy to the energy dissipated by the circuit in one period

$$Q = \frac{\omega_0 L}{R} = \omega_0 \cdot \frac{LI_0^2}{RI_0^2} = 2\pi \frac{LI_0^2}{RI_0^2 T_0}$$


The third one...

9

Frequency response of Series Resonance Current

Selectivity (选择性)

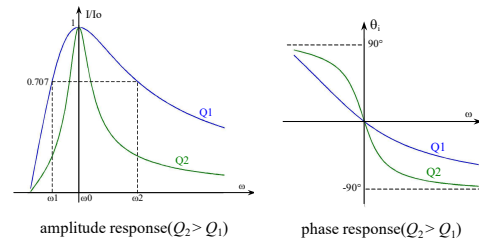The bandwidth (带宽) B is defined as the difference between the two half-power frequencies. $B = \omega_2 - \omega_1$ $\dot{U}/\dot{I}_0 = 1/\sqrt{2}$



10

Frequency response of Series Resonance Current

Normalization (归一化处理): universal resonance curve (通用谐振曲线)

$$\omega \rightarrow \frac{\omega}{\omega_0} = \eta, \quad I(\omega) \rightarrow \frac{I(\omega)}{I(\omega_0)} = \frac{I}{I_0}$$

$$\begin{aligned} \frac{I(\omega)}{I(\omega_0)} &= \frac{U/|Z|}{U/R} = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{1}{\sqrt{1 + (\frac{\omega L}{R} - \frac{1}{\omega RC})^2}} \\ &= \frac{1}{\sqrt{1 + (\frac{\omega_0 L}{R} \cdot \frac{\omega}{\omega_0} - \frac{1}{\omega_0 RC} \cdot \frac{\omega_0}{\omega})^2}} = \frac{1}{\sqrt{1 + (Q \cdot \frac{\omega}{\omega_0} - Q \cdot \frac{\omega_0}{\omega})^2}} \\ \frac{I}{I_0} &= \frac{1}{\sqrt{1 + Q^2(\eta - \frac{1}{\eta})^2}} \end{aligned}$$

11

Frequency response of Series Resonance Current

Normalization (归一化处理): universal resonance curve (通用谐振曲线)

$$\eta_1 = \frac{\omega_1}{\omega_0}, \quad \eta_2 = \frac{\omega_2}{\omega_0}, \quad \omega_2 > \omega_1.$$

$$\frac{I}{I_0} = \frac{1}{\sqrt{1 + Q^2(\eta - \frac{1}{\eta})^2}}$$

$$\frac{1}{\sqrt{1 + Q^2(\eta - \frac{1}{\eta})^2}} = \frac{1}{\sqrt{2}}$$

$$\eta_1 = \frac{-1 + \sqrt{1 + 4Q^2}}{2Q}$$

$$\eta_2 = \frac{1 + \sqrt{1 + 4Q^2}}{2Q}$$

$$\Delta\eta = \eta_2 - \eta_1 = \frac{1}{Q} \quad \boxed{Q = \frac{\omega_0}{\Delta\omega}}$$

universal resonance curve

12

The third aspect of Physical significance of Q

Frequency response of Series Resonance Voltage

Normalization (归一化处理)

$$U_C(\omega) = \frac{I}{\omega C} = \frac{U}{\omega C \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad \frac{d}{d\eta} [\eta^2 + Q^2(\eta^2 - 1)^2] = 0$$


$$= \frac{QU}{\sqrt{\eta^2 + Q^2(\eta^2 - 1)^2}} \quad \eta_{C1} = 0 \quad \eta_{C2} = \sqrt{1 - \frac{1}{2Q^2}} < 1$$

$$U_L(\omega) = \omega LI = \omega L \cdot \frac{U}{|Z|} = \frac{\omega LU}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad U_{Cm}(\omega_{cm}) = \frac{QU}{\sqrt{1 - \frac{1}{4Q^2}}} > QU$$

$$= \frac{QU}{\sqrt{\frac{1}{\eta^2} + Q^2(1 - \frac{1}{\eta^2})^2}} \quad Q > \frac{1}{\sqrt{2}} \quad \omega_{cm} \text{ 存在}$$

13

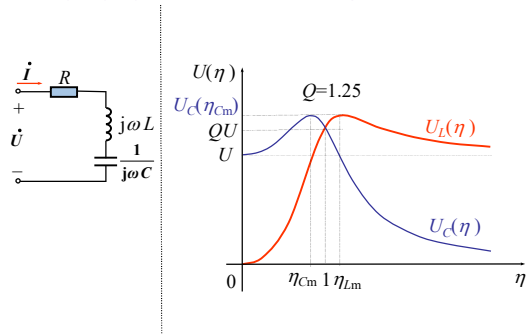Frequency response of Series Resonance Voltage




14


例1 电路如图12-18所示。已知 $u_S(t) = 10\sqrt{2} \cos \omega t$ V

求: (1) 频率 ω 为何值时, 电路发生谐振。

(2) 电路谐振时, U_L 和 U_C 为何值。

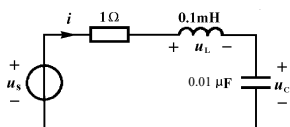

15

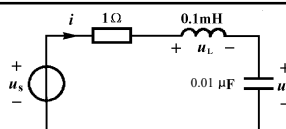

解: (1) 电压源的角频率应为

$$\omega = \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-4} \times 10^{-8}}} \text{ rad/s} = 10^6 \text{ rad/s}$$

(2) 电路的品质因数为


$$Q = \frac{\omega_0 L}{R} = 100$$

则

$$U_L = U_C = QU_s = 100 \times 10 \text{ V} = 1000 \text{ V}$$

16

例2.

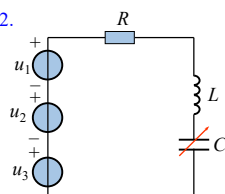

一接收器的电路参数为:

$$L=250\mu\text{H}, R=20\Omega,$$

$$U_1=U_2=U_3=10\mu\text{V},$$


$$f_0=820\text{ kHz}.$$

$$820 \times 10^3 = \frac{1}{2\pi\sqrt{LC}}$$

请问当电容调至 $C=150\text{pF}$ 时谐振, 接收到那个电台的信号?

17

	电台1	电台2	电台3
$f(\text{kHz})$	820	640	1026
$\omega L (\Omega)$	1290	1000	1612
$\frac{1}{\omega C} (\Omega)$	1290	-1660	1034
X	0	-660	577
$I=U/ Z (\mu\text{A})$	$I_0=0.5$	$I_1=0.015$	$I_2=0.017$

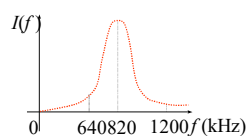 \therefore 收到台820kHz的节目。* 选择性与 Q 有关

18

例3 欲接收载波频率为10MHz的某短波电台的信号, 试设计接收机输入谐振电路的电感线圈。要求带宽 $\Delta f=100\text{kHz}$, $C=100\text{pF}$ 。

解: 由

19