

例3 欲接收载波频率为10MHz的某短波电台的信号，试设计接收机输入谐振电路的电感线圈。要求带宽 $\Delta f=100\text{kHz}$, $C=100\text{pF}$ 。

解: 由 $f_0 = \frac{1}{2\pi\sqrt{LC}}$

求得: $L = \frac{1}{4\pi^2 f_0^2 C} = \frac{1}{4\pi^2 \times 10^{14} \times 10^{-10}} \text{H} = 2.53\mu\text{H}$


$$Q = \frac{f_0}{\Delta f} = \frac{10 \times 10^6}{100 \times 10^3} = 100$$

$$R = \frac{1}{Q\omega_0 C} = \frac{1}{100 \times 2\pi \times 10^7 \times 10^{-10}} \Omega = 1.59\Omega$$

由此得到电感线圈的参数为 $L=2.53\mu\text{H}$ 和 $R=1.59\Omega$ 。

19


2. Parallel Resonance (并联谐振)

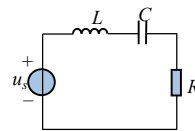

RLC Series Resonance

$$Z = R + j(\omega L - \frac{1}{\omega C})$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

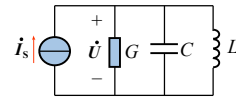



GCL Parallel Resonance

$$Y = G + j(\omega C - \frac{1}{\omega L})$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$



20

RLC Series Resonance

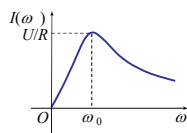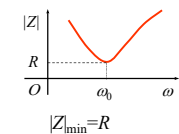

The current is the maximum.


GCL Parallel Resonance

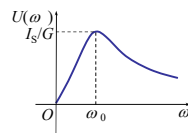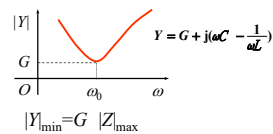

The voltage is the maximum.

21

RLC Series Resonance

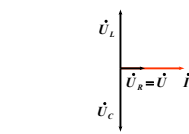


Voltage resonance

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$U_L(\omega_0) = U_C(\omega_0) = QU_S$$

GCL Parallel Resonance

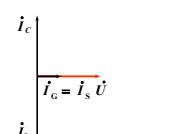

Current resonance

$$Q = \frac{\omega_0 C}{G} = \frac{1}{\omega_0 GL} = \frac{1}{G} \sqrt{\frac{C}{L}}$$

$$I_L(\omega_0) = I_C(\omega_0) = QI_S$$

$$I_C = j\omega_0 C \dot{U} = j\omega_0 C \frac{\dot{I}_s}{G} = jQ \dot{I}_s$$

22

RLC Series Resonance

$P = RI^2 = U^2/R$
 $Q_L = \omega_0 LI^2 \quad Q_C = -\frac{1}{\omega_0 C} I^2$
 $Q = Q_L + Q_C = 0$

GCL Parallel Resonance

$P = UI = I^2/G$
 $Q_L = \frac{U^2}{\omega_0 L} \quad Q_C = -\omega_0 CU^2$
 $Q = Q_L + Q_C = 0$

23

$w_C(t) + w_L(t) = LQ^2 I_s^2$

Notice:
 The parallel LC combination acts like an **open circuit**, so that the entire currents flows through R.
 The inductor and capacitor current can be much more than the source current at resonance.

24

3. Resonance Occurs In RLC Circuit

$Y = j\omega C + \frac{1}{R + j\omega L}$
 $= \frac{R}{R^2 + (\omega L)^2} + j(\omega C - \frac{\omega L}{R^2 + (\omega L)^2})$
 $= G + jB$

Resonant frequency

$\omega_0 C - \frac{\omega_0 L}{R^2 + (\omega_0 L)^2} = 0$
 $\omega_0 = \sqrt{\frac{1}{LC} - (\frac{R}{L})^2}$

Resonance occurs only when: $\frac{1}{LC} > (\frac{R}{L})^2$ or $R < \sqrt{\frac{L}{C}}$

25

Simplification of RLC Circuit

$Y = j\omega C + \frac{1}{R + j\omega L}$
 $= \frac{R}{R^2 + (\omega L)^2} + j(\omega C - \frac{\omega L}{R^2 + (\omega L)^2})$


When $R \ll \omega L$

$Y \approx \frac{R}{(\omega L)^2} + j(\omega C - \frac{1}{\omega L})$
 $G_e = \frac{R}{(\omega_0 L)^2} \quad \omega_0 = \frac{1}{\sqrt{LC}}$

$Q = \frac{\omega_0 C}{G_e} = \frac{\omega_0 C}{R/(\omega_0 L)^2} = \frac{\omega_0^3 CL^2}{R} = \frac{\omega_0 L}{R}$

Quality factor of inductance coil ²⁶

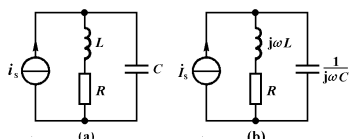例 下图是电感线圈和电容器并联的电路模型。
已知 $R=1\Omega$, $L=0.1\text{mH}$, $C=0.01\mu\text{F}$ 。试求电路的谐振角频率和谐振时的阻抗。



解: $\omega_0 = \frac{1}{\sqrt{10^{-4} \times 10^{-8}}} \sqrt{1 - \frac{10^{-8}}{10^{-4}}} \text{ rad/s} = 10^6 \text{ rad/s}$

$R \ll \omega L \quad Z = \frac{1}{G_e} = \frac{(\omega_0 L)^2}{R} = \frac{10^{-6} \times 10^{-4}}{1} \Omega = 10 \text{ k}\Omega$

27

例 RLC 并联谐振电路中, 已知 $R=10\text{k}\Omega$, $L=1\text{H}$, $C=1\mu\text{F}$ 。试求电路的谐振角频率、品质因数和3dB带宽。

解:

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10^{-6}}} \text{ rad/s} = 10^3 \text{ rad/s}$$


$$Q = R\omega_0 C = \frac{R}{\omega_0 L} = R \sqrt{\frac{C}{L}} = 10$$

$$\Delta\omega = \frac{\omega_0}{Q} = 100 \text{ rad/s} \quad \Delta f = \frac{100}{2\pi} \text{ Hz} = 15.9 \text{ Hz}$$


28

Bode Plots (波特图)

Frequency range

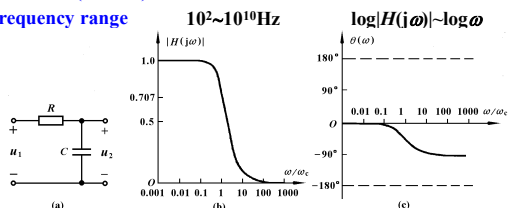

$20\log|H(j\omega)| - \log(\omega/\omega_c)$

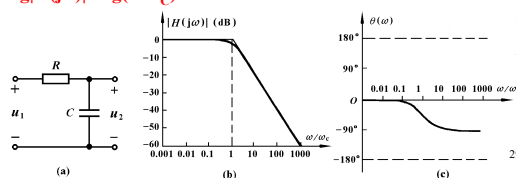

29

Bode Plots (波特图)

$20\log|H(j\omega)| - \log(\omega/\omega_c)$

dB

Becibel Scale (dB, 分贝)

A	0.01	0.1	0.707	1	2	10	100	1000
$20\log A/\text{dB}$	-40	-20	-3.0	0	6.0	20	40	60

30

例: $L_1 = 100\text{mH}$, 要使 $Z_{in}(10^3) = \infty$, 确定 C_1 值; 要使 $Z_{in}(500) = 0$, 在已确定 C_1 情况下, 确定 C_2 值。

解:


L_1 与 C_1 发生并联谐振, $\omega_0 = 10^3 \text{ rad/s}$

$$\therefore \omega_0^2 = \frac{1}{L_1 C_1}, \Rightarrow C_1 = \frac{1}{\omega_0^2 L_1} = \frac{1}{(10^3)^2 \times 100 \times 10^{-3}} = 10 \mu\text{F}$$

在 $\omega_1 = 500 \text{ rad/s}$ 时发生串联谐振

$$Z_{in} = -j \frac{1}{\omega_1 C_2} + \frac{1}{j(\omega_1 C_1 - \frac{1}{\omega_1 L_1})} = 0$$
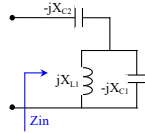
$$\frac{-1}{\omega_1 C_2} = \frac{1}{\omega_1 C_1 - \frac{1}{\omega_1 L_1}} \Rightarrow C_2 = 30 \mu\text{F}$$



31

例: 测电感 L 的电阻与电感, 角频率 $\omega = 10^3 \text{ rad/s}$, $I_s = 1\text{A}$, $C = 50 \mu\text{F}$ 时, 电压表读数为最大, $U = 50\text{V}$ 。求 R 、 L 。

解:

$$Y = \frac{R}{R^2 + (\omega L)^2} - j \left(\frac{\omega L}{R^2 + (\omega L)^2} - \omega C \right)$$

$$= G - j(B_L - B_C) = G - jB = ye^{-j\theta}$$

$$\text{电压表: } U = \frac{I_s}{y}$$


y 最小时 U 最大, 改变 C 不影响 G 。

$$\therefore B = 0 \text{ (并联谐振) 时 } U \text{ 最大。} \Rightarrow G = \frac{I_s}{U} = \frac{1}{50} = 0.02\text{S}$$

$$B_L = B_C = \omega C = 10^3 \times 50 \times 10^{-6} = 0.05\text{S}$$

$$\frac{R}{R^2 + (\omega L)^2} = G = 0.02 \Rightarrow \omega L = 17.24\Omega, L = 17.2\text{mH}$$


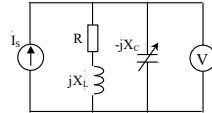
$$\frac{\omega L}{R^2 + (\omega L)^2} = B_L = 0.05 \Rightarrow R = 6.9\Omega$$



32

Example Resonance occurs in the circuit, then $U=100\text{V}$, $I_1=I_2=10\text{A}$, Calculate: R , X_L and X_C

Solution: Phasor Diagrams

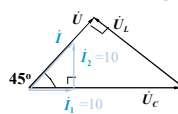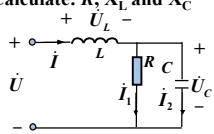

According to the current triangle $I = 14.14\text{A}$

According to the voltage triangle

$$U_L = U = 100\text{V} \quad U_C = 141.4\text{V}$$



$$R = U_C / I_1 = 14.14\Omega, \quad X_C = -U_C / I_2 = -14.14\Omega$$

$$X_L = U_L / I = 7.07\Omega$$

33

Example Resonance occurs when $\omega = 1000\text{rad/s}$, we know $R_0 = 25\Omega$, $C = 16 \mu\text{F}$, the reading of voltmeter is 100V , the reading of Ammeter is 1.2A , calculate R and L 。

Solution: Phasor Diagrams

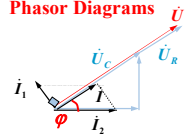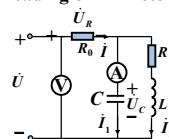

$$I_1 = 1.2\text{A}$$

$$U_C = \frac{1.2}{(1000 \times 1.6 \times 10^{-6})} = 75\text{V}$$

According to the resonance condition

$$U_R = 25\text{V} \quad I = 1\text{A}$$

$$I_2 = \sqrt{I_1^2 + I^2} = 1.562\text{A}$$

$$\phi = \arctan(I_1 / I) = 50.2^\circ$$

$$|Z| = U / I_2 = 75 / 1.562 = 48.01\Omega$$

$$R = 48.01 \cos 50.2^\circ = 30.7\Omega$$

$$L = 48.01 \sin 50.2^\circ / 1000 = 36.9\text{mH}$$

34