

Transmission of energy(传送功率)

$$Z_I = \frac{(\omega M)^2}{Z_{22}} = \frac{\omega^2 M^2}{R_{22} + jX_{22}} = \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} - \frac{j\omega^2 M^2 X_{22}}{R_{22}^2 + X_{22}^2}$$

$$= R_I + jX_I$$

$$R_I = \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} \quad R_I > 0, \text{ absorbing power, providing by primary coil}$$


$$\text{Power developed by source} = \text{Power absorbed by load} = I_1^2 R_I + I_1^2 R_L$$

absorbing by primary coil absorbing by secondary coil, transferring by mutual inductance

$$I_1^2 R_I^2 = I_2^2 R_{22}$$

53

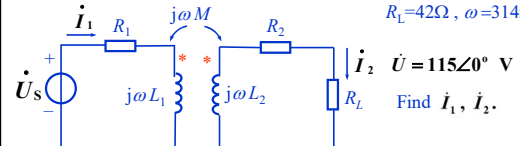Example 1. $L_1=3.6\text{H}$, $L_2=0.06\text{H}$, $M=0.465\text{H}$, $R_1=20\Omega$, $R_2=0.08\Omega$, $R_L=42\Omega$, $\omega=314\text{rad/s}$, $\dot{U}=115\angle 0^\circ \text{ V}$



Find \dot{I}_1 , \dot{I}_2 .


Solution 1: Mesh Analysis

$$\begin{cases} \dot{I}_1(R_1 + j\omega L_1) - \dot{I}_2 j\omega M = \dot{U}_s \\ \dot{I}_2(R_2 + R_L + j\omega L_2) - \dot{I}_1 j\omega M = 0 \end{cases}$$

$$\dot{I}_1 = 110.5\angle(-64.9^\circ) \text{ A} \quad \dot{I}_2 = 0.351\angle 1^\circ \text{ A}$$

54

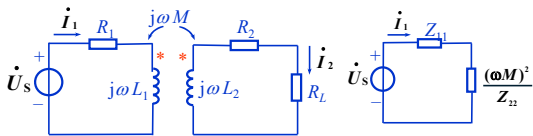Solution 2: Primary coil equivalent circuit of linear transformer



$$Z_{11} = R_1 + j\omega L_1 = 20 + j1130.4\Omega$$


$$Z_{22} = R_2 + R_L + j\omega L_2 = 42.08 + j18.85\Omega$$

$$Z_I = \frac{X_{22}^2}{Z_{22}} = 464\angle(-24.1^\circ) \Omega$$

$$\dot{I}_1 = \frac{\dot{U}_s}{Z_{11} + Z_I} = 110.5\angle(-64.9^\circ) \text{ A} \quad \dot{I}_2 = \frac{j\omega M \dot{I}_1}{Z_{22}} = 0.351\angle 1^\circ \text{ A}$$

55

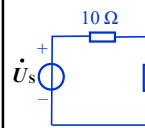
Example 2. $U_s=20\text{V}$, add a transformer between the source and load, proof that the circuit transfers maximum power transfer, Find P_I .



Solution:

Reflected impedance
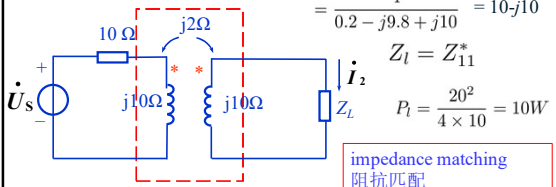
$$Z_I = \frac{(\omega M)^2}{Z_{22}} = \frac{4}{0.2 - j9.8 + j10} = 10 - j10$$




$$Z_I = Z_{11}^*$$

$$P_I = \frac{20^2}{4 \times 10} = 10\text{W}$$

impedance matching
阻抗匹配

56

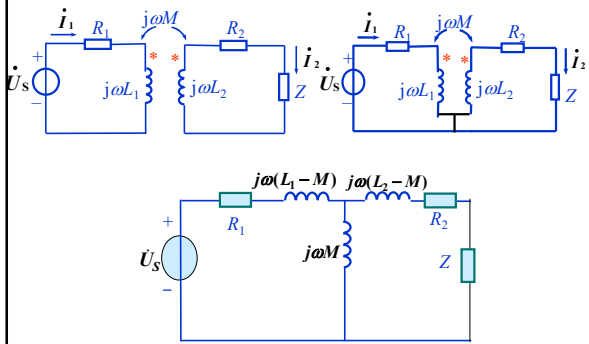T equivalent circuit of linear transformer



57

13.5 The Ideal Transformer


An ideal transformer is the limiting case of two coupled inductors where the inductances approach infinitely and coupling is perfect.

$$K = \frac{M}{\sqrt{L_1 L_2}}$$

$$M = \sqrt{L_1 L_2}$$

$$\dot{U}_1 = j\omega L_1 \dot{I}_1 + j\omega M \dot{I}_2$$
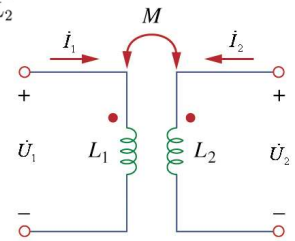
$$\dot{U}_2 = j\omega M \dot{I}_1 + j\omega L_2 \dot{I}_2$$



58

$$\begin{cases} \dot{U}_1 = j\omega L_1 \dot{I}_1 + j\omega M \dot{I}_2 \\ \dot{U}_2 = j\omega L_2 \dot{I}_2 + j\omega M \dot{I}_1 \\ \dot{I}_1 = \frac{\dot{U}_2 - j\omega L_2 \dot{I}_2}{j\omega M} \end{cases}$$

$$\dot{U}_1 = \frac{L_1}{M} (\dot{U}_2 - j\omega L_2 \dot{I}_2) + j\omega M \dot{I}_2 = \frac{L_1}{M} \dot{U}_2$$


$$\text{全耦合时: } M = \sqrt{L_1 L_2}, k = 1$$

$$\frac{\dot{U}_1}{\dot{U}_2} = \frac{L_1}{M} = \frac{M}{L_2} = \sqrt{\frac{L_1}{L_2}} = \frac{N_1}{N_2} = n$$

n 称为变比

59

从磁通分析:

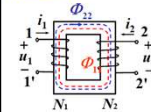

$$u_1 = N_1 \frac{d\Phi_1}{dt}, u_2 = N_2 \frac{d\Phi_2}{dt}$$

$$\Phi_1 = \Phi_2 = \Phi_{11} + \Phi_{22}$$

$$\frac{u_1}{u_2} = \frac{N_1}{N_2} = n$$

$$\dot{U}_1 = j\omega L_1 \dot{I}_1 + j\omega M \dot{I}_2$$

$$\dot{I}_1 = \frac{\dot{U}_1 - j\omega M \dot{I}_2}{j\omega L_1} = \frac{\dot{U}_1}{j\omega L_1} - \frac{j\omega M}{j\omega L_1} \dot{I}_2 = \frac{\dot{U}_1}{j\omega L_1} - \frac{1}{n} \dot{I}_2$$

全耦合变压器的电压、电流关系:

$$\begin{cases} \dot{U}_1 = n \dot{U}_2 \\ \dot{I}_1 = \frac{\dot{U}_1}{j\omega L_1} - \frac{1}{n} \dot{I}_2 \end{cases}$$

60


A transformer is said to be ideal if it has the following properties:

1. Coils have very large reactances ($L_1 \rightarrow \infty, L_2 \rightarrow \infty, M \rightarrow \infty$)
2. Coupling coefficient is equal to unity ($k=1$)
3. Primary and secondary coils are lossless ($R_1 = R_2 = 0$)

An ideal transformer is a unity-coupled, lossless transformer in which the primary and secondary coils have infinite self-inductances


61

Circuit symbol for ideal transformer

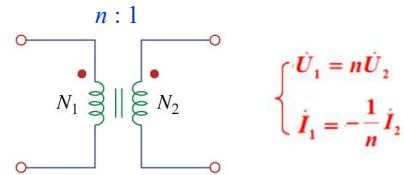


62

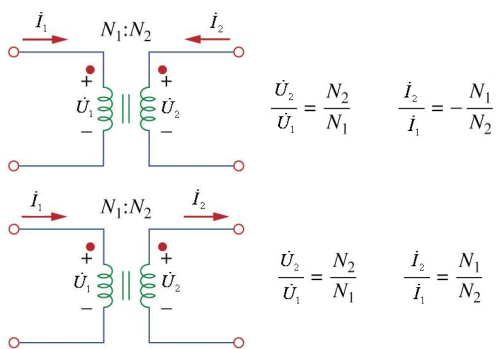The different relationships between the polarity of the voltages and the direction of the currents for the transformer




63

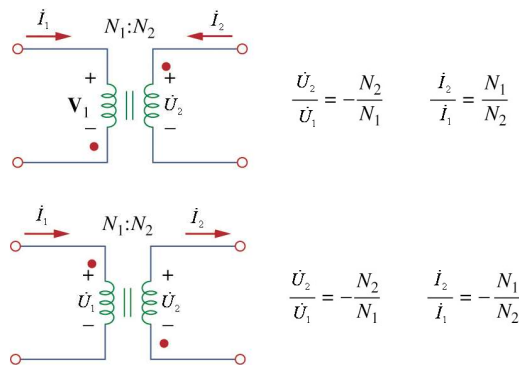

64

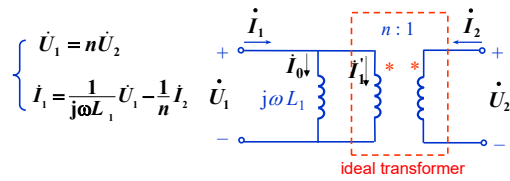
A unity-coupled transformer by using circuit symbol of ideal transformer



65

Characteristics of ideal transformer

(1) Impedance transformation

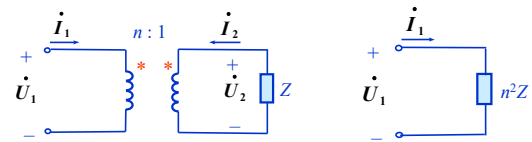


$$\frac{\dot{U}_1}{\dot{I}_1} = \frac{n\dot{U}_2}{-1/n\dot{I}_2} = n^2 \left(-\frac{\dot{U}_2}{\dot{I}_2} \right) = n^2 Z$$

66

Characteristics of ideal transformer

(2) Power consumption

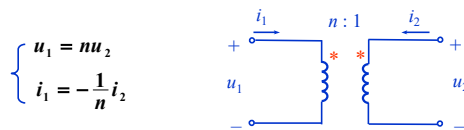


$$p = u_1 i_1 + u_2 i_2 = u_1 i_1 + \frac{1}{n} u_1 \times (-ni_1) = 0$$

The ideal transformer absorbs no power, which is lossless.

67

Example 1

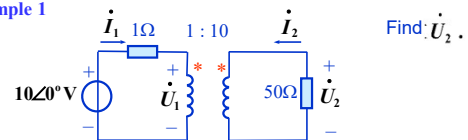


Solution 1: Mesh Analysis


$$\begin{cases} 1 \times \dot{I}_1 + \dot{U}_1 = 10\angle 0^\circ \\ 50\dot{I}_2 + \dot{U}_2 = 0 \\ \dot{U}_1 = \frac{1}{10}\dot{U}_2 \\ \dot{I}_1 = -10\dot{I}_2 \end{cases} \quad \begin{matrix} \text{obtained} \\ \Rightarrow \end{matrix} \quad \dot{U}_2 = 33.33\angle 0^\circ \text{ V}$$

68

Solution 2: Impedance transformation

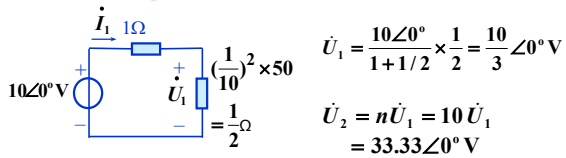


Solution 3: Thevenin equivalent circuit

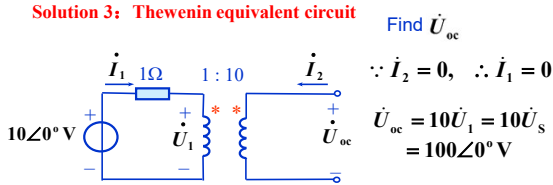


69

Find R_0 :

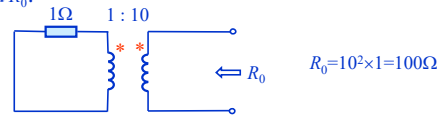


Thevenin equivalent circuit

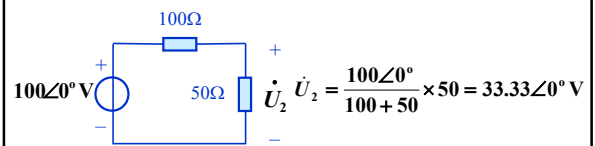

70

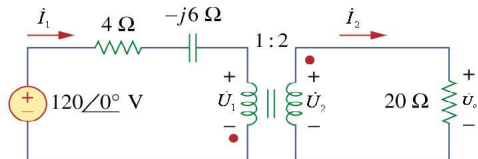Example 2 For the ideal transformer circuit shown in Fig., find: (1) the source current \dot{I}_1 , (b) the output \dot{U}_o , and (c) the complex power supplied by the source.



Solution:


(1) The impedance can be reflected to the primary side and we get

$$\mathbf{Z}_R = \frac{20}{n^2} = \frac{20}{4} = 5\Omega$$

$$\mathbf{Z}_{in} = 4 - j6 + \mathbf{Z}_R = 9 - j6 = 10.82\angle -33.69^\circ \Omega$$

$$\mathbf{I}_1 = \frac{120\angle 0^\circ}{\mathbf{Z}_{in}} = \frac{120\angle 0^\circ}{10.82\angle -33.69^\circ} = 11.09\angle 33.69^\circ \text{ A}$$

71

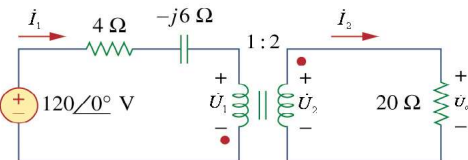

(2) Since both \dot{I}_1 and \dot{I}_2 leave the dotted terminals

$$\mathbf{I}_2 = -\frac{1}{n}\mathbf{I}_1 = -5.545\angle 33.69^\circ \text{ A}$$


$$\mathbf{V}_o = 20\mathbf{I}_2 = 110.9\angle 213.69^\circ \text{ V}$$

(3) The complex power supplied is

$$\mathbf{S} = \mathbf{V}_s \mathbf{I}_1^* = (120\angle 0^\circ)(11.09\angle -33.69^\circ) = 1,330.8\angle -33.69^\circ \text{ VA}$$

72

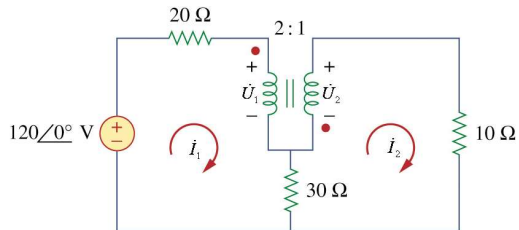Example 3 Calculate the power supplied to 10-Ω resistor in the ideal transformer circuit shown in the following Fig.



73

Solution:

There is direct connection between the primary and secondary sides due to the 30-Ω resistor. We apply mesh analysis.

For mesh 1,

$$-120 + (20 + 30)I_1 - 30I_2 + V_1 = 0$$

$$50I_1 - 30I_2 + V_1 = 120$$

For mesh 2,

$$-V_2 + (10 + 30)I_2 - 30I_1 = 0$$

$$-30I_1 + 40I_2 - V_2 = 0$$

$$I_2 = -\frac{120}{165} = -0.7272 \text{ A}$$


$$P = (-0.7272)^2(10) = 5.3 \text{ W}$$

$$V_2 = -\frac{1}{2}V_1$$

$$I_2 = -2I_1$$


74

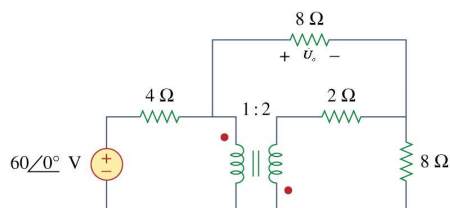Practice Find \dot{U}_o in the circuit shown in following Fig.



75

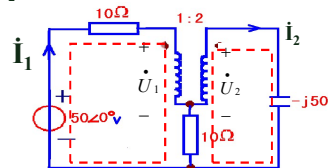Example 4 In the circuit shown in following Fig., find $\dot{I}_1 = ?$ $\dot{I}_2 = ?$



Solution Using mesh analysis:

$$20\dot{I}_1 - 10\dot{I}_2 = 50\angle 0^\circ - \dot{U}_1 \quad \dot{U}_2 = 2\dot{U}_1 \quad \dot{I}_2 = \frac{1}{2}\dot{I}_1$$

$$-10\dot{I}_1 + (10 - j50)\dot{I}_2 = \dot{U}_2 \quad \therefore \dot{I}_1 = 2 + j2(A)$$

$$\dot{I}_2 = 1 + j1(A)$$

76

Summary

- Dot Convention.
- Decoupling Equivalent Circuit
 - series connection $L = L_1 + L_2 + 2M$
 - parallel connection
 - T-connection
- Linear Transformer $Z_1 = \frac{(\omega M)^2}{Z_{22}}$;
- Ideal transformer

$$\begin{cases} u_1 = nu_2 \\ i_1 = -\frac{1}{n}i_2 \end{cases} \quad n^2 Z$$

77